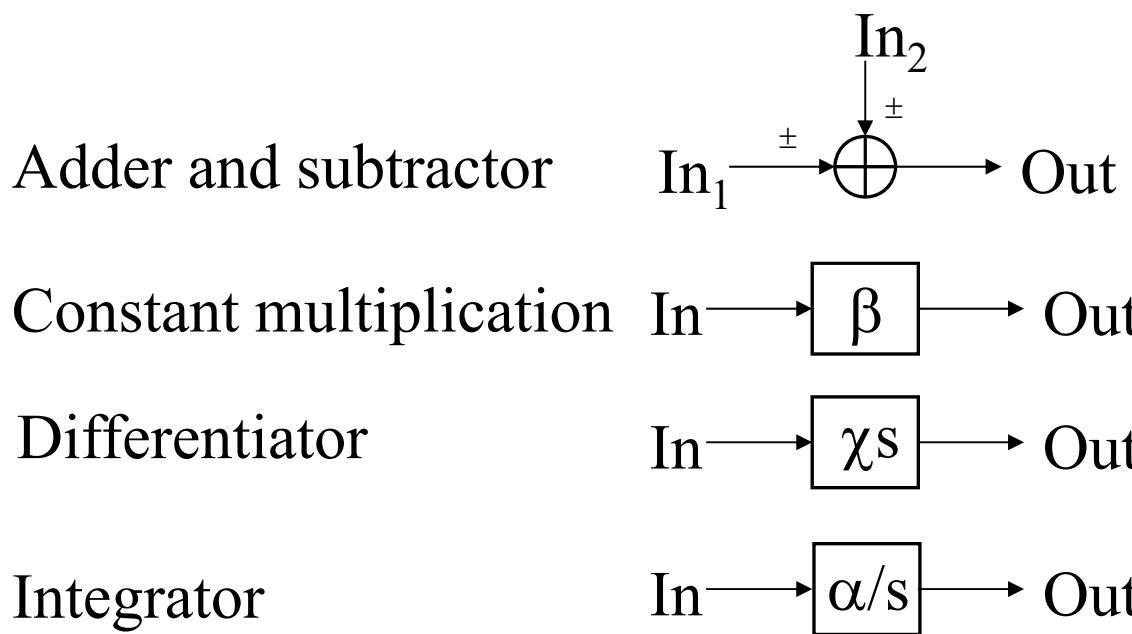


## 2. Circuit implementation of the transfer function

Kanazawa University  
Microelectronics Research Lab.  
Akio Kitagawa


## 2.1 Block diagram of continuous-time circuit

# Linear elements for continuous-time circuit



The parameters  $\beta$ ,  $\chi$ , and  $\alpha$  are the gain of an amplifier, a differentiator, and an integrator, respectively.

# Block diagram of 1st-order LPF

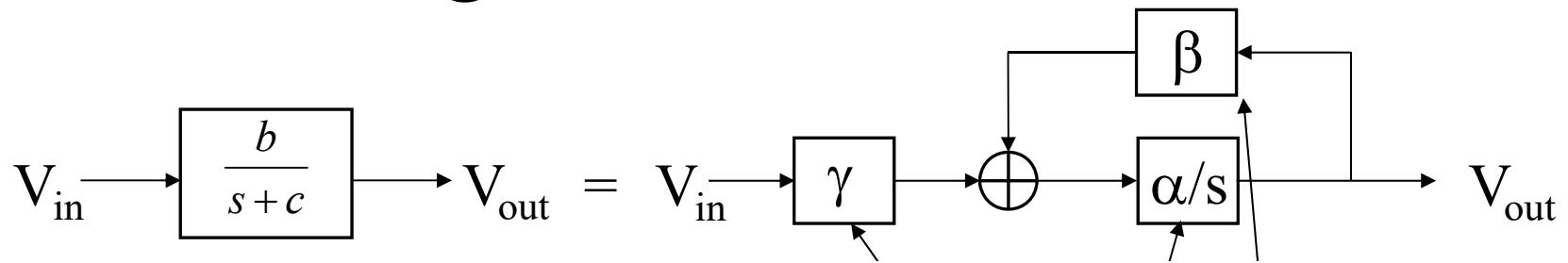

Transfer function

$$\frac{V_{out}}{V_{in}} = \frac{b}{s + c}$$

$$(s + c) \cdot V_{out} = b \cdot V_{in}$$

$$V_{out} = \frac{1}{s} (b \cdot V_{in} - c \cdot V_{out}) = \frac{\alpha}{s} \left( \frac{b}{\alpha} V_{in} - \frac{c}{\alpha} V_{out} \right) \equiv \frac{\alpha}{s} (\gamma \cdot V_{in} + \beta \cdot V_{out})$$

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{b}{s + c} = \frac{\alpha \cdot \gamma}{s - \alpha \cdot \beta} \quad \left\{ \begin{array}{l} b = \alpha \cdot \gamma \\ c = -\alpha \cdot \beta \end{array} \right.$$

NOTE: A feedback of a constant introduces a constant term in a denominator.

# Block diagram of 1st-order HPF

$$V_{\text{in}} \rightarrow \boxed{\frac{a \cdot s}{s + c}} \rightarrow V_{\text{out}}$$


Transfer function

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{a \cdot s}{s + c}$$


$$(s + c) \cdot V_{\text{out}} = a \cdot s \cdot V_{\text{in}}$$

$$V_{\text{out}} = \frac{1}{s} (a \cdot s \cdot V_{\text{in}} - c \cdot V_{\text{out}}) = \frac{\alpha}{s} \left( \frac{a}{\alpha} s \cdot V_{\text{in}} - \frac{c}{\alpha} V_{\text{out}} \right) \equiv \frac{\alpha}{s} (\chi \cdot s \cdot V_{\text{in}} + \beta \cdot V_{\text{out}})$$
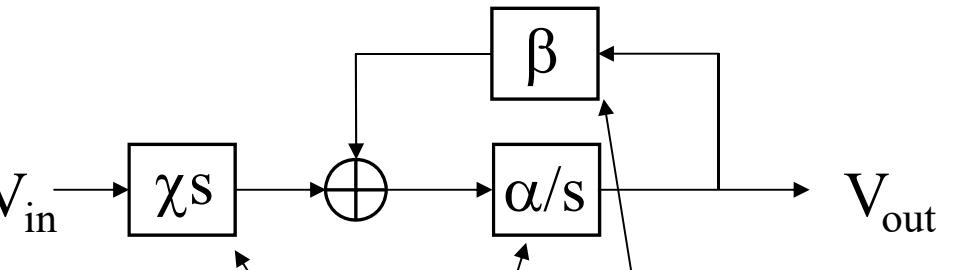
$$H(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{a \cdot s}{s + c} = \frac{\alpha \cdot \chi \cdot s}{s - \alpha \cdot \beta}$$



Block diagram of transfer function

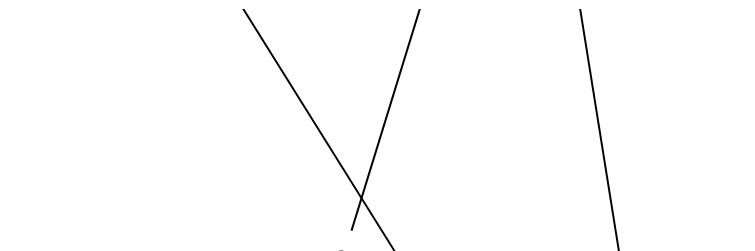

$$\left\{ \begin{array}{l} a = \alpha \cdot \chi \\ c = -\alpha \cdot \beta \end{array} \right.$$

# Block diagram of 1st-order transfer function

$$V_{\text{in}} \rightarrow \boxed{\frac{a \cdot s + b}{s + c}} \rightarrow V_{\text{out}}$$


Transfer function

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{a \cdot s + b}{s + c}$$

$$(s + c) \cdot V_{\text{out}} = (a \cdot s + b) \cdot V_{\text{in}}$$

$$V_{\text{out}} = \frac{1}{s} (a \cdot s \cdot V_{\text{in}} + b \cdot V_{\text{in}} - c \cdot V_{\text{out}}) = \frac{\alpha}{s} \left( \frac{a}{\alpha} s \cdot V_{\text{in}} + \frac{b}{\alpha} V_{\text{in}} - \frac{c}{\alpha} V_{\text{out}} \right) \equiv \frac{\alpha}{s} (\chi \cdot s \cdot V_{\text{in}} + \gamma \cdot V_{\text{in}} + \beta \cdot V_{\text{out}})$$
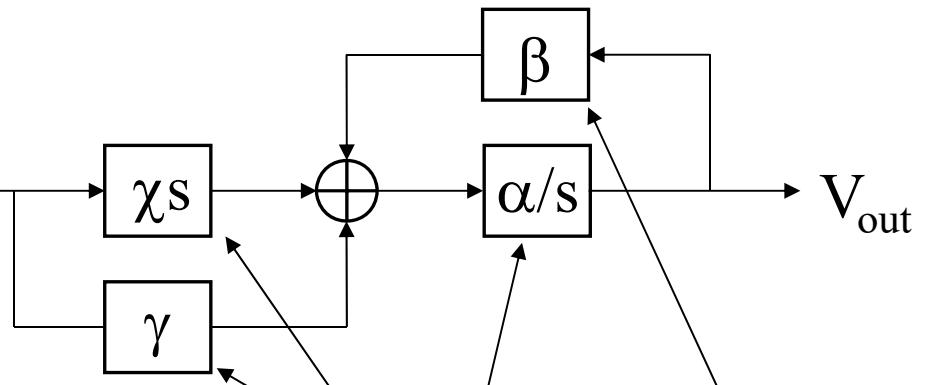
$$H(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{a \cdot s + b}{s + c} = \frac{\alpha \cdot \chi \cdot s + \alpha \cdot \gamma}{s - \alpha \cdot \beta}$$




Block diagram of transfer function

$$\left\{ \begin{array}{l} a = \alpha \cdot \chi \\ b = \alpha \cdot \gamma \\ c = -\alpha \cdot \beta \end{array} \right.$$
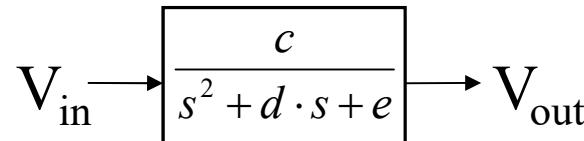
# Block diagram of 2nd-order LPF 1


$$\frac{V_{out}}{V_{in}} = \frac{c}{s^2 + d \cdot s + e}$$

$$(s^2 + d \cdot s + e) \cdot V_{out} = c \cdot V_{in}$$



$$V_{out} = \frac{1}{s^2} (c \cdot V_{in} - d \cdot s \cdot V_{out} - e \cdot V_{out}) = \frac{1}{s} \left\{ \frac{1}{s} (c \cdot V_{in} - e \cdot V_{out}) - d \cdot V_{out} \right\}$$
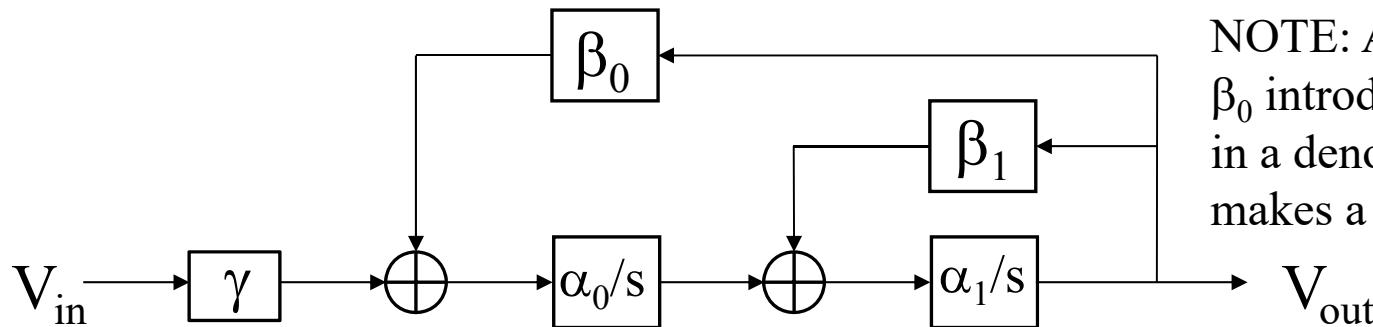
$$= \frac{\alpha_1}{s} \left\{ \frac{\alpha_0}{s} \left( \frac{c}{\alpha_1 \alpha_0} V_{in} - \frac{e}{\alpha_1 \alpha_0} V_{out} \right) - \frac{d}{\alpha_1} V_{out} \right\} \equiv \frac{\alpha_1}{s} \left\{ \frac{\alpha_0}{s} (\gamma \cdot V_{in} + \beta_0 \cdot V_{out}) + \beta_1 \cdot V_{out} \right\}$$



NOTE: A feedback element  $\beta_0$  introduces a constant term in a denominator, and  $\beta_1$  makes a design flexibility.


$$H(s) = \frac{V_{out}}{V_{in}} = \frac{c}{s^2 + d \cdot s + e} = \frac{\alpha_0 \cdot \alpha_1 \cdot \gamma}{s^2 - \alpha_1 \cdot \beta_1 \cdot s - \alpha_0 \cdot \alpha_1 \cdot \beta_0}$$

$$\begin{cases} c = \alpha_0 \cdot \alpha_1 \cdot \gamma \\ d = -\alpha_1 \cdot \beta_1 \\ e = -\alpha_0 \cdot \alpha_1 \cdot \beta_0 \end{cases}$$
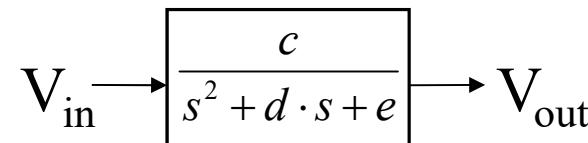
# Block diagram of 2nd-order LPF 2


$$\frac{V_{out}}{V_{in}} = \frac{c}{s^2 + d \cdot s + e}$$

$$(s^2 + d \cdot s + e) \cdot V_{out} = c \cdot V_{in}$$



$$V_{out} = \frac{1}{s^2} (c \cdot V_{in} - d \cdot s \cdot V_{out} - e \cdot V_{out}) = \frac{\alpha_1}{s} \frac{\alpha_0}{s} \left( \frac{c}{\alpha_1 \alpha_0} \cdot V_{in} - \frac{d}{\alpha_0} \frac{s}{\alpha_1} V_{out} - \frac{e}{\alpha_1 \alpha_0} V_{out} \right)$$
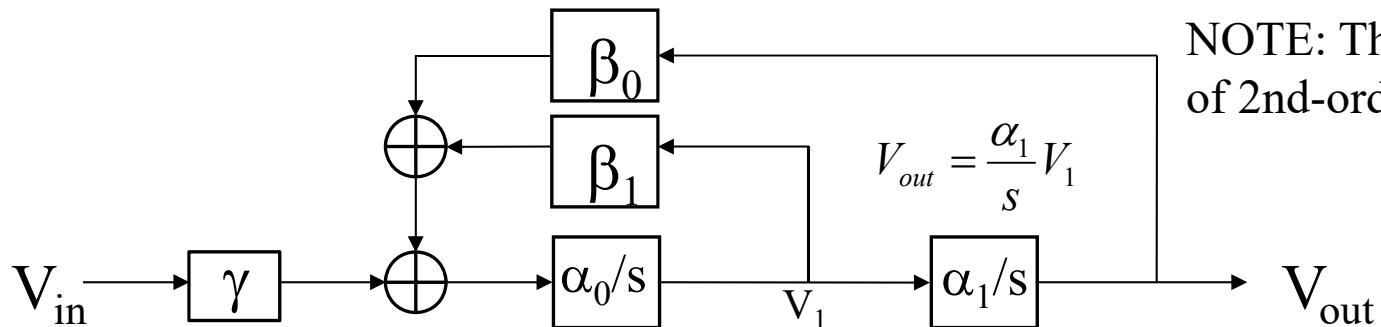
$$= \frac{\alpha_1}{s} \frac{\alpha_0}{s} \left( \frac{c}{\alpha_1 \alpha_0} \cdot V_{in} - \frac{d}{\alpha_0} V_1 - \frac{e}{\alpha_1 \alpha_0} V_{out} \right) \equiv \frac{\alpha_1}{s} \frac{\alpha_0}{s} (\gamma \cdot V_{in} + \beta_1 \cdot V_1 + \beta_0 \cdot V_{out})$$



NOTE: This is another solution of 2nd-order LPF.


$$H(s) = \frac{V_{out}}{V_{in}} = \frac{c}{s^2 + d \cdot s + e} = \frac{\alpha_0 \cdot \alpha_1 \cdot \gamma}{s^2 - \alpha_1 \cdot \beta_1 \cdot s - \alpha_0 \cdot \alpha_1 \cdot \beta_0}$$

$$\begin{cases} c = \alpha_0 \cdot \alpha_1 \cdot \gamma \\ d = -\alpha_0 \cdot \beta_1 \\ e = -\alpha_0 \cdot \alpha_1 \cdot \beta_0 \end{cases}$$
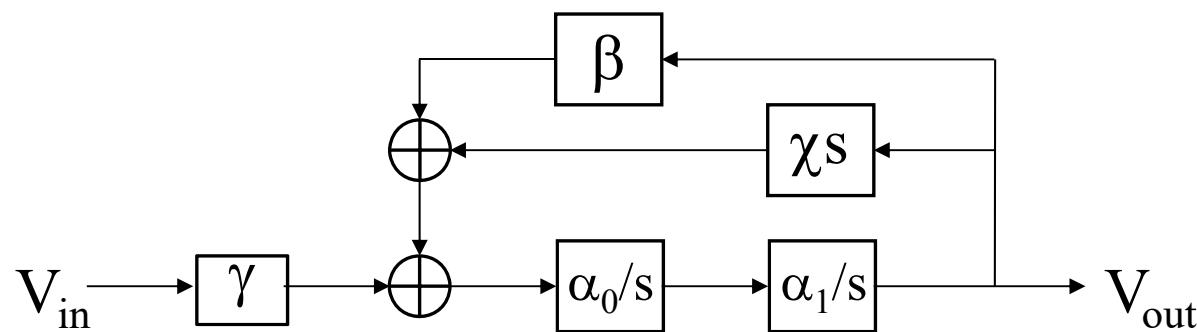
# Block diagram of 2nd-order LPF 3

$$\begin{aligned}
 V_{out} &= \frac{1}{s^2} (c \cdot V_{in} - d \cdot s \cdot V_{out} - e \cdot V_{out}) \\
 &= \frac{\alpha_0}{s} \frac{\alpha_1}{s} \left( \frac{c}{\alpha_0 \alpha_1} V_{in} - \frac{d}{\alpha_0 \alpha_1} s \cdot V_{out} - \frac{e}{\alpha_0 \alpha_1} V_{out} \right) \\
 &\equiv \frac{\alpha_0}{s} \frac{\alpha_1}{s} (\gamma \cdot V_{in} + \chi \cdot s \cdot V_{out} + \beta \cdot V_{out})
 \end{aligned}$$

$$V_{in} \rightarrow \boxed{\frac{c}{s^2 + d \cdot s + e}} \rightarrow V_{out}$$



$$H(s) = \frac{V_{out}}{V_{in}} = \frac{c}{s^2 + d \cdot s + e} = \frac{\alpha_0 \cdot \alpha_1 \cdot \gamma}{s^2 - \alpha_0 \cdot \alpha_1 \cdot \chi \cdot s - \alpha_0 \cdot \alpha_1 \cdot \beta} \quad \leftarrow \quad \begin{cases} c = \alpha_0 \cdot \alpha_1 \cdot \gamma \\ d = -\alpha_0 \cdot \alpha_1 \cdot \chi \\ e = -\alpha_0 \cdot \alpha_1 \cdot \beta \end{cases}$$

9


# Block diagram of 2nd-order transfer function

$$\frac{V_{out}}{V_{in}} = \frac{a \cdot s^2 + b \cdot s + c}{s^2 + d \cdot s + e}$$

$$V_{out} = \frac{1}{s^2} (a \cdot s^2 \cdot V_{in} + b \cdot s \cdot V_{in} + c \cdot V_{in}) + \frac{1}{s^2} (-d \cdot s \cdot V_{out} - e \cdot V_{out})$$

$$= \frac{\alpha_0}{s} \frac{\alpha_1}{s} \frac{c}{\alpha_0 \alpha_1} \cdot V_{in} + \frac{\alpha_1}{s} \left( \frac{a}{\alpha_1} \cdot s \cdot V_{in} + \frac{b}{\alpha_1} \cdot V_{in} \right) + \frac{\alpha_0}{s} \frac{\alpha_1}{s} \left( -\frac{d}{\alpha_0 \alpha_1} \cdot s \cdot V_{out} - \frac{e}{\alpha_0 \alpha_1} \cdot V_{out} \right)$$

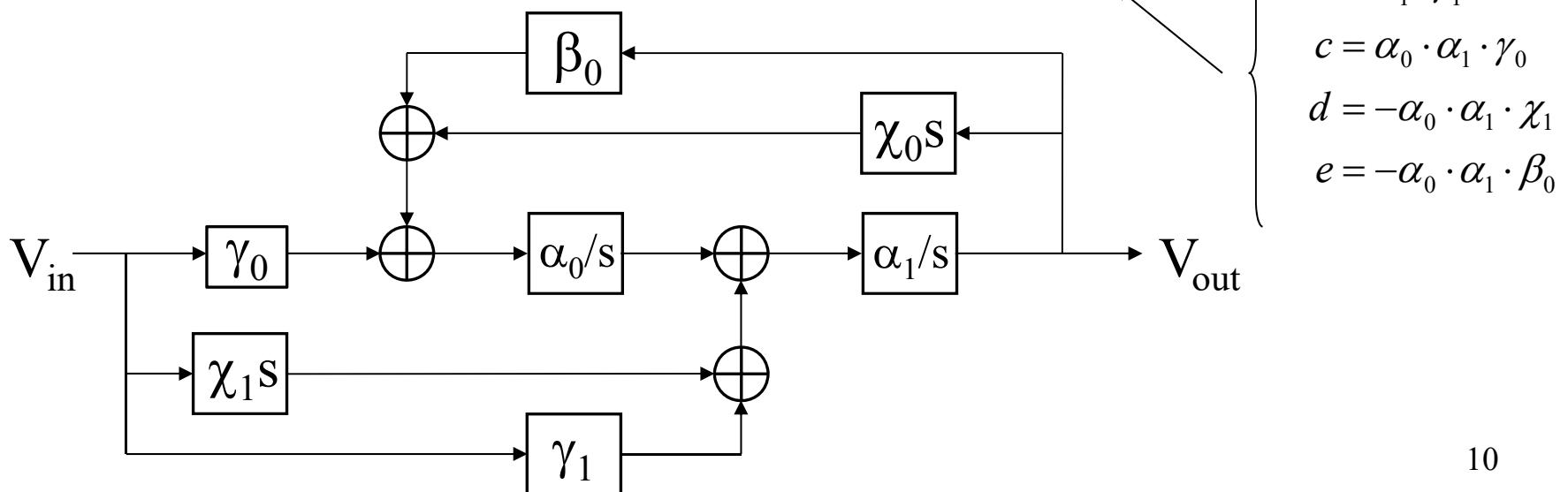
$$\equiv \frac{\alpha_0}{s} \frac{\alpha_1}{s} \gamma_0 \cdot V_{in} + \frac{\alpha_1}{s} (\chi_1 \cdot s \cdot V_{in} + \gamma_1 \cdot V_{in}) + \frac{\alpha_0}{s} \frac{\alpha_1}{s} (\chi_0 \cdot s \cdot V_{out} + \beta_0 \cdot V_{out})$$


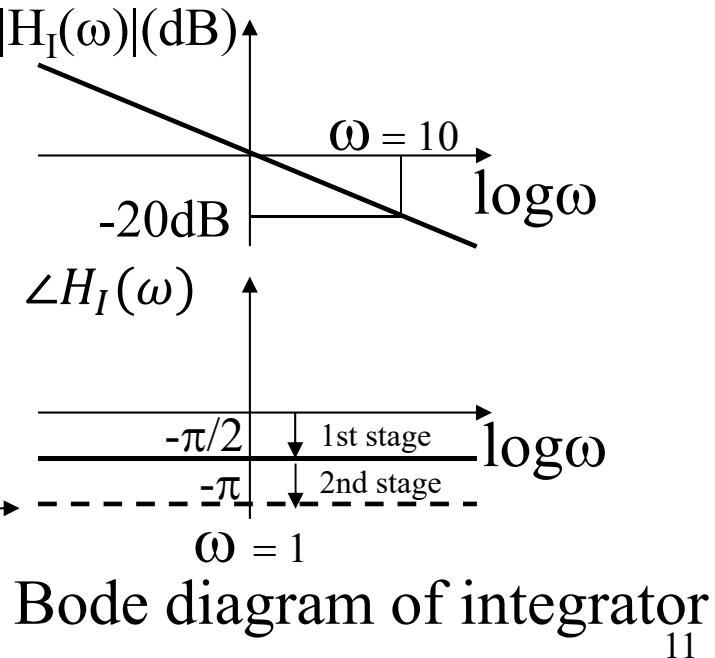
# Stability of higher order transfer function


- A 2-stage-cascade connection of the integrators or differentiators can cause instability of the circuit with the feedback loop, because of the phase rotation  $> \pi$ . In the worst case, the circuit unexpectedly oscillates.

The feedback loop with the phase shift  $> \pi$  causes the negative feedback (NFB) or positive feedback (PFB).



# Stability and distribution of pole

Pole	Impulse response
positive real number	exponential growth
conjugate complex number	divergent vibration
pure imaginary number	steady-state vibration

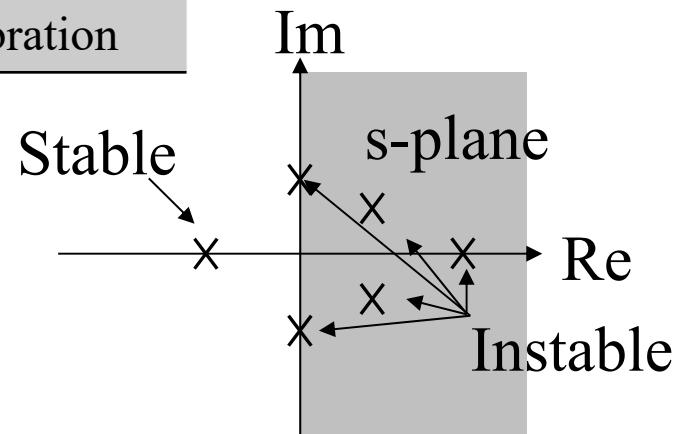

You can simply check the stability of the circuit with the pole arrangement of the transfer function. **The poles on the imaginary axis and right half plane cause the instability of the circuit.**

## 2.2 Block diagram of discrete-time circuit


# Integrator and differentiator (1)

Integrator by BET

$$V_{out}(z) = \frac{T_S}{1 - z^{-1}} V_{in}(z)$$

Differentiator by BET

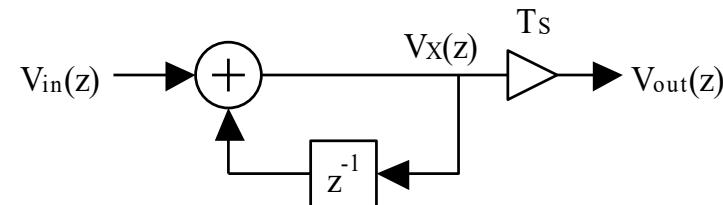
$$V_{out}(z) = \frac{1 - z^{-1}}{T_S} V_{in}(z)$$



$$V_X(z) = V_{in}(z) + z^{-1}V_X(z)$$

$$V_X(z) = \frac{V_{in}(z)}{1 - z^{-1}}$$
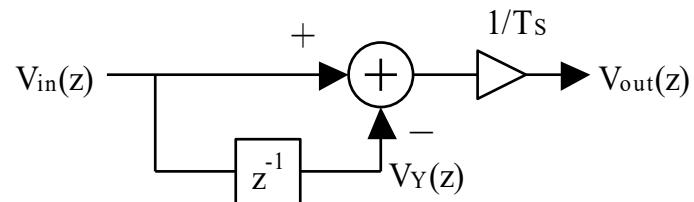
$$V_{out}(z) = T_S \cdot V_X(z) = \frac{T_S}{1 - z^{-1}} V_{in}(z)$$



$$V_Y(z) = z^{-1}V_{in}(z)$$

$$V_{out}(z) = \frac{1}{T_S} \{-z^{-1}V_{in}(z) + V_{in}(z)\}$$

$$= \frac{1 - z^{-1}}{T_S} V_{in}(z)$$


# Integrator and differentiator (2)

Integrator by bilinear transform

$$V_{out}(z) = \frac{T_S}{2} \frac{1+z^{-1}}{1-z^{-1}} V_{in}(z)$$

Differentiator by bilinear transform

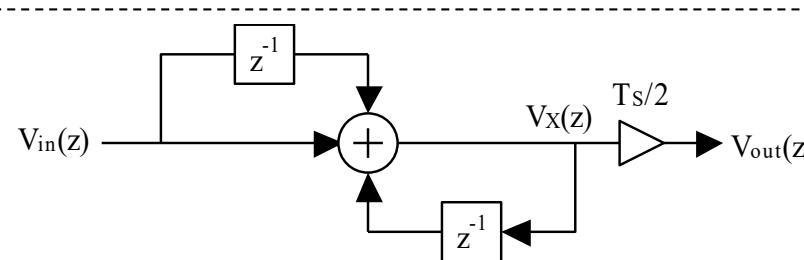
$$V_{out}(z) = \frac{2}{T_S} \frac{1-z^{-1}}{1+z^{-1}} V_{in}(z)$$



$$V_X(z) = (1+z^{-1})V_{in}(z) + z^{-1}V_X(z)$$

$$(1-z^{-1})V_X(z) = (1+z^{-1})V_{in}(z)$$
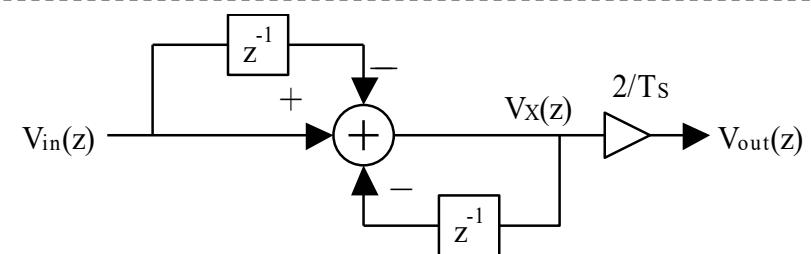
$$V_{out}(z) = \frac{T_S}{2} V_X(z) = \frac{T_S}{2} \frac{1+z^{-1}}{1-z^{-1}} V_{in}(z)$$



$$V_X(z) = (1-z^{-1})V_{in}(z) - z^{-1}V_X(z)$$


$$(1+z^{-1})V_X(z) = (1-z^{-1})V_{in}(z)$$

$$V_{out}(z) = \frac{2}{T_S} V_X(z) = \frac{2}{T_S} \frac{1-z^{-1}}{1+z^{-1}} V_{in}(z)$$


# Integrator
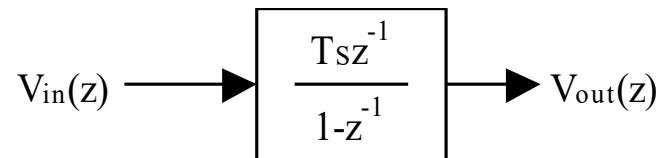
## Integrator by FET

$$V_{out}(z) = \frac{T_s \cdot z^{-1}}{1 - z^{-1}} V_{in}(z)$$



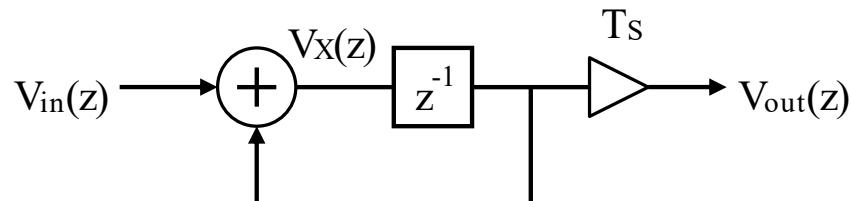The FET integrator is equivalent to the BET integrator + the delay element of  $T_s$ .




NOTE: The integrator and delaying integrator show the same characteristic except for delay time. The delaying integrator **does not output the hazard** generated by the adder.

# Block diagram of variable s and z

Examples of 1st-order LPF


variable s

Continuous-time analog circuits

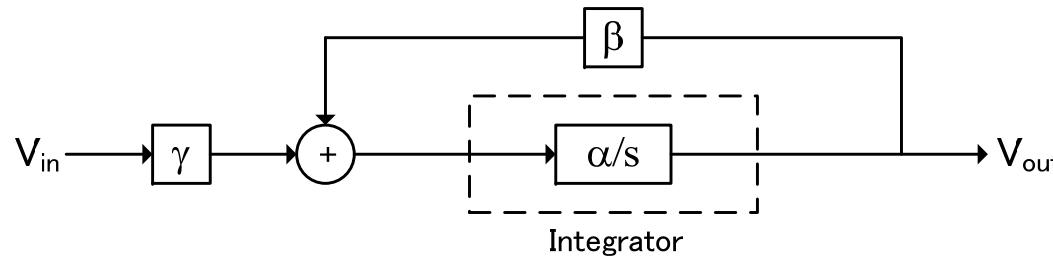

variable z

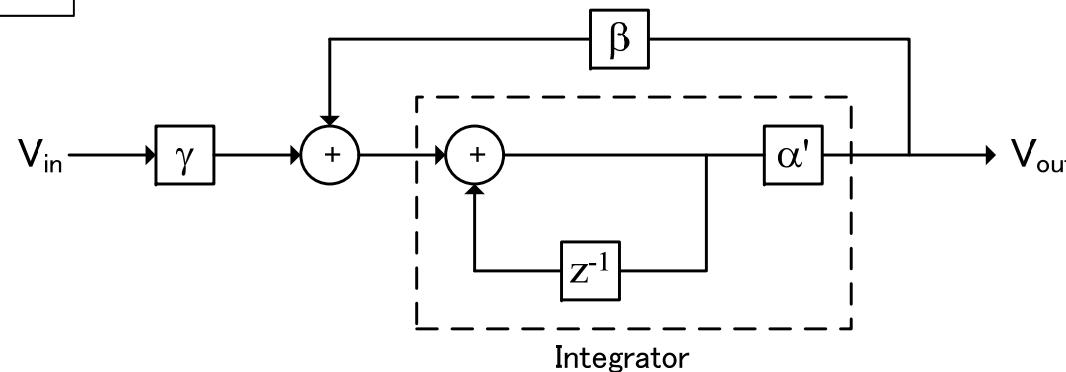Discrete-time analog circuits and digital circuits




## 2.3 Continuous-time analog implementation

# Implementation methods of analog circuits

Signal	Circuitry	Components	Features
Continuous time	RC	R, C, OPA	High precision, low power consumption
	gm-C	C, OTA	High speed, low power consumption
Discrete time	Switched capacitor	C, CMOS-switch, OPA	Very high precision
	Switched Current	Current mirror, CMOS-switch	Very high speed


# 2 types of OPA

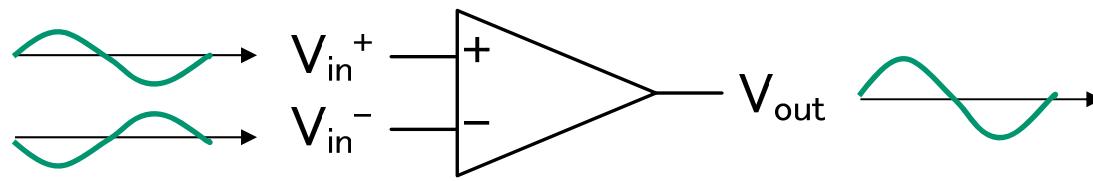

Function

$$\left\{ \begin{array}{l} V_{out} = A_d (V_{in}^+ - V_{in}^-) \\ A_d = \text{Differential Gain} \end{array} \right.$$

Symbol of Single-end OPA

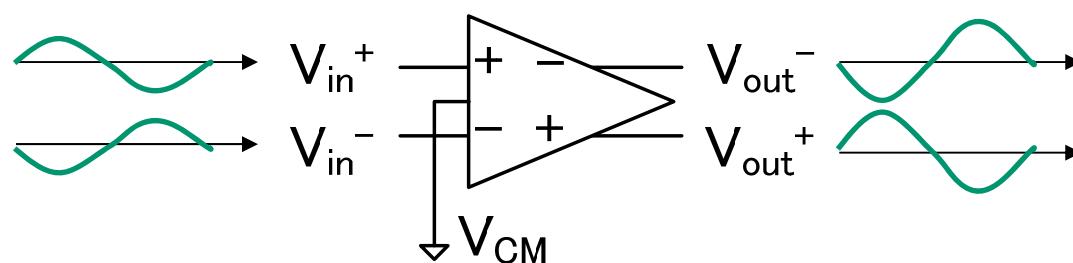


Symbol of Full-differential OPA

$$\left\{ \begin{array}{l} V_{out}^+ = \frac{A_d}{2} (V_{in}^+ - V_{in}^-) \\ V_{out}^- = -\frac{A_d}{2} (V_{in}^+ - V_{in}^-) \\ V_{out} = V_{out}^+ - V_{out}^- \end{array} \right.$$

$A_d$  = Differential Gain

# AC characteristic of OPA

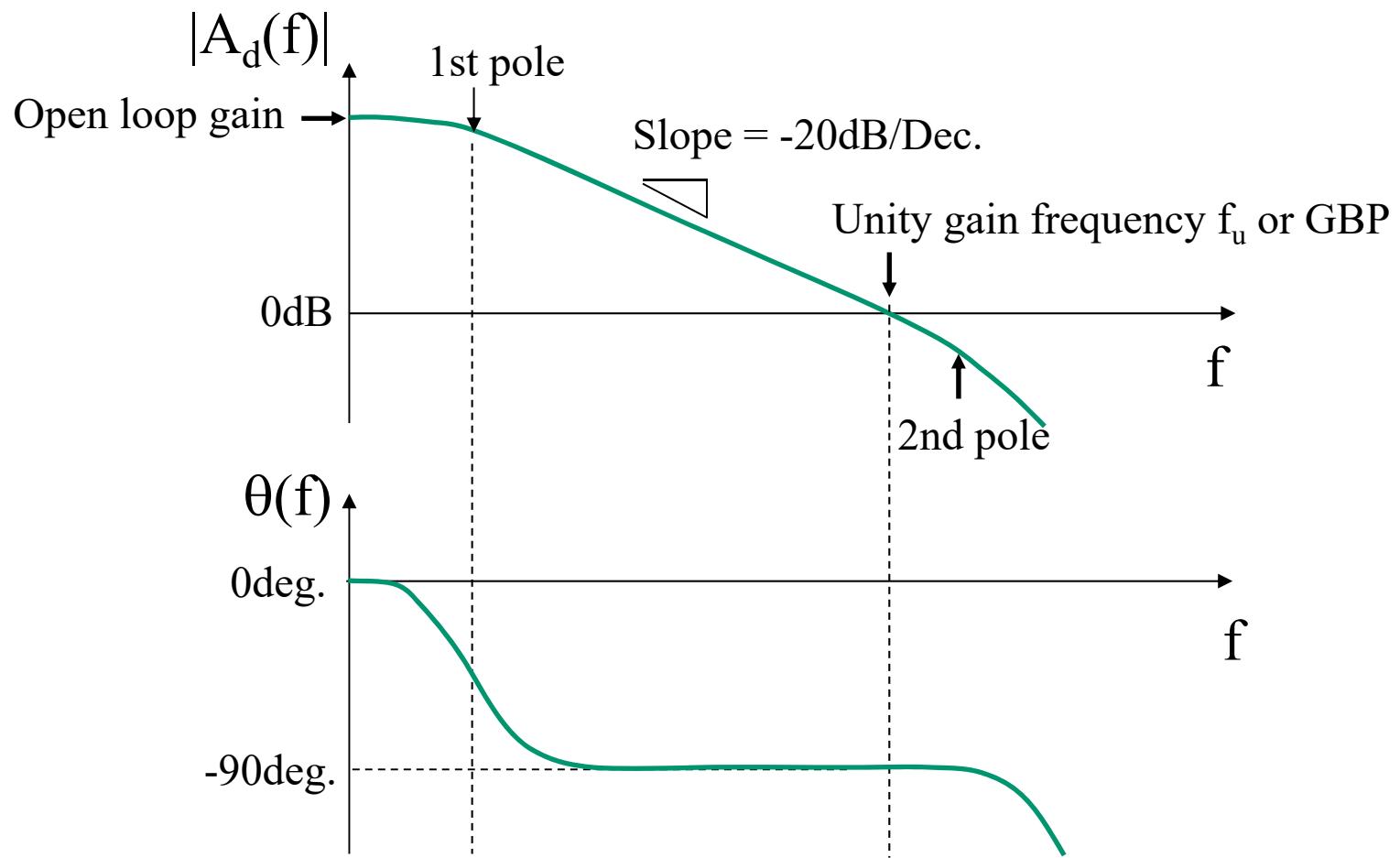




# Linear operators

Linear operation elements in the analog circuits



Operation	Symbol	(Typical implementation)
Addition and subtraction	$\text{In}_1 \xrightarrow[\pm]{} \oplus \xrightarrow[\pm]{} \text{In}_2 \rightarrow \text{Out}$	(Current summing)
Constant factor	$\text{In} \rightarrow \boxed{b} \rightarrow \text{Out}$	(Resistor)
Derivation	$\text{In} \rightarrow \boxed{cs} \rightarrow \text{Out}$	(Capacitor)
Integral	$\text{In} \rightarrow \boxed{a/s} \rightarrow \text{Out}$	(OPA or OTA)

a, b, c : circuit constants

# Continuous-time analog operators

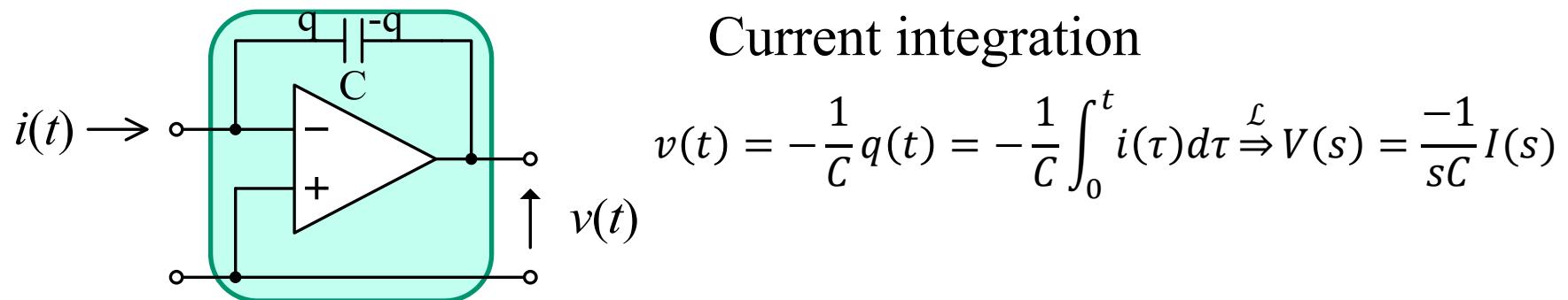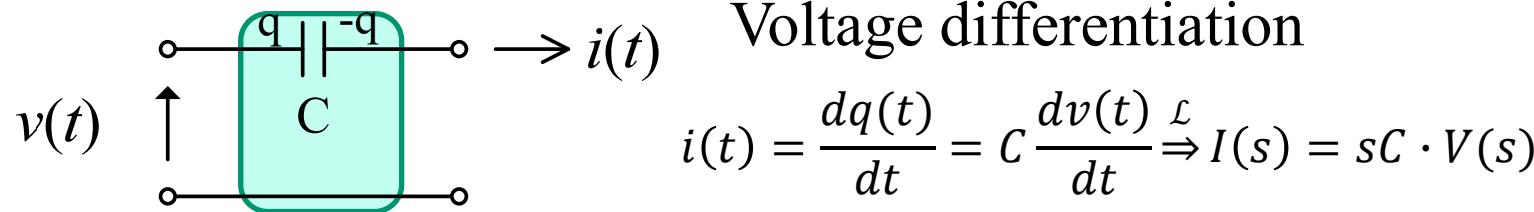
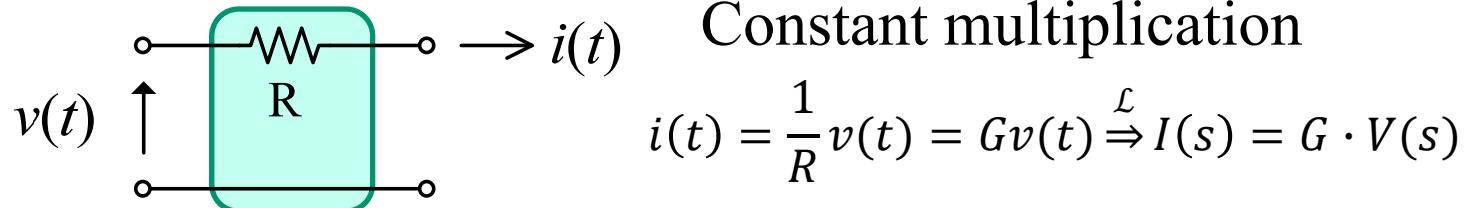

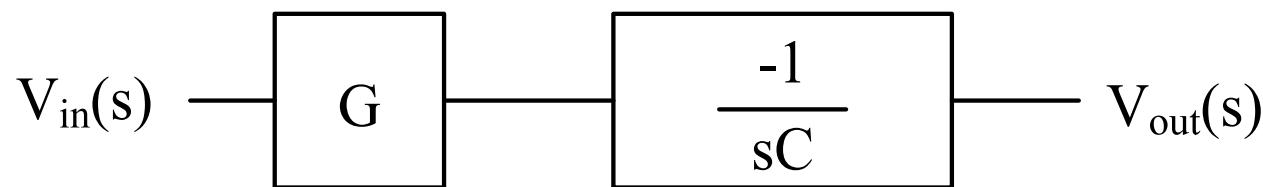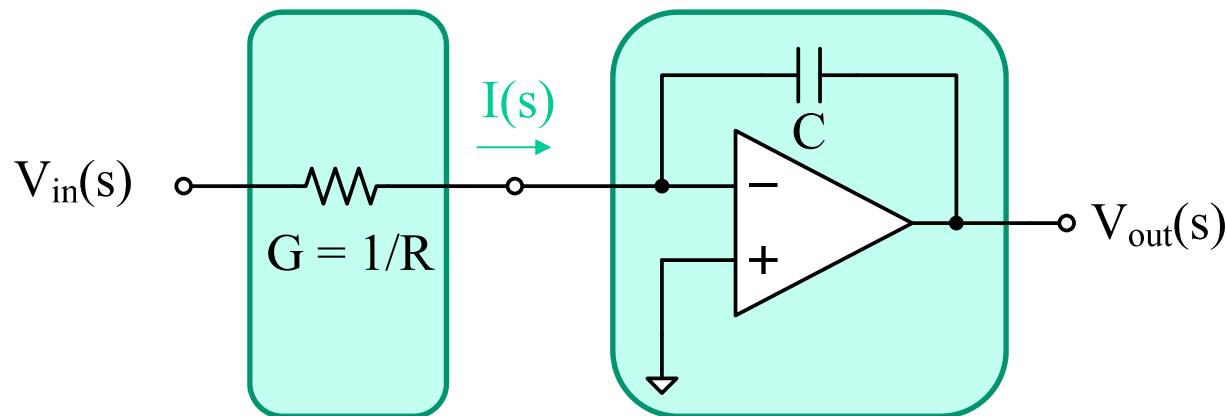
# Continuous-time analog integrator (CAI)



Transfer function of CAI:  $H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{-\frac{G}{sC}}{s} = \frac{G}{sC}$



# Implementation example 1

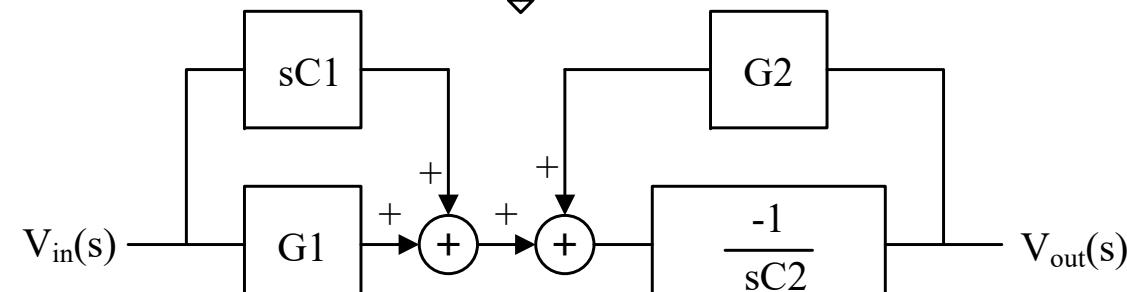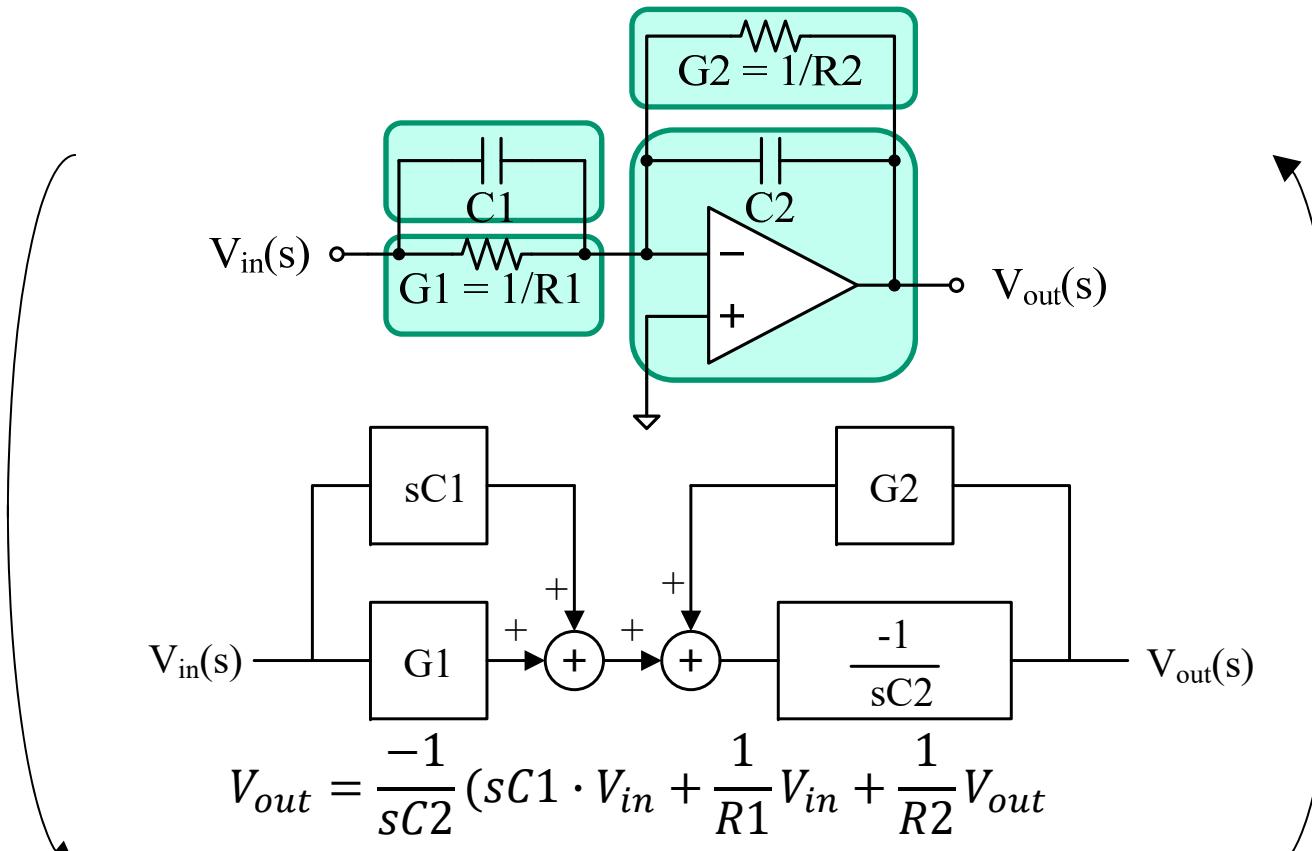

$$V_{out} = \frac{-1}{sC2} (sC1 \cdot V_{in} + \frac{1}{R1} V_{in} + \frac{1}{R2} V_{out})$$

$$H(s) = \frac{V_{out}}{V_{in}} = -\frac{C1 s + \frac{G1}{C1}}{\frac{G2}{C2} s + \frac{G2}{C2}} = a \frac{s + b}{s + c}$$


# Full-differential implementation

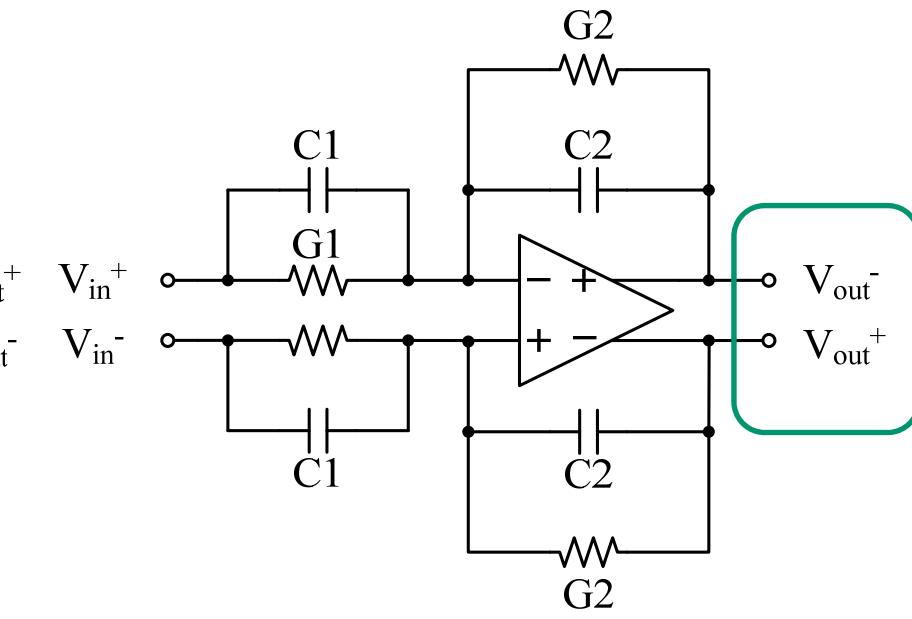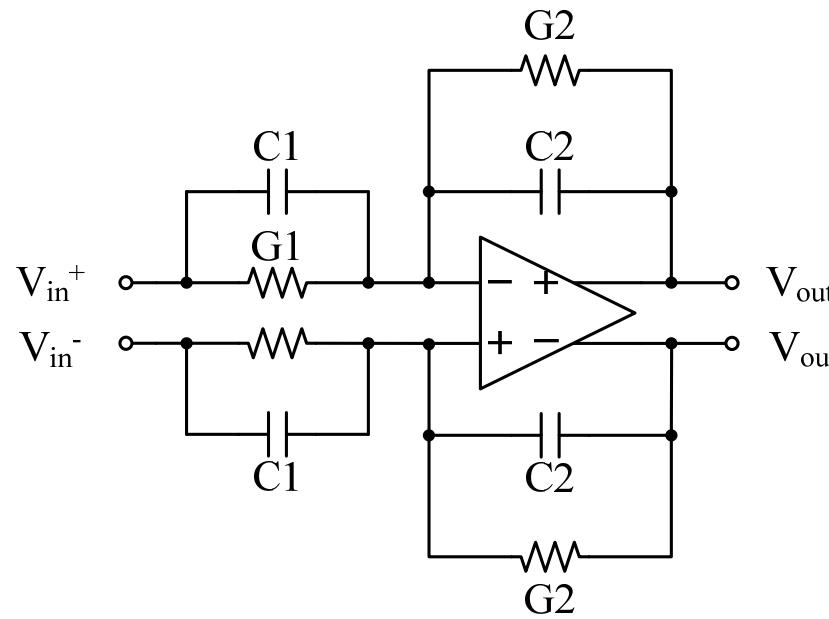

$$H(s) = \frac{V_{out}}{V_{in}} = -\frac{C_1 s + \frac{G_1}{C_1}}{C_2 s + \frac{G_2}{C_2}}$$

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{C_1 s + \frac{G_1}{C_1}}{C_2 s + \frac{G_2}{C_2}}$$

# Implementation example 2

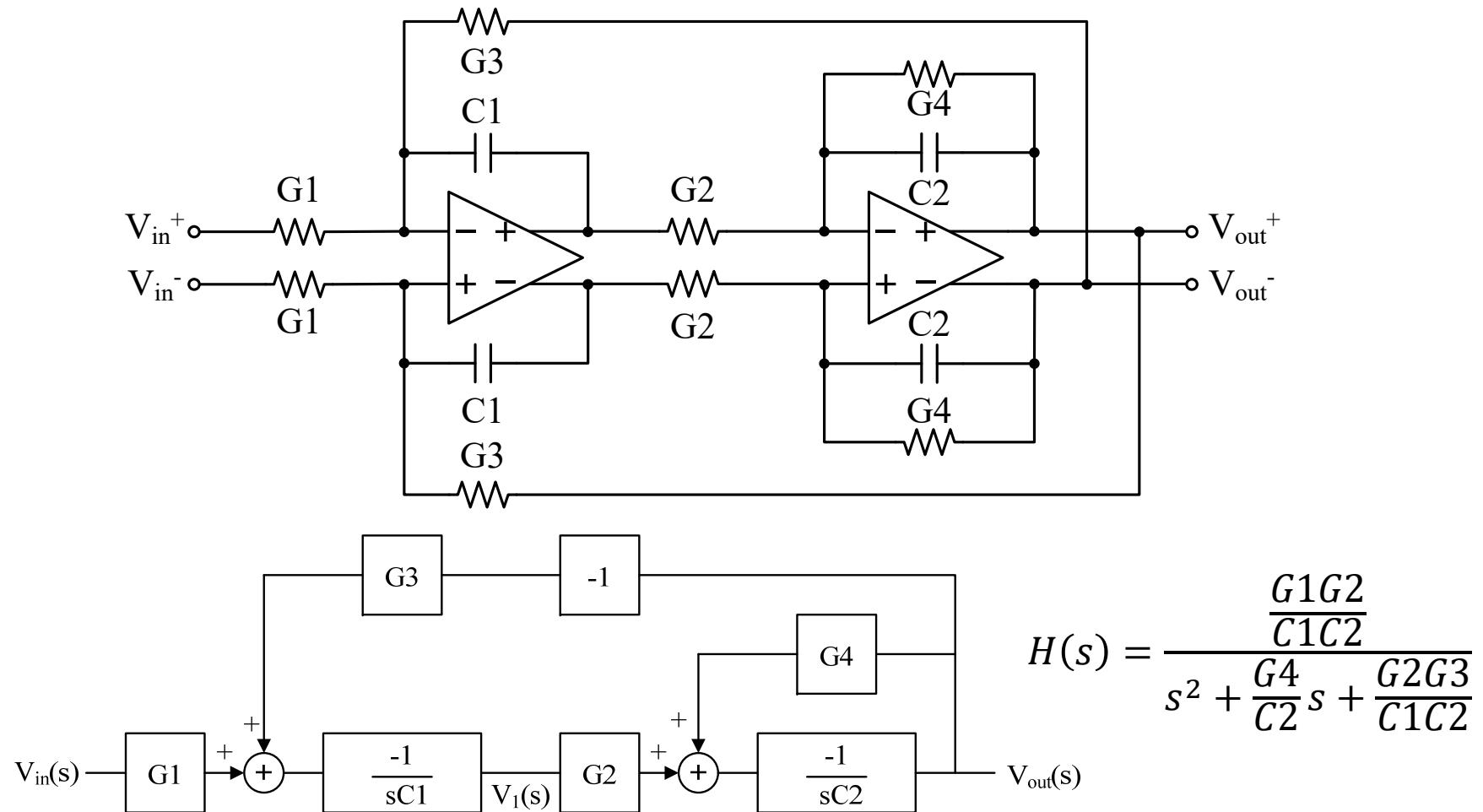


## 2.4 Discrete-time analog implementation
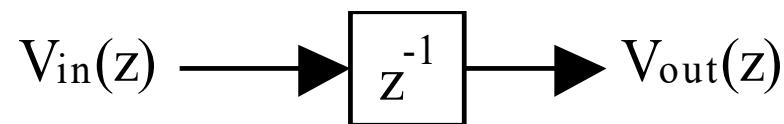
# Delay element


$$x_d(t - T_S) = x(t) \cdot \delta(t - T_S)$$

$$\begin{aligned} \int_0^\infty x_d(t - T_S) \cdot e^{-st} dt &= \int_0^\infty x(t) \cdot \delta(t - T_S) \cdot e^{-st} dt \\ &= x(T_S) e^{-sT_S} = x(T_S) \cdot z^{-1} \end{aligned}$$



$v(t) \rightarrow$  Time shift for 1-cycle  $\rightarrow v(t - T_S)$



# Discrete-time analog operators 1

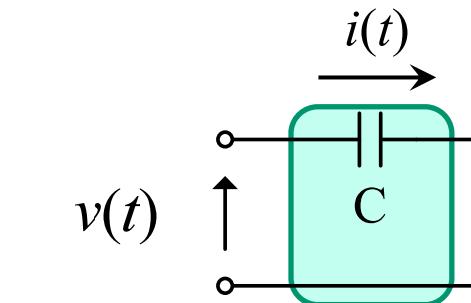

Voltage differentiation

$$I(s) = sC \cdot V(s) \xrightarrow{BET} I(z) = C(1 - z^{-1}) \frac{1}{T_S} V(z)$$


$$Q(z) = I(z)T_S = C(1 - z^{-1})$$

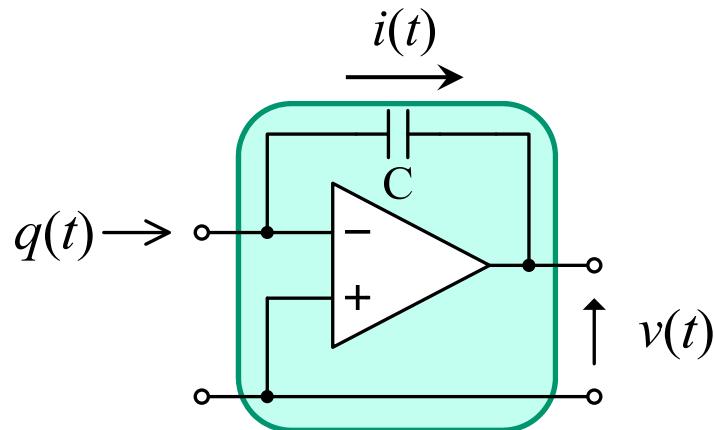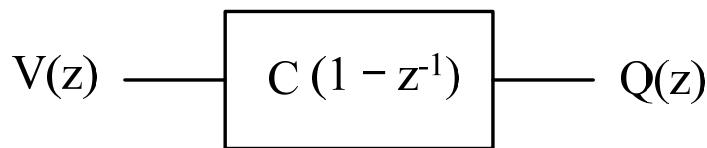

Charge integration


$$V(s) = \frac{-1}{sC} I(s) \xrightarrow{FET} V(z) = \frac{-1}{C} \frac{1}{1 - z^{-1}} I(z) T_S$$
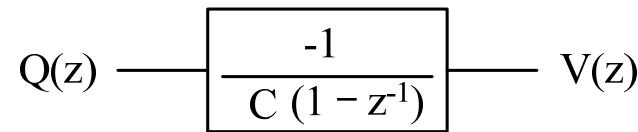
$$V(z) = \frac{-1}{C} \frac{1}{1 - z^{-1}} Q(z)$$



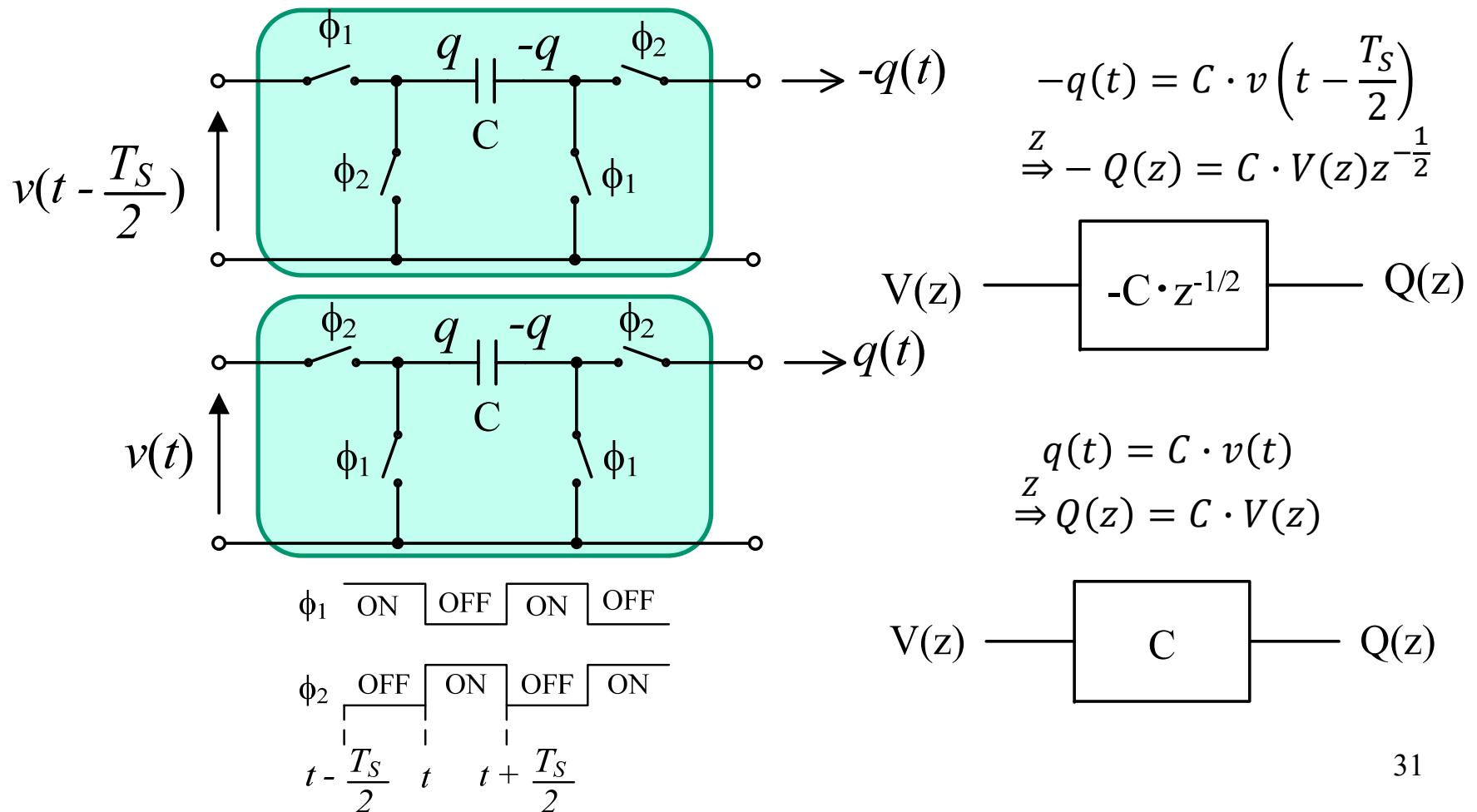
# Discrete-time analog operators 2

Constant multiplication (Switched capacitor)




# Non-overlapping clock generator

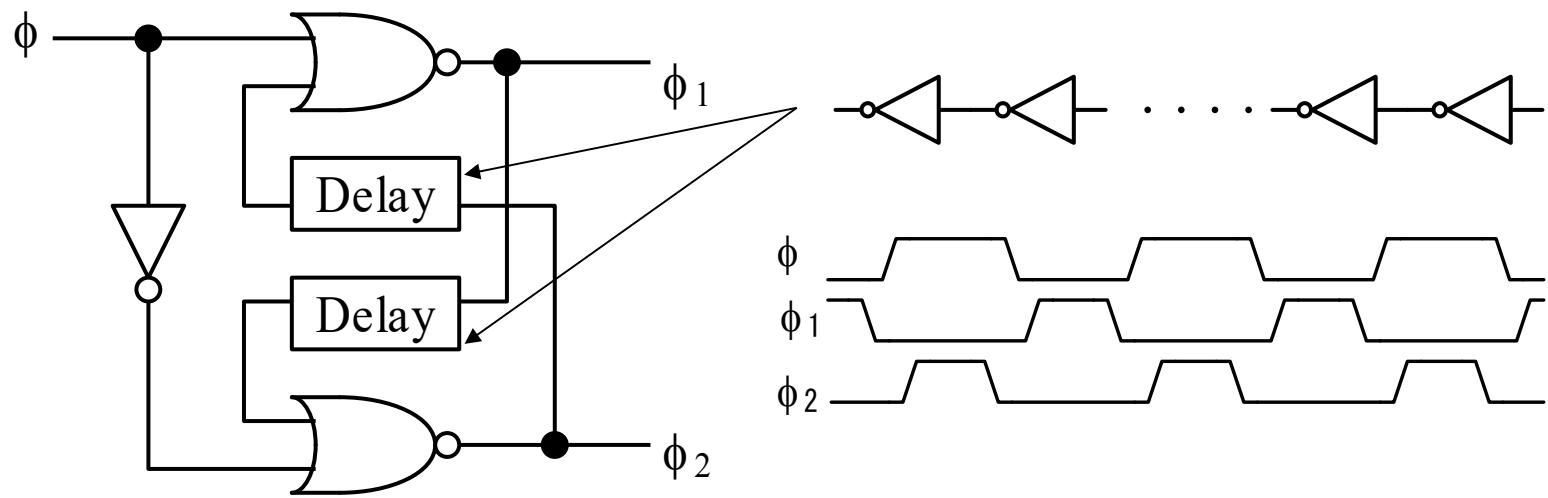

The two-phase clocks  $\phi_1$  and  $\phi_2$  are required to drive the switched capacitor. The edge of clocks  $\phi_1$  and  $\phi_2$  must not overlap, because the leak of the charge stored in capacitors causes the error of the signal processing.

# DAI: discrete-time analog integrator 1

## Positive phase integrator

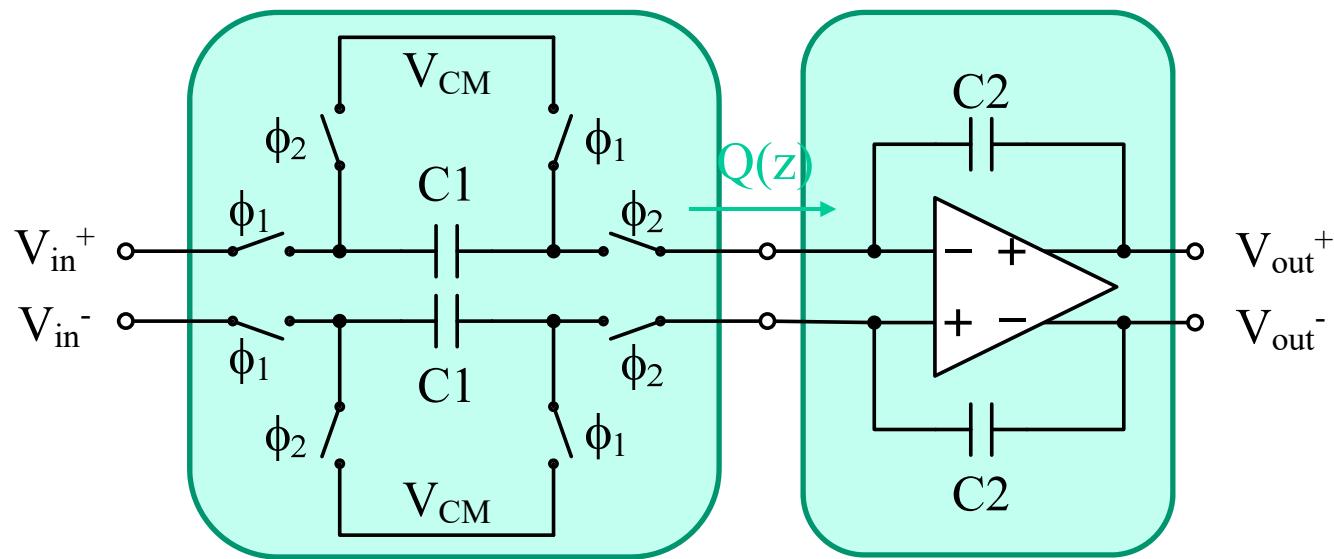


$$V_{in}(z) \rightarrow [-C_1 \cdot z^{-1/2}] \rightarrow \frac{-1}{C_2(1 - z^{-1})} \rightarrow V_{out}(z)$$

$$H(z) = \frac{C_1}{C_2} \frac{z^{-\frac{1}{2}}}{1 - z^{-1}}$$


# DAI: discrete-time analog integrator 2

Opposite phase integrator

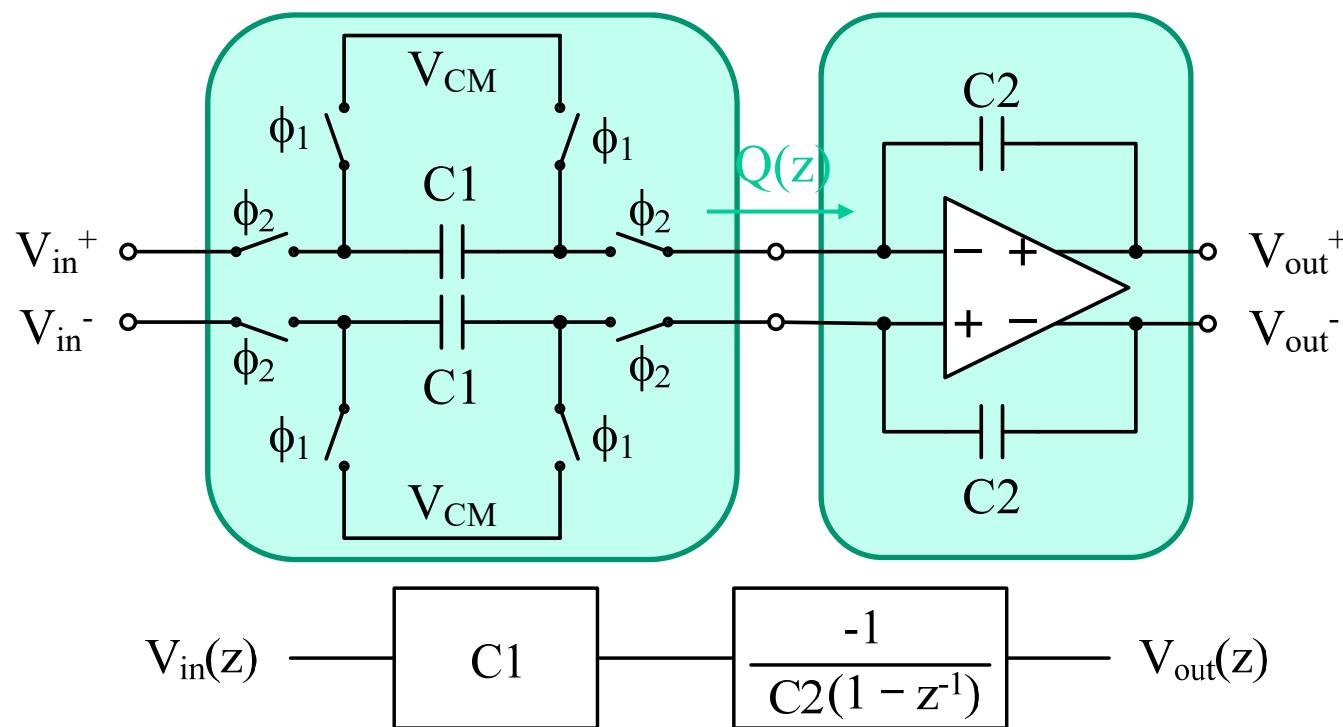

$$H(z) = -\frac{C_1}{C_2} \frac{1}{1 - z^{-1}}$$


# Implementation example

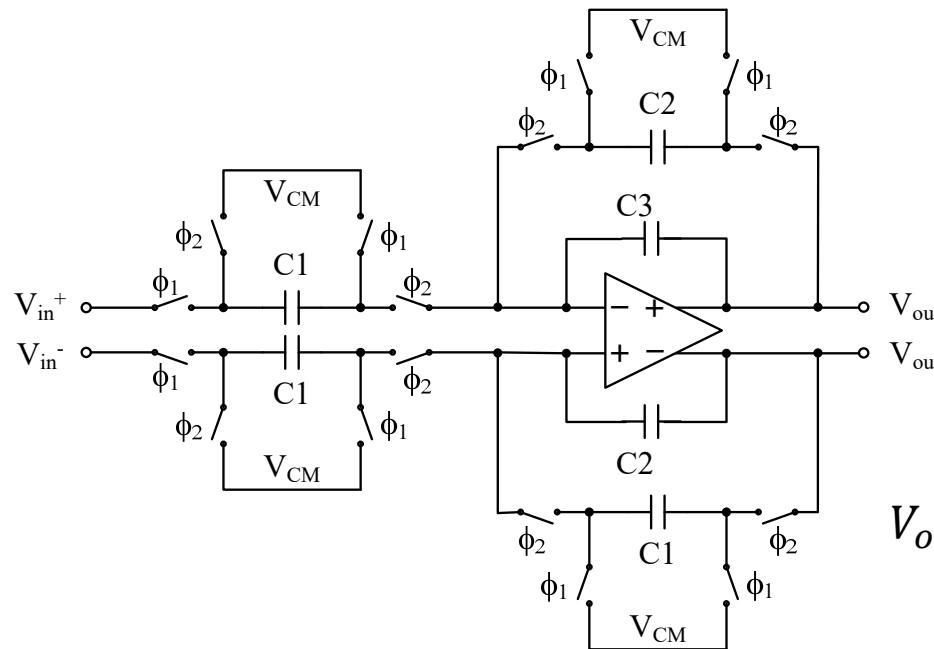


$$V_{out} = -\frac{1}{C3} \frac{1}{1 - z^{-1}} (-C1z^{-\frac{1}{2}}V_{in} + C2 \cdot V_{out})$$

$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = -\frac{C1}{C2 + C3} \frac{z^{-\frac{1}{2}}}{z - \frac{C3}{C2 + C3}}$$

(LPF)

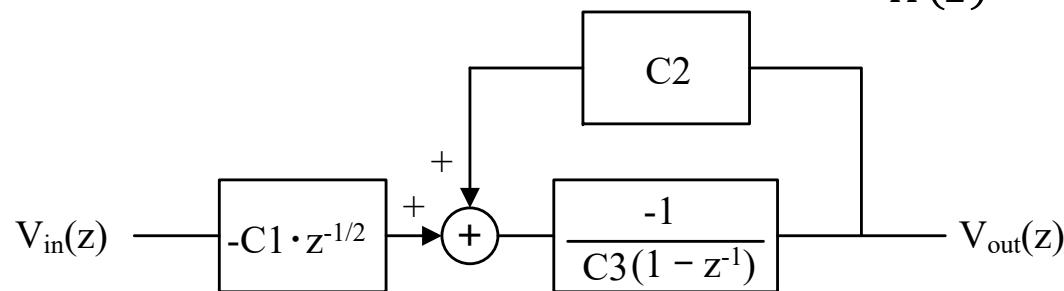


# Poles in s-plane and z-plane

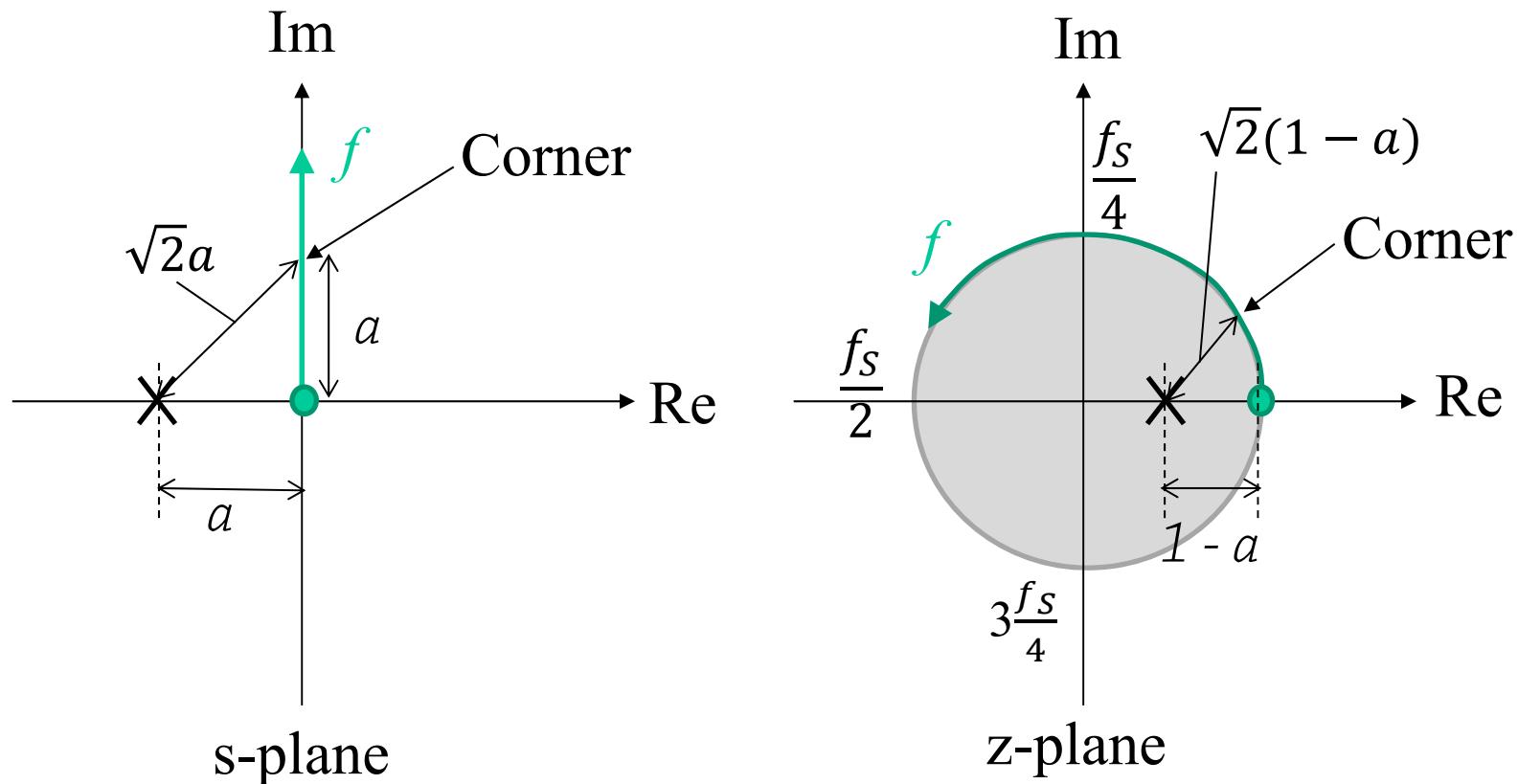

## 2.5 Digital implementation


# Digital operators 1

Delay

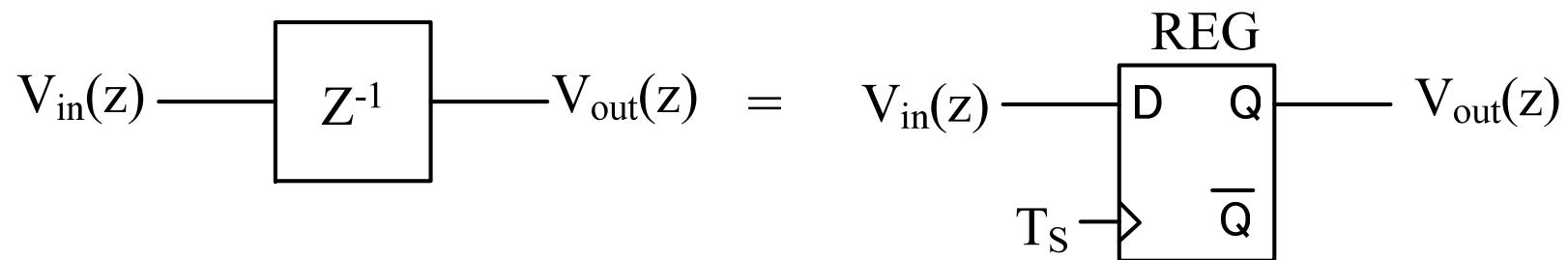


Differentiation (BET)

$$V_{out}(z) = (1 - z^{-1})V_{in}(z)$$

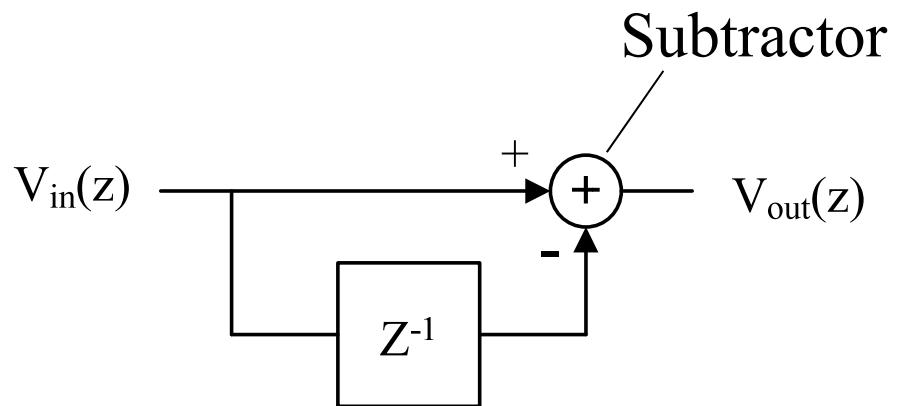


# Digital operators 2

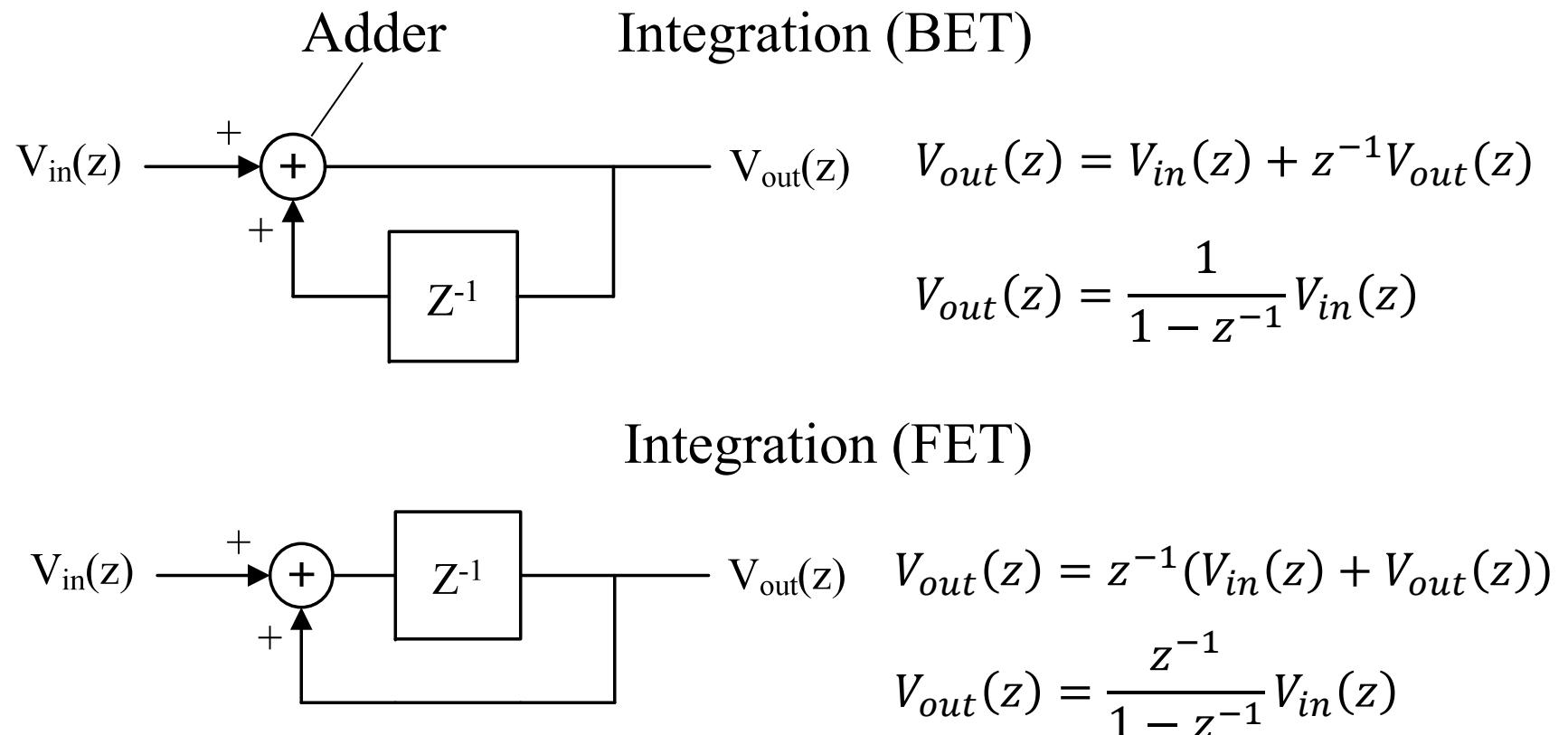

NOTE: The FET integrator does not output the hazards, because the digital delay element is the same as an register.

# Implementation example

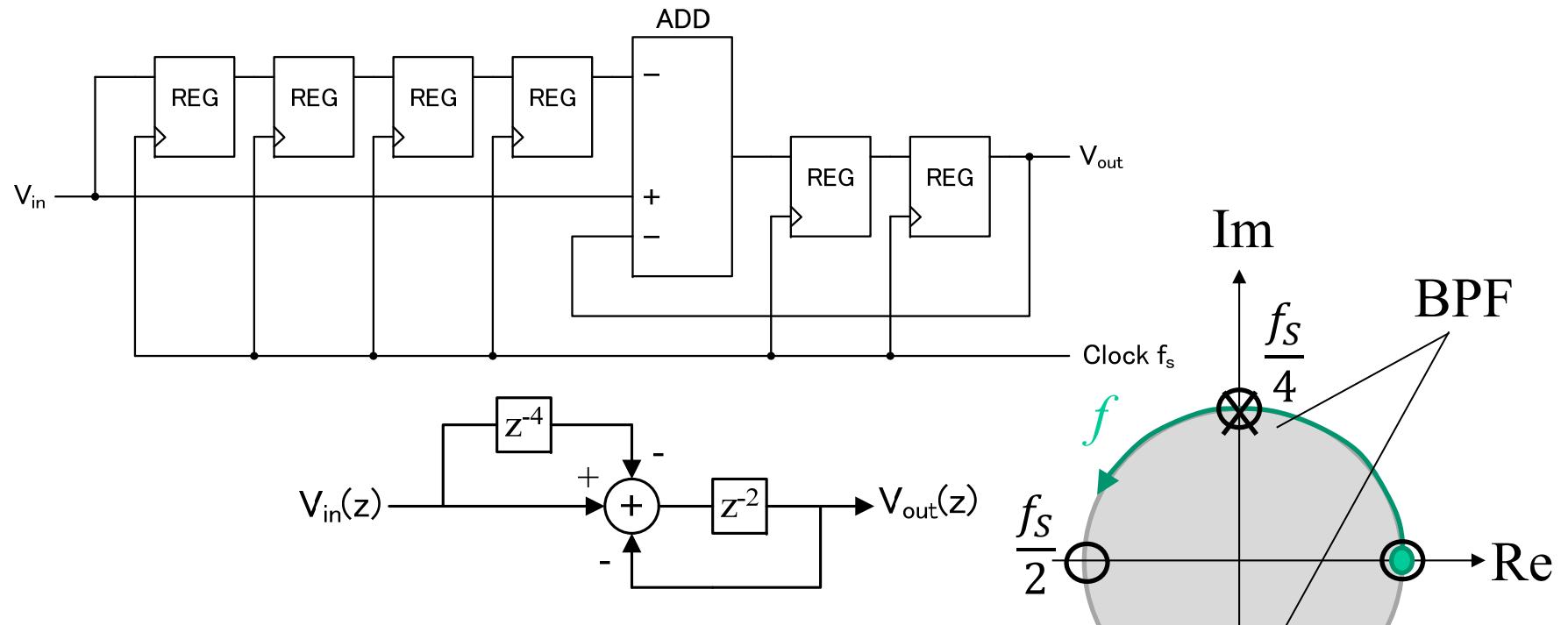

$$V_{out}(z) = z^{-2}(1 - z^{-4})V_{in}(z) - z^{-2}V_{out}(z)$$

$$= \frac{z^{-2}(1 - z^{-4})}{1 + z^{-2}} V_{in}(z)$$

Comb filter      Resonator