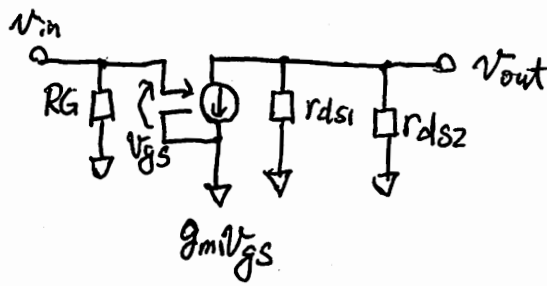


Q1

(1)



(2)

$$G = \frac{V_{out}}{V_{in}} = -g_{m1} (r_{ds1} \parallel r_{ds2})$$

$$I_{D1} = \frac{\beta_n}{2} V_{ov}^2 = \frac{1\text{m}}{2} 0.2^2 = 20.0 \mu\text{A}$$

$$g_{m1} = \sqrt{2\beta_n I_{D1}} = \sqrt{2 \cdot 1\text{m} \cdot 20\mu} = 0.200\text{mS}$$

$$G = -0.200\text{mS} \frac{5\text{M}\Omega}{2} = -500 \frac{\text{V}}{\text{V}}$$


$$G(\text{dB}) = 20 \log |G| = 54.0\text{dB}$$

(3) $Z_{in} = R_G = 5.00\text{M}\Omega$

$$Z_{out} = r_{ds1} \parallel r_{ds2} = \frac{5.00\text{M}}{2} = 2.50\text{M}\Omega$$

Q2

(1)

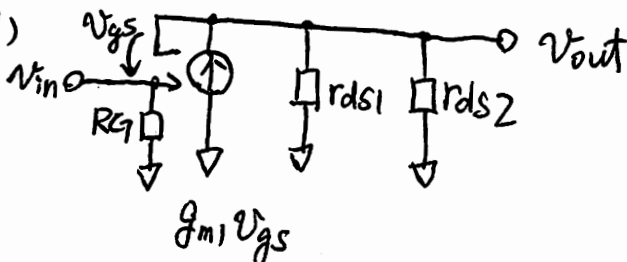

(2)

$$I_{D1} = +\frac{\beta_n}{2} V_{ov}^2 = +20.0 \mu\text{A} \quad (I_{D1} \text{ は正})$$

$$g_{m1} = \sqrt{2\beta_n I_{D1}} = 0.200\text{mS}$$

$$r_{ds1} = r_{ds2} = \frac{1}{\lambda_n \beta_n I_{D1}} = 5.00\text{M}\Omega$$

$$G = \frac{V_{out}}{V_{in}} = \frac{\lambda_n g_{m1} (r_{ds1} \parallel r_{ds2})}{1 + g_{m1} (r_{ds1} \parallel r_{ds2})} = \frac{0.2\text{m} \frac{5\text{M}}{2}}{1 + 0.2\text{m} \frac{5\text{M}}{2}} = \frac{500}{501} = 0.998 \frac{\text{V}}{\text{V}}$$

$$G(\text{dB}) = 20 \log 0.998 = -0.0174\text{dB}$$


(3)

$$Z_{in} = R_G = 5.00\text{M}\Omega$$

$$Z_{out} = \left. \frac{V_{out}}{i_{out}} \right|_{V_{in}=0} = \frac{r_{ds1} \parallel r_{ds2}}{1 + g_{m1} (r_{ds1} \parallel r_{ds2})} = \frac{\frac{5\text{M}}{2}}{1 + 0.2\text{m} \frac{5\text{M}}{2}} = 4.99\text{k}\Omega$$

Q3

(1)

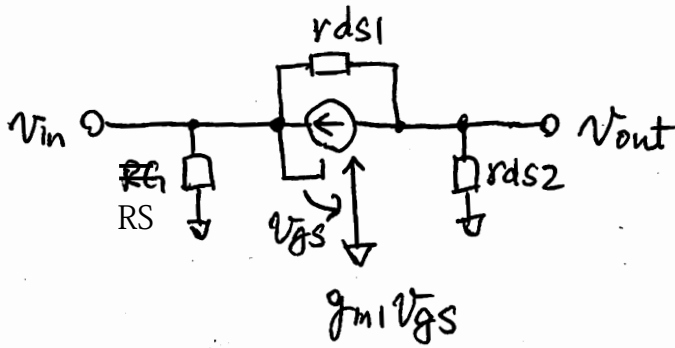

(2)

$$G = \frac{V_{out}}{V_{in}} = \frac{1 + g_m r_{ds1}}{1 + \frac{r_{ds1}}{r_{ds2}}} = \frac{1 + 0.2 \text{ mS} \cdot 5 \text{ M}\Omega}{1 + 1} = 50 \text{ } \left| \frac{\text{V}}{\text{V}} \right|$$

$$\begin{cases} I_{D1} = \frac{\beta_n}{2} V_{ov}^2 = 20.0 \text{ mA} \\ g_{m1} = \sqrt{2\beta_n I_{D1}} = 0.200 \text{ mS} \\ r_{ds1} = r_{ds2} = \frac{1}{\lambda_n I_{D1}} = 5.00 \text{ M}\Omega \end{cases}$$

$$G(\text{dB}) = 20 \cdot \log 50 = 54.0 \text{ dB}$$

(3)

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{r_{ds1} + r_{ds2}}{1 + g_m r_{ds1} + \frac{r_{ds1} + r_{ds2}}{R_S}}$$

$$= \frac{2.5 \text{ M}\Omega}{1 + 0.2 \text{ mS} \cdot 5 \text{ M}\Omega + \frac{2.5 \text{ M}\Omega}{50 \text{ k}\Omega}} = \frac{2.5 \text{ M}\Omega}{8.33} = 300 \text{ k}\Omega$$

$$Z_{out} = \frac{V_{out}}{i_{out}} \Big|_{V_{in}=0} = r_{ds1} \parallel r_{ds2} = 2.50 \text{ M}\Omega$$

(注) ここでは、信号源の内部抵抗 $r_s = 0$ のため、 $R_S \parallel r_s = 0$ として Z_{out} を求めている。実際には、 $r_s \neq 0$ のため、 Z_{out} は非常に大きい値となることが多い。

Q4

1) M1: $V_{ov1} = V_{bias1} - V_{Tn}$

M2: $V_{ov2} = V_{bias2} - VDD - V_{Tp}$

$V_{bias1} = VDD - V_{bias2}$, $V_{Tn} = -V_{Tp}$ より

$V_{ov1} = -V_{ov2}$ → n-ch a M1 と p-ch a M2 の π -r.t. の電圧が等しいから

$V_{Ds1} = \frac{VDD}{2}$ ↑の大きさ

$I_{D3} = |I_{D4}| = 64|I_{D2}| = 64I_{D1}$

$V_{ov3} = \sqrt{\frac{2I_{D3}}{64\beta_n}} = \sqrt{\frac{2 \cdot 64I_{D1}}{64\beta_n}} = \sqrt{\frac{2I_{D1}}{\beta_n}} = V_{ov1}$


$V_{GS3} - V_{Tn} = V_{GS1} - V_{Tn}$ より

$V_{GS3} = V_{GS1} = V_{bias1}$

$V_{DS3} = V_{DS1} + V_{GS3} = \frac{VDD}{2} + V_{bias1}$

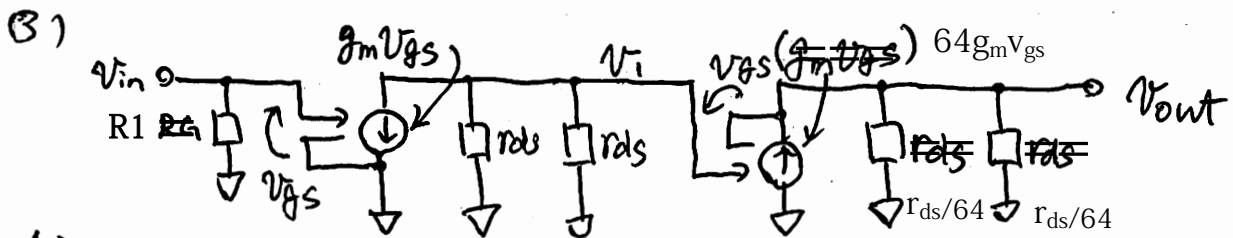2) $g_{m3} = \sqrt{2 \cdot 64\beta_n I_{D3}} = \sqrt{2 \cdot 64\beta_n I_{D1} \cdot 64} = 64g_m = 25.6 \text{ mS}$

$g_{ds3} = \lambda_n I_{D3} = 64\lambda_n I_{D1} = 64g_{ds} = \frac{64}{5 \text{ M}} = 12.8 \mu\text{S}$



4) $G = \frac{V_{out}}{V_{in}} = - \frac{\frac{1}{4} g_m^2 r_{ds}^2}{1 + \frac{1}{2} g_m r_{ds}} = -999 \frac{\mu\Omega}{\Omega}$


5) $Z_{in} = R1 = 10.0 \text{ M}\Omega$

$Z_{out} = \frac{V_{out}}{I_{out}} \Big|_{V_{in}=0} = \frac{\frac{r_{ds} (1/64)}{2}}{1 + \frac{r_{ds} g_m}{2}} = 39.1 \mu\Omega$

(注) $V_{in} = 0$ のとき $V_i = 0$, (3)参照

Q5

(1)

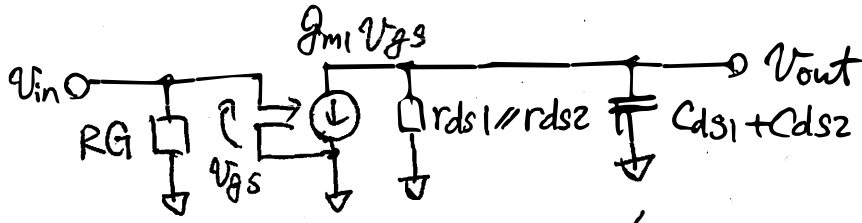

$$Y = \frac{1}{r_{ds1}} + \frac{1}{r_{ds2}} + j\omega(C_{ds1} + C_{ds2})$$

(2)

$$G(\omega) = - \frac{g_{m1} (r_{ds1} \parallel r_{ds2})}{1 + j\omega (C_{ds1} + C_{ds2}) (r_{ds1} \parallel r_{ds2})} \quad \#$$

(3)

$$\omega_p = \frac{1}{(C_{ds1} + C_{ds2}) (r_{ds1} \parallel r_{ds2})} = \frac{1}{20 \text{ pF} \cdot \frac{5 \text{ M}\Omega}{2}} = 20.0 \text{ Mrad/s}$$

$$(4) \quad G(\omega \ll \omega_p) = -g_{m1} (r_{ds1} \parallel r_{ds2}) = -0.4 \text{ mS} \cdot \frac{5 \text{ M}\Omega}{2} = -1000 \frac{\text{V}}{\text{V}}$$

$$|G(\omega)| (\text{dB}) = 20 \log 1000 = 60.0 \text{ dB}$$


$$\text{負の乗数} \rightarrow \angle G(\omega) = 180^\circ \quad (\text{フェーズ} -180^\circ)$$

(5) $\omega = \omega_p$ at \angle



$$G(\omega_p) = - \frac{g_{m1} (r_{ds1} \parallel r_{ds2})}{1 + j} = - \frac{g_{m1} (r_{ds1} \parallel r_{ds2})}{\sqrt{2}} (1 - j)$$

$$|G(\omega_p)| = \frac{1000}{\sqrt{2}} \quad \# \quad 20 \log(1000/\sqrt{2}) = 60 \text{ dB} - 3.01 \text{ dB} = 57.0 \text{ dB}$$
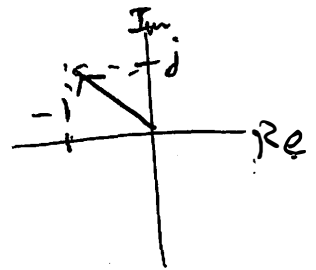
$$\angle G(\omega_p) = 135^\circ \quad (\text{フェーズ} -225^\circ)$$



(6)

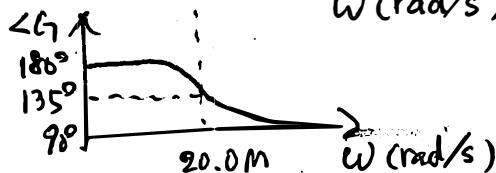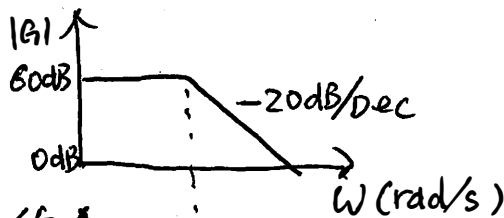

(7) $\omega_p = 20.0 \text{ Mrad/s}$

$$f_p = \frac{1}{2\pi} \cdot \omega_p = 3.18 \text{ MHz}$$

$$|G(\omega=0)| = 60.0 \text{ dB} = 1000 \frac{\text{V}}{\text{V}}$$

$$\text{GB積} = |G(\omega=0)| \cdot f_p = 1000 \cdot 3.18 \text{ MHz} = 3.18 \text{ GHz}$$


Q6

$$a) H(j\omega) = \frac{-A}{1 + j\omega CR(1+A)}$$

$$b) \bar{Z}_{in} = \frac{V_{in}}{i} = R + \frac{1}{j\omega C(1+A)}$$

$$c) \omega_p CR(1+A) = 1 \text{ 即}$$

$$\omega_p = \frac{1}{CR(1+A)}$$

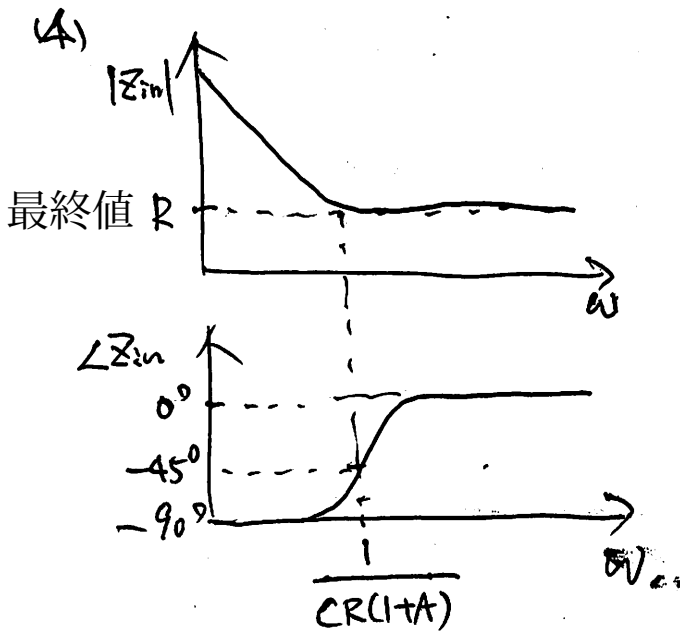

Q7.

$$(1) A(\omega) = \frac{-A_0}{1 + j\omega B}$$

$$|A(\omega)| = \frac{A_0}{\sqrt{1 + \omega^2 B^2}}$$

$$|A(\omega_u)| = \frac{A_0}{\sqrt{1 + \omega_u^2 B^2}} = 1$$

$$\omega_u = \frac{\sqrt{A_0^2 - 1}}{B}$$

$$f_u = \frac{\omega_u}{2\pi} = \frac{\sqrt{A_0^2 - 1}}{2\pi B}$$

$$(2) \omega_p = \frac{1}{B}$$

$$GB \text{ 積} = A_0 \cdot \frac{\omega_p}{2\pi} = \frac{A_0}{2\pi B}$$

$$(3) \omega = 0 \text{ rad/s} \quad G(\omega) = -A_0, \quad \angle G(\omega) = 180^\circ$$

$$\omega = \frac{1}{B} \text{ rad/s} \quad G(\omega) = \frac{-A_0}{1 + j} = \frac{A_0}{\sqrt{2}} (-1 + j), \quad \angle G(\omega) = 135^\circ$$

$$\omega \gg \frac{1}{B} \text{ rad/s} \quad G(\omega) \doteq \frac{-A_0}{j\omega B} = j \frac{A_0}{\omega B}, \quad \angle G(\omega) = 90^\circ$$

$$(4) G(\omega) = \frac{-A_0 \frac{R_2}{R_1 + R_2 + A_0 R_1}}{1 + j\omega B \frac{R_1 + R_2}{R_1 + R_2 + A_0 R_1}}$$

$$(5) \omega_p = \frac{A_0 + 1 + \frac{R_2}{R_1}}{B \left(1 + \frac{R_2}{R_1}\right)}$$

$$(6) GBP = \frac{1}{2\pi B} \frac{R_2 A_0}{R_1 + R_2} = \frac{1}{2\pi B} \frac{A_0}{\left(1 + \frac{R_1}{R_2}\right)}$$

Q8

$$(1) NF = SNR_{in} - SNR_{out} = 50 \text{ dB} - 46.5 \text{ dB} = 3.5 \text{ dB}$$

$$(2) S_2 = S_1 + G_p = 0 \text{ dBm}$$

$$N_2 = N_1 + G_p + NF = -126.5 \text{ dBm}$$

$$(3) \lambda \text{ の SNR} = \frac{S_1}{N_1} \text{ (dB)} = -20 \text{ dBm} - (-150 \text{ dBm}) = +130 \text{ dB}$$

$$\text{出力 SNR} = \frac{S_2}{N_2} \text{ (dB)} = 0 \text{ dBm} - (-126.5 \text{ dBm}) = 126.5 \text{ dB}$$

Q9

$$(1) V_{out} = \frac{H}{1-H} V_{in} + \frac{1}{1-H} V_d$$

$$(2) V_{out} = \frac{-A_0}{A_0 + j\omega C} V_{in} + \frac{j\omega C}{A_0 + j\omega C} V_d$$

$$(3) \text{ ~~(A)~~ } V_{out} = -V_{in} \text{ の Gain} = -1$$

(5) ~~(A)~~ (C), 理由: $1 - \frac{A_0}{A_0 + j\omega C} = H(j\omega) = j \frac{A_0}{\omega C}$ の
 ω が増える位相 = 90° とおける。
 正帰還, 負帰還の区別は不明。

$$(4) \text{ ~~(B)~~ } \text{ 信号伝達関数} = \frac{-A_0}{A_0 + j\omega C} = -1$$

$$\text{誤差伝達関数} = \frac{j\omega C}{A_0 + j\omega C} = 0$$

Q10

$$(1) G_i = -\frac{R_2}{R_1}$$

$$(2) G_r = -\frac{R_2}{R_1} \frac{1}{\left(1 + \frac{R_2}{R_1}\right) \frac{1}{A_d} + 1}$$

$$(3) R_{err} = \frac{-\frac{R_2}{R_1} \frac{A_d}{1 + A_d + R_2/R_1} + \frac{R_2}{R_1}}{-\frac{R_2}{R_1}} = \frac{1}{\left(1 + \frac{R_2}{R_1}\right) \frac{1}{A_d} + 1} - 1$$


$$(4) R_{err} = \frac{1}{\frac{2}{A_d} + 1} - 1 = -\frac{1}{1000}$$

$$A_d = 1998 \frac{1}{2}$$

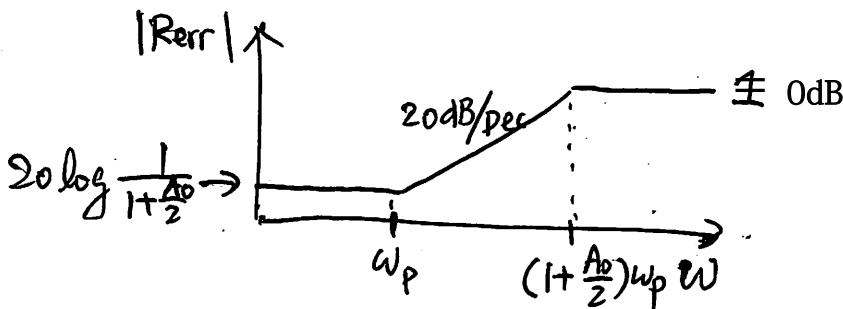(5)


$$R_{err} = \frac{1}{\frac{2}{A_d} + 1} - 1 = \frac{-2}{2 + A_d} = \frac{-2}{2 + \frac{A_0}{1 + j\omega/\omega_p}}$$

$$= \frac{-\frac{1}{1 + \frac{A_0}{2}} (1 + j\omega/\omega_p)}{1 + j\omega/\omega_p (1 + \frac{A_0}{2})}$$



Q11

(1)

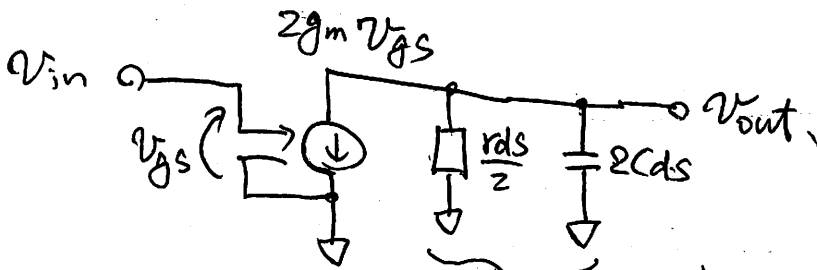



(2)

$$Z = \left(\frac{2}{r_{ds}} + j\omega 2C_{ds} \right)^{-1}$$

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{-2g_m}{\frac{2}{r_{ds}} + j\omega 2C_{ds}} = - \frac{g_m r_{ds}}{1 + j\omega(C_{ds} r_{ds})}$$

\uparrow -180° \uparrow -60°

(3)

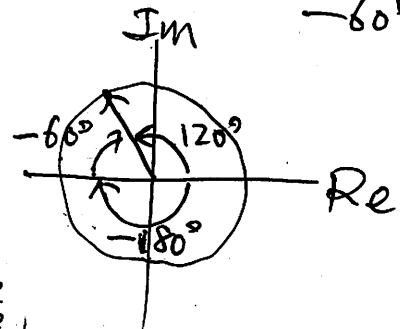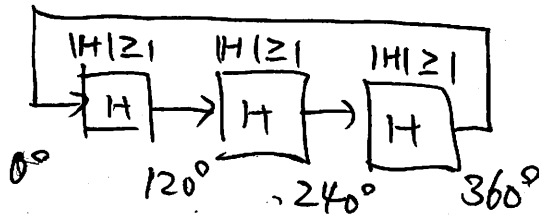

1段当り 120° の位相遅延

$$\omega_{osc} C_{ds} r_{ds} = \sqrt{3}$$

位相条件: $\omega_{osc} = \frac{\sqrt{3}}{C_{ds} r_{ds}}$

このとき $H(\omega_{osc}) = - \frac{g_m r_{ds}}{1 + j\sqrt{3}}$

$$|H(\omega_{osc})| = \frac{g_m r_{ds}}{\sqrt{1+3}} \geq 1$$

振幅条件: $g_m r_{ds} \geq 2$

Q12

$$(1) G_{loop} = -\frac{G}{A_3} = -\frac{G}{(1 - 5\omega^2 C^2 R^2) + j\omega CR(6 - \omega^2 C^2 R^2)}$$

↑
FISX-G

$$(2) \angle G_{loop} = \tan^{-1} \frac{\omega CR(6 - \omega^2 C^2 R^2)}{1 - 5\omega^2 C^2 R^2} = 0$$

零点

$$\omega_{osc} = \frac{\sqrt{6}}{CR} \quad (\text{位相条件})$$

$$G_{loop}(\omega_{osc}) = -\frac{G}{1 - 5\frac{6}{C^2 R^2} C^2 R^2} \geq 1$$

$$G \geq 4 \quad (\text{振幅条件})$$

29

- (B) RC-LPF 2段 \Rightarrow 発振不可
 RC-LPF 4段 \Rightarrow 発振可能
 理由は、口頭で説明済み

Q13

$$\Delta V = \frac{\Delta Q}{C} = \frac{I_L \frac{1}{2}}{C} = \frac{I_L}{C} \frac{1}{2f}$$

$$\gamma = \frac{\Delta V}{V_{DC}} = \frac{I_L}{2CfV_{DC}} = \frac{100\text{mA}}{C \cdot 2 \cdot 60\text{Hz} \cdot 6.20\text{V}} \leq 0.05$$

$$C \geq \frac{100\text{m}}{2 \cdot 60 \cdot 6.20 \cdot 0.05} = 2.69\text{mF}$$