

2.2 CMOS static logic gates

The design of primitive logic gates


CMOS

CMOS = Complementary MOS

This term has two meanings.

- The process technology to integrate p-ch MOSFETs and n-ch MOSFETs
- The circuit structure with p-ch MOSFETs and n-ch MOSFETs

MOSFET switch

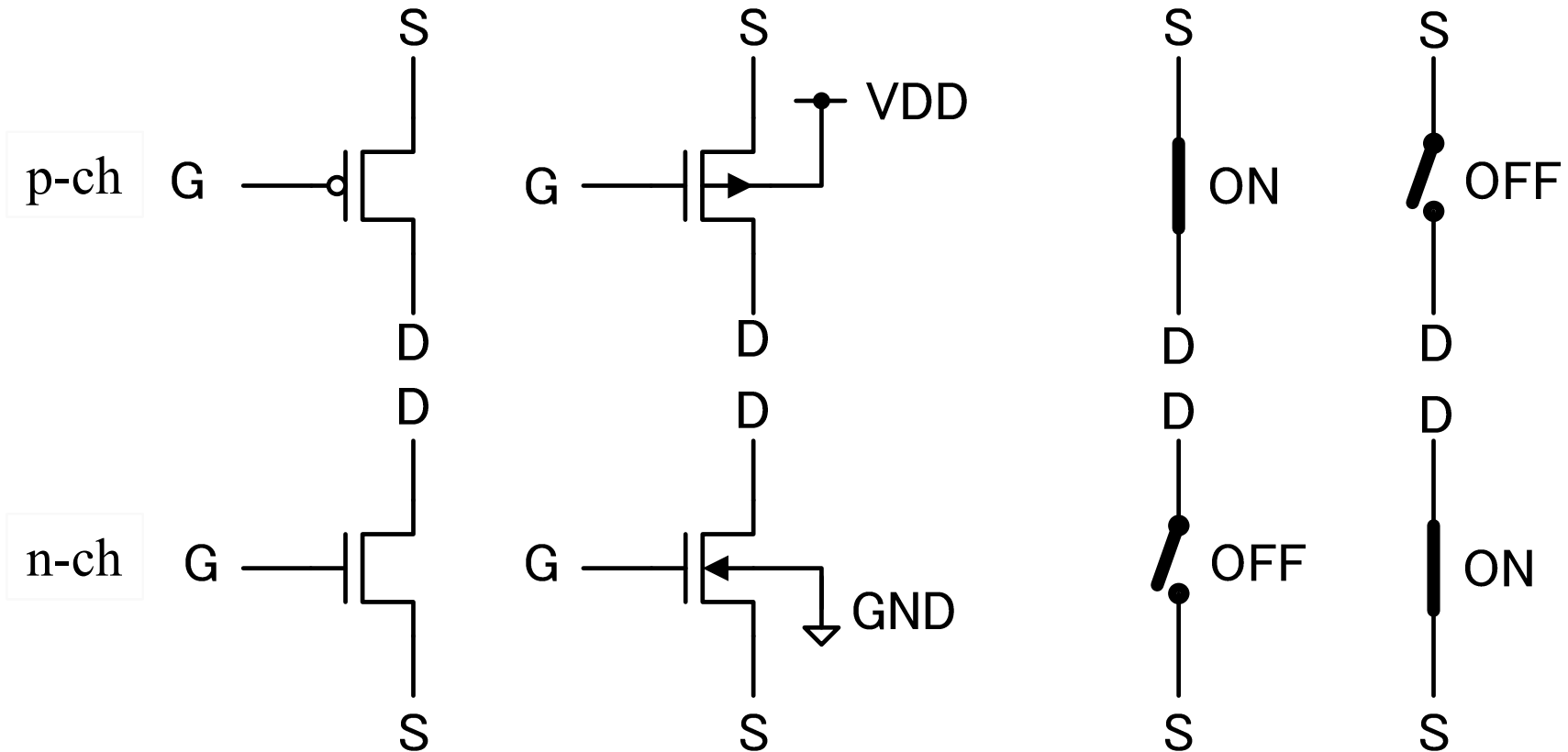


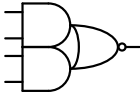
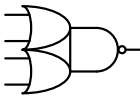
 












MOSFET symbol with 3 terminals


MOSFET symbol with 4 terminals

$V_G = \text{Low}$ $V_G = \text{High}$
Analogy of switch

Primitive logic gates

  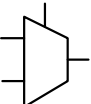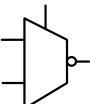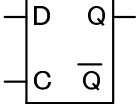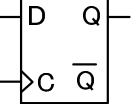Combinational logic		Sequential logic	
1 stage	2 stages	Latch	Flip-flop
     	       		



Inverter

 

Truth table

IN	OUT
0	1
1	0

Schematic

  


The terminal of OUT is switched to VDD or GND.


Connection of body terminal

The MOSFET cannot turn on the GND.


p-ch

 


A p-ch MOSFET can output VDD.

 

n-ch

 


The MOSFET cannot turn on the VDD.

 



A n-ch MOSFET can output GND.

General form of the static logic

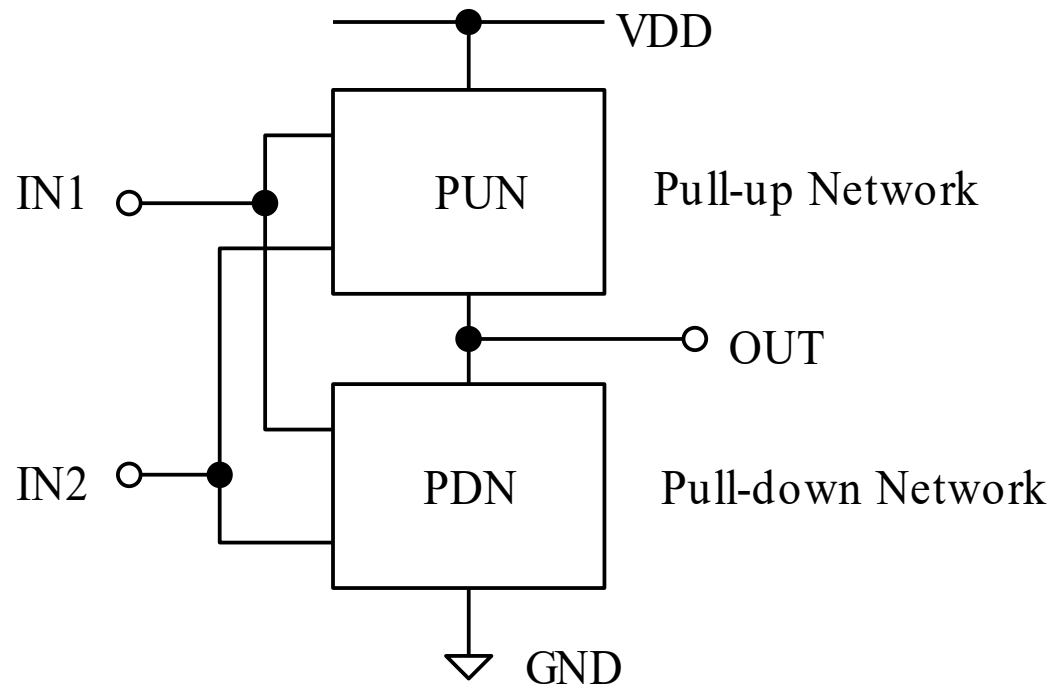



- { A **pull-up network** is a switch network for VDD.
- { A **pull-down network** is a switch network for GND.

2-input switch networks

  


PUN consists of p-ch MOSFETs.

PDN consists of n-ch MOSFETs.

  

Function of 2-input NAND

Symbol

 

Truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

de Morgan's laws

$$\begin{aligned}
 \longrightarrow Y &= \overline{A + B} & \longrightarrow & \text{p-ch MOSFET network} \\
 &= \overline{A \cdot B} & \longrightarrow & \text{n-ch MOSFET network}
 \end{aligned}$$

At first, find 2 equivalent Boolean expressions.

- (1) The expression of each variable negation
- (2) The expression of the total negation


Note: If you cannot find the equivalent Boolean expressions, there is no logic circuit that consists of 1-stage.

Design of 2-input NAND

$$Y = \begin{cases} \overline{A + B} & \longrightarrow \text{PUN} \\ \overline{A \cdot B} & \longrightarrow \text{PDN} \end{cases}$$



PUN

If A=0 OR B=0,
then Y=1

 

PDN


If A=1 AND B=1,
then Y=0

  

Connection of PUN
and PDN

Function of 2-input NOR

Symbol

 


Truth table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

de Morgan's laws

$$Y = \overline{A \cdot B} \longrightarrow \text{p-ch MOSFET network}$$
$$= \overline{A + B} \longrightarrow \text{n-ch MOSFET network}$$

Design of 2-input NOR

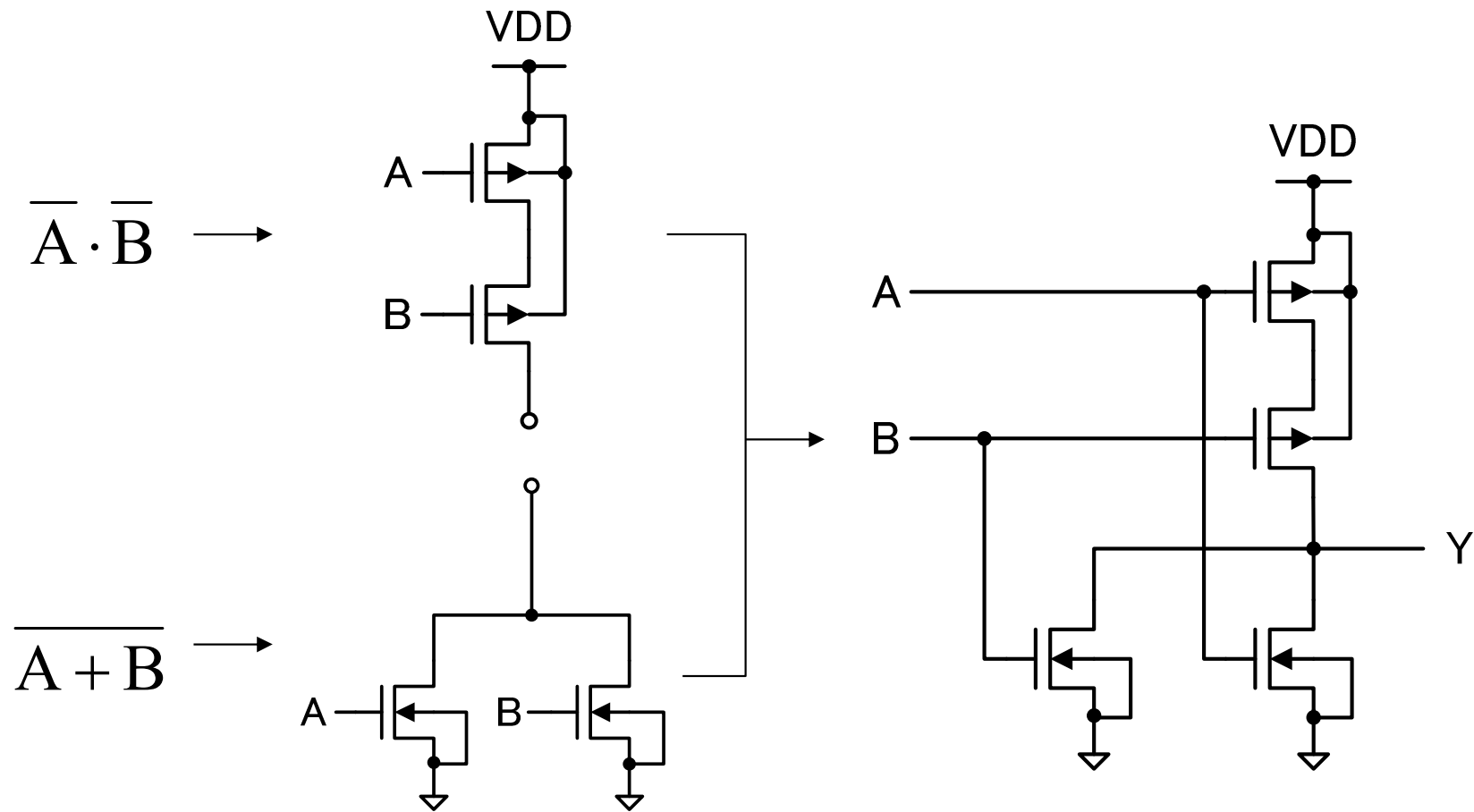



Connection of PUN
and PDN

Design of AND, OR

$$\text{AND} \rightarrow A \cdot B = \overline{\overline{A + B}}$$

$$\text{OR} \rightarrow A + B = \overline{\overline{A \cdot B}}$$

  PUN and PDN cannot build the operations shown above.




AND operation and OR operation require 2 stage(*) logic circuits.

* Stage: 段数

1-stage + 1 stage

Multi-input gates

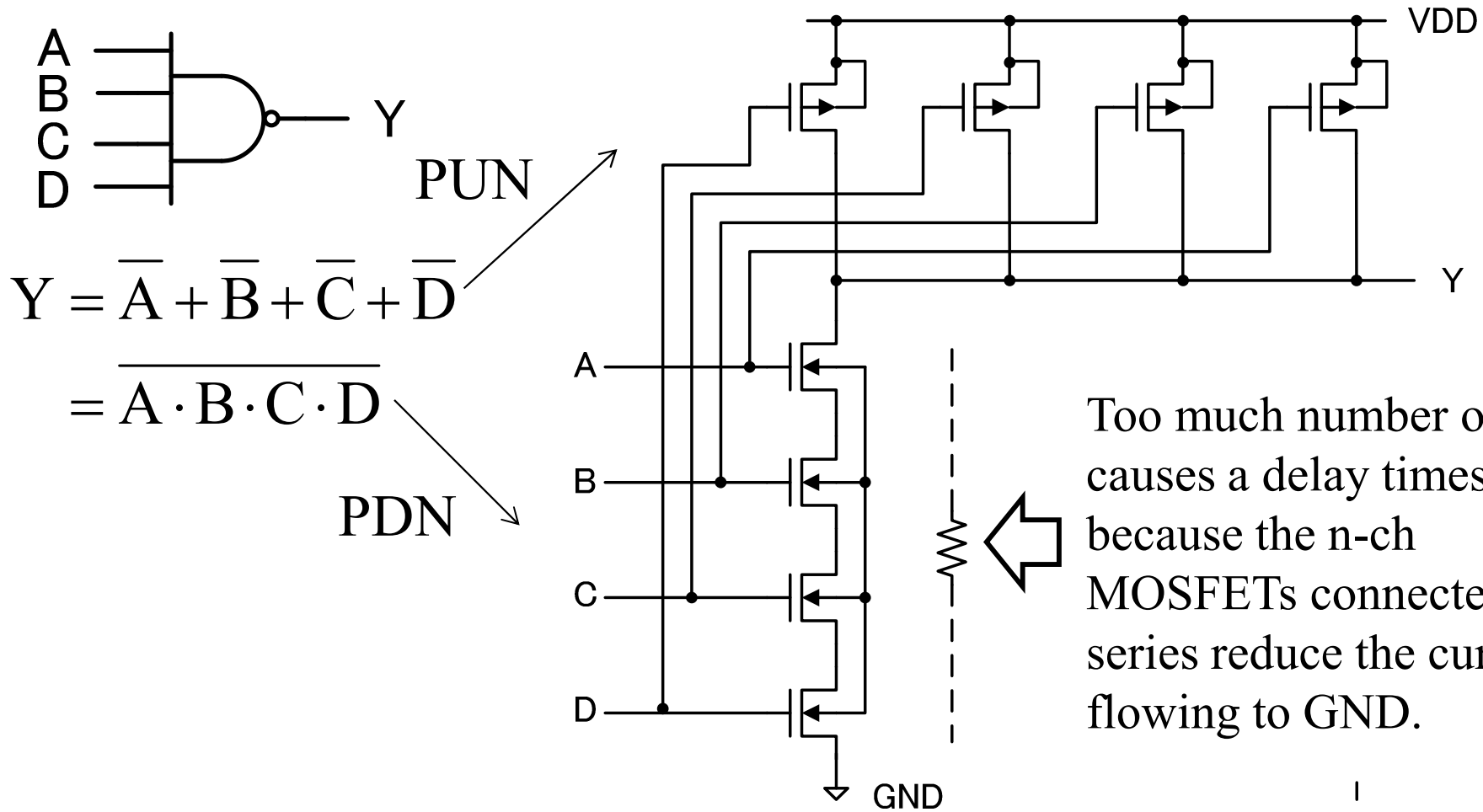

DO not over 4-input.



8-input NAND

$$Y = \overline{A \cdot B \cdot C \cdot D \cdot E \cdot F \cdot G \cdot H}$$

$$= \overline{(A \cdot B \cdot C \cdot D) \cdot (E \cdot F \cdot G \cdot H)}$$

$$= \overline{A \cdot B \cdot C \cdot D} + \overline{E \cdot F \cdot G \cdot H}$$

de Morgan's laws

  

1 stage + 2 stages


8-input AND

$$Y = A \cdot B \cdot C \cdot D \cdot E \cdot F \cdot G \cdot H$$

$$= (A \cdot B \cdot C \cdot D) \cdot (E \cdot F \cdot G \cdot H)$$

$$= \overline{\overline{A \cdot B \cdot C \cdot D} + \overline{E \cdot F \cdot G \cdot H}}$$


de Morgan's laws

 

Counting method of gate stages

- A number of stages is defined as a **maximum number of gate electrodes** of MOSFET on the path from an input port to an output port.

Example of 2- stage gate

 


Propagation delay

- A **propagation delay (伝搬遅延時間)** is defined as a time between 50% points of input and output.
- The propagation delay t_{logic} of the logic circuit is estimated from the number of stages K and the propagation delay t_d of 1-stage gate.


$$t_{logic} = K \cdot t_d$$

3-input AND-NOR gate 1

$$Z = \overline{(A \cdot B) + C}$$

 

10 MOSFETs

 


Construction by PUN and PDN

AND-NOR and OR-NAND are also called a complex gate (複合ゲート).

3-input AND-NOR gate 2


$$\begin{aligned} Y &= \overline{(A \cdot B) + C} \\ &= \overline{A \cdot B} \cdot \overline{C} \\ &= (\overline{A} + \overline{B}) \cdot \overline{C} \end{aligned}$$

de Morgan's laws

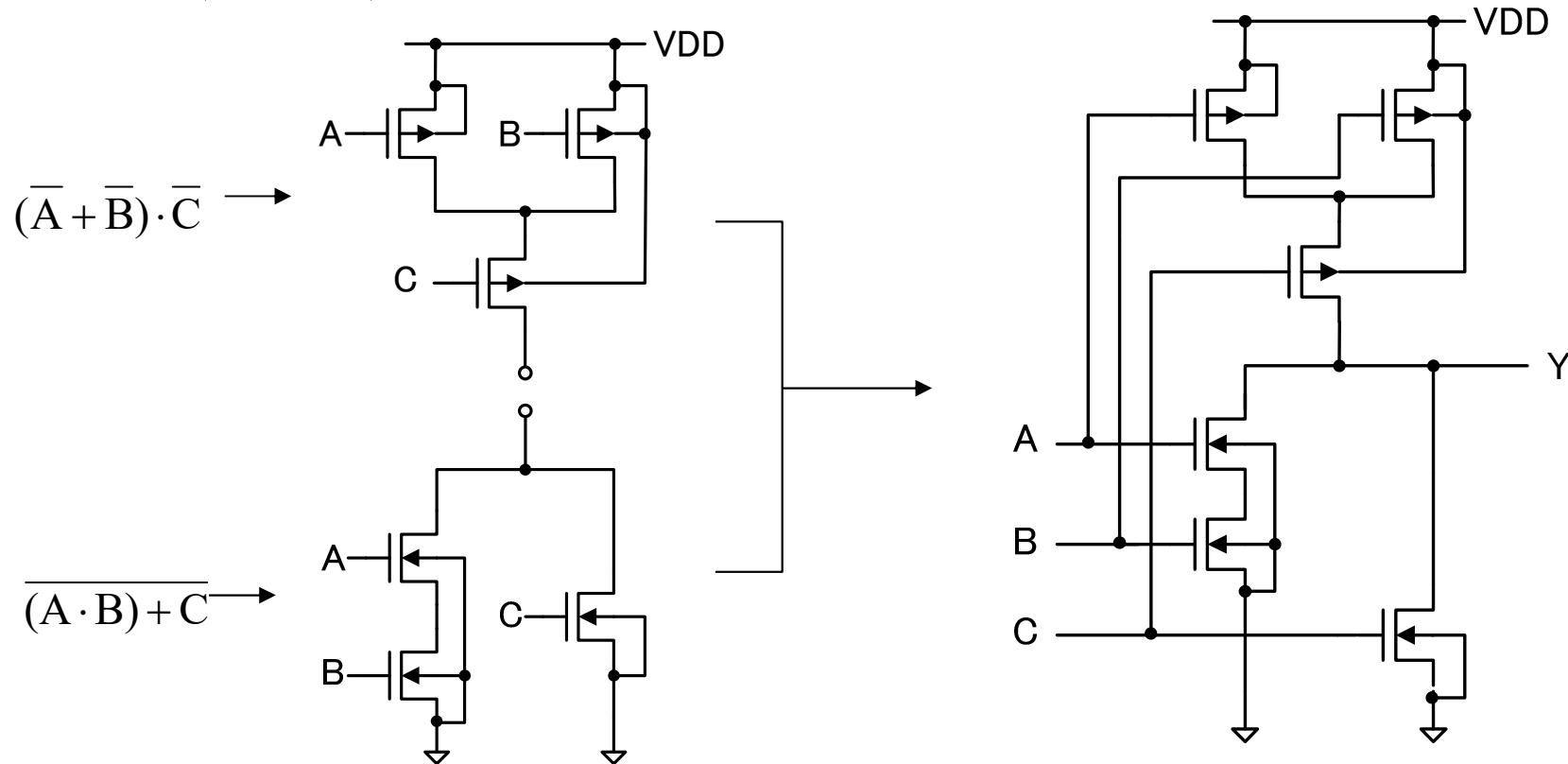


3-input OR-NAND gate 1

$$Y = \overline{(A + B) \cdot C}$$

 

10 MOSFETs

 


Construction by PUN and PDN

3-input OR-NAND gate 2

$$\begin{aligned} Y &= \overline{(A + B) \cdot C} \\ &= \overline{A + B} + \overline{C} \\ &= (\overline{A} \cdot \overline{B}) + \overline{C} \end{aligned}$$

de Morgan's laws

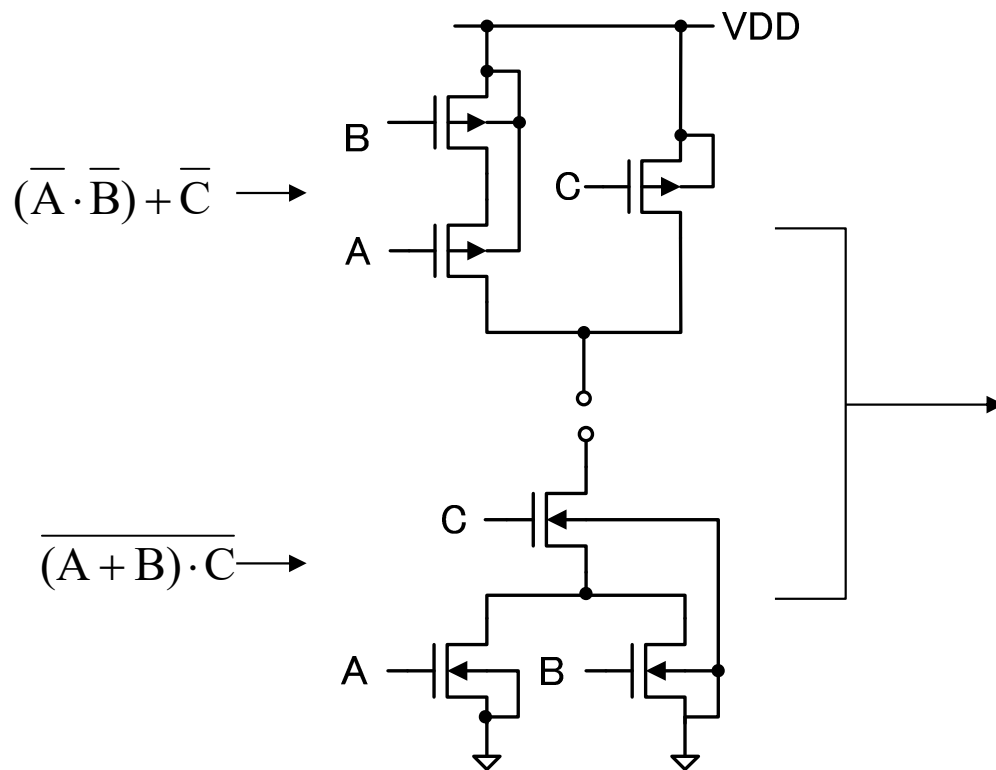

6 MOSFETs, 1 stage

