

2.4 Latch and flip-flop

Primitive gates of sequential circuits


Applications of D-type flip-flop (D-FF)

Register = Parallel connection of D-FFs


Synchronization (同期) = Combinational logic + Register
(without feedback)

Sequential logic = Combinational logic + Register
(with feedback)

D-type latch

 


CMOS

 


Addition of
input switch

D-Latch with enable-input

 


Timing diagram of D-latch

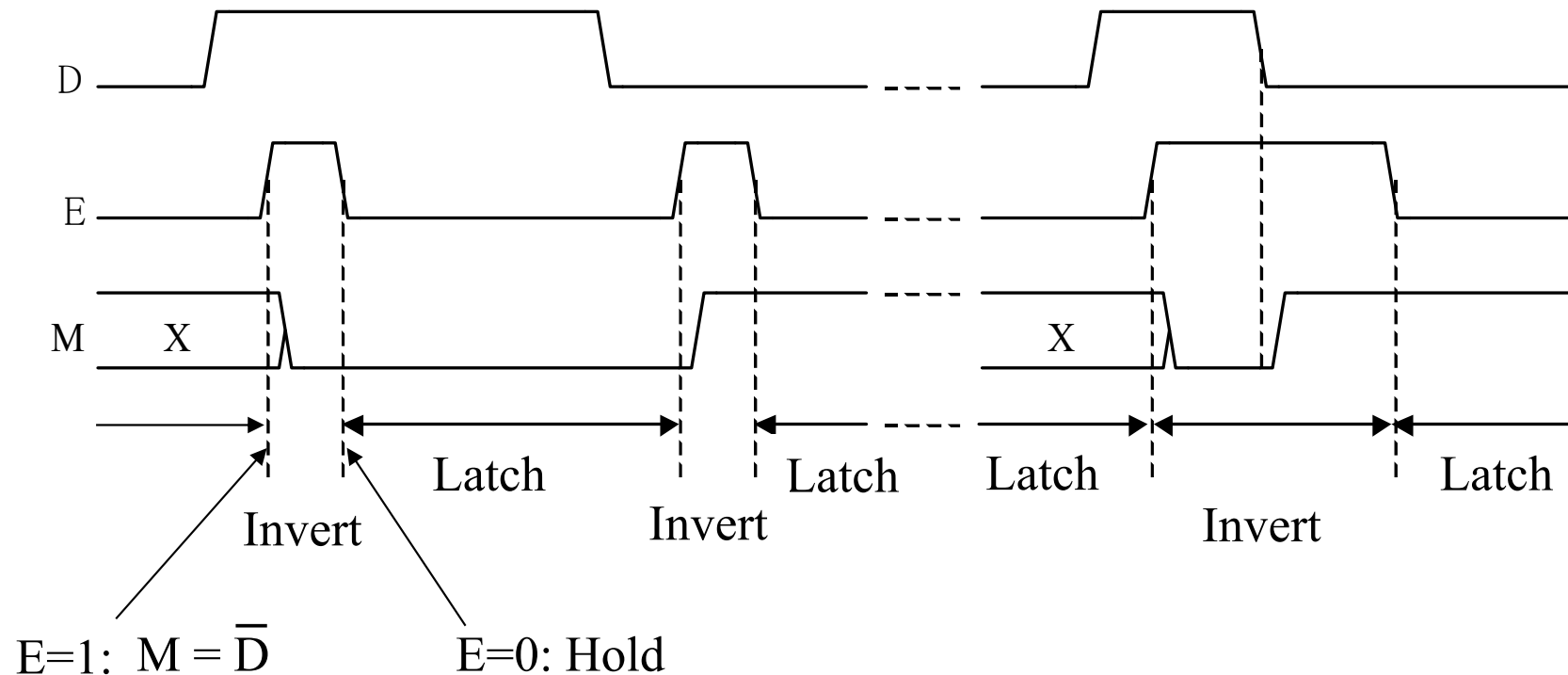


- The input value is latched at the falling edge of E.
- When the clock is input to E, this circuit operates as a **level sensitive flip-flop**.
 - The input value cannot update during the period of $E = 1$.

D-type flip-flop (D-FF)

 

- When the master latch is in the inverter mode, the slave latch hold the logic value of Q and vice versa.
- When the clock is input to ϕ , this circuit operates as an **edge sensitive flip-flop**.


Timing diagram of D-FF

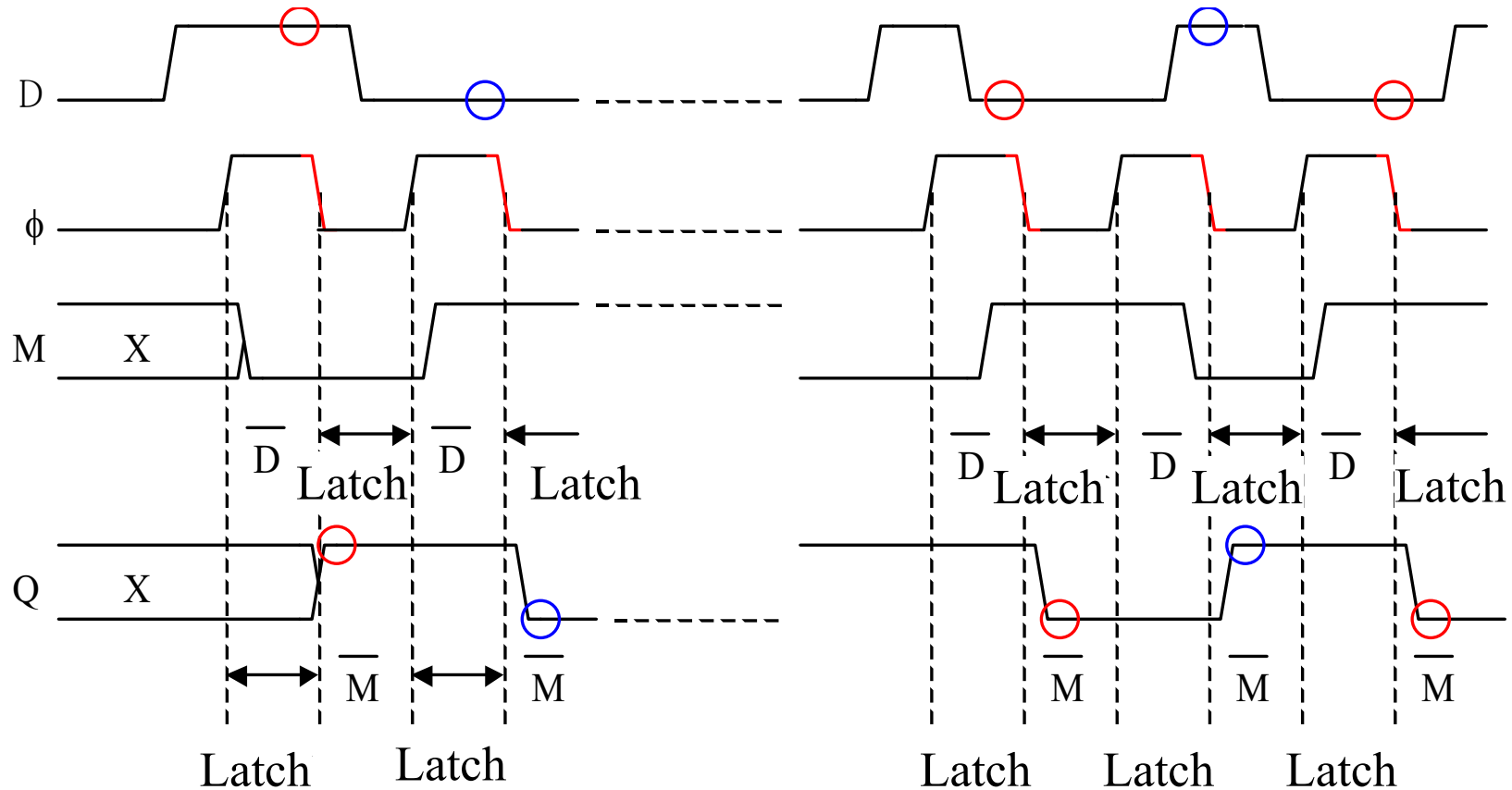

The value of Q is not changed at a timing other than the falling edge of the clock ϕ , because the slave latch hold the output Q, if the value of the input D is changed during $\phi = 1$. If you employ the clock $\bar{\phi}$, the flip-flop updates the output value Q at the rising edge of the clock.

Setup time and hold time

 The **jitter** (timing variation) of the rising edge and the falling edge is observed in the digital signal. Therefore, timing constraints are imposed on the flip-flop.



➔ The prohibited timing
The fluctuation of D at the clock edge causes the unstable state of the positive feedback loop of D-FF (Meta-stable).

Setup time t_s


The value of D should arrive the setup time before the clock edge.

Hold time t_h

The value of D should be held the hold time before the clock edge.

D-FF with reset

Symbol

 


RST	B	M	
0	0	1	\bar{B}
0	1	0	
1	0	1	Set
1	1	1	

RST	B'	Q	
0	0	1	\bar{B}'
0	1	0	
1	0	0	Reset
1	1	0	

Characteristic table


RST	EN	Q_{n+1}
0	0	Q_n (Quiescent state)
0	1	D_n (D-FF operation)
1	0	Reset
1	1	Reset

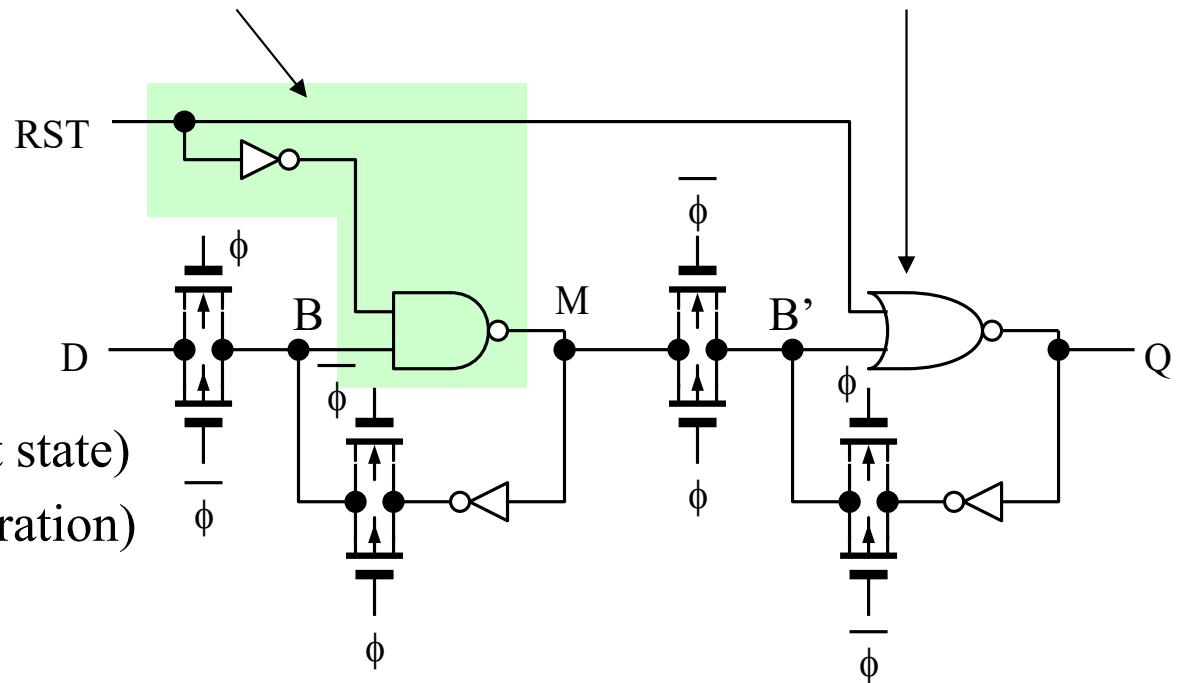

The term "Reset (RST)" is the same as the term "Clear (CLR)".


D-FF with Enable

 - EN=0: Q is input into D-FF. (The output is fed back to the input of D-FF.)
- EN=1: D is input into D-FF. (The operation is the same as D-FF.)





2 types of reset

 - Asynchronous reset (非同期リセット) → Circuits shown in slide 8
 - The output value is reset at the rising edge of RST signal.



  - Synchronous reset (同期リセット)
 - The output value is reset at the rising edge of clock signal, when the RST signal is asserted.



T-FF (Toggle flip-flop)

Other flip-flops can be derived from D-FF.



T-FF	
T	Q_{n+1}
0	Q_n
1	$\overline{Q_n}$

➔

D-FF (Synchronization)	
D	Q_{n+1}
0	0
1	1

$$Q_{n+1} = \overline{T} \cdot Q_n + T \cdot \overline{Q_n} = T \oplus Q_n = D$$

Edge trigger T-FF

  

JK-FF


JK-FF		
J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

➔

D-FF	
D	Q_{n+1}
0	0
1	1
Synchronization	

$$\begin{aligned}
 Q_{n+1} &= \overline{J} \cdot \overline{K} \cdot Q_n + J \cdot \overline{K} + J \cdot K \cdot \overline{Q_n} = \overline{J} \cdot \overline{K} \cdot Q_n + J \cdot \overline{K} \cdot (Q_n + \overline{Q_n}) + J \cdot K \cdot \overline{Q_n} \\
 &= J \cdot \overline{Q_n} + \overline{K} \cdot Q_n = \overline{(\overline{J} + Q_n)} \cdot \overline{(K + \overline{Q_n})} = D
 \end{aligned}$$

Edge trigger JK-FF

 

Register


I/O register

Pipeline register

Instruction register

Address register

...

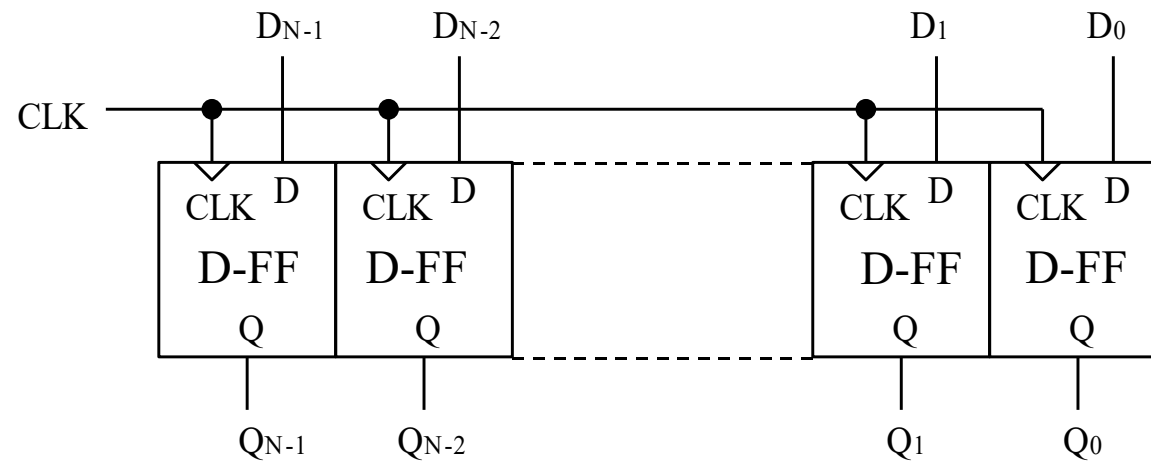

N bit Register