

# 11. Phase compensation


Kanazawa University  
Microelectronics Research Lab.  
Akio Kitagawa

# 11.1 AC characteristics of CS amplifier



- A main factor to decide an AC characteristic
  - Output capacitance
    - Capacitive Load + Parasitic capacitance
  - Input capacitance
    - Parasitic capacitance
  - Input-output capacitance
    - Parasitic capacitance

(AC characteristic: The small-signal frequency response)


# Parasitic capacitance

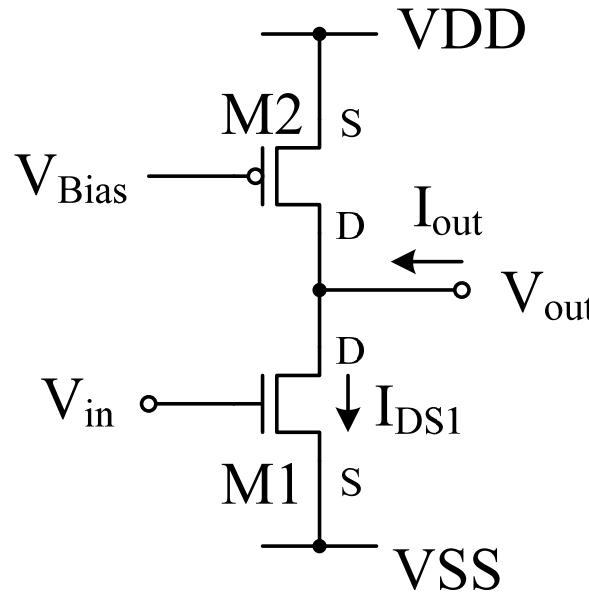

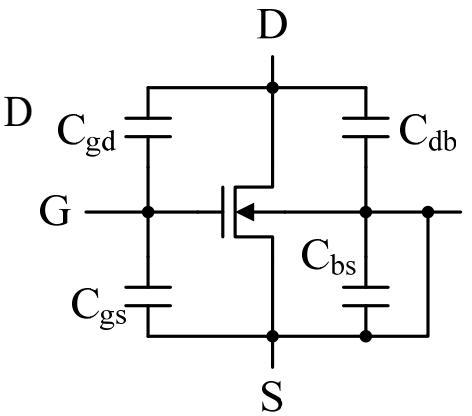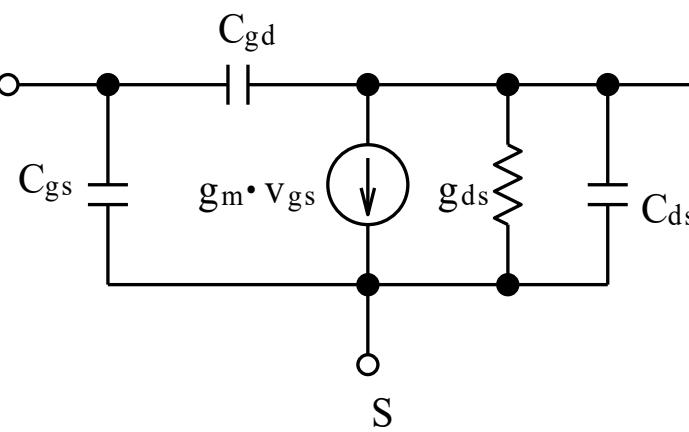
High frequency small-signal equivalent circuit of MOSFET



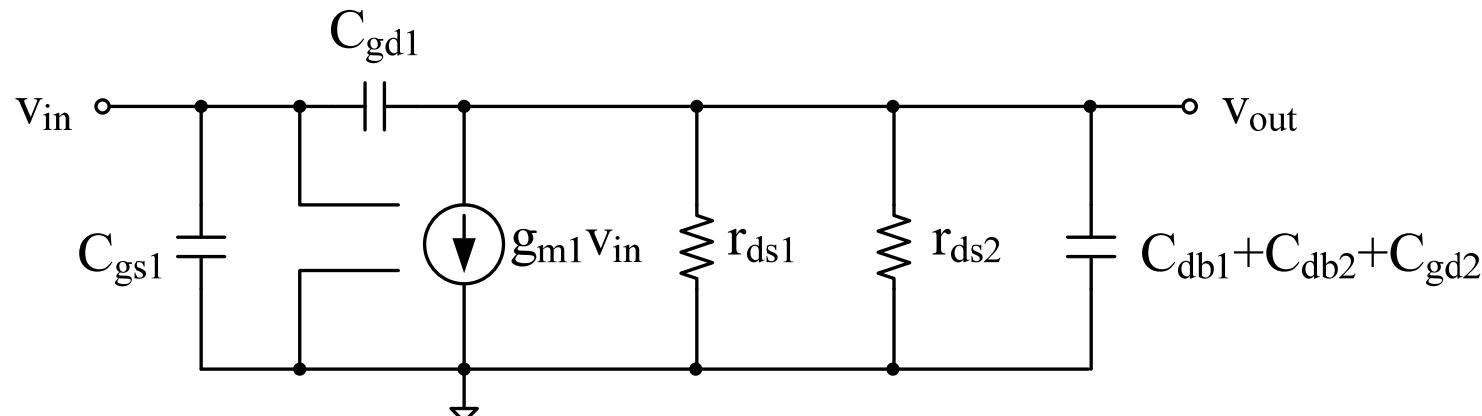High frequency small-signal equivalent circuit of CS amplifier



# Influence of the output capacitance

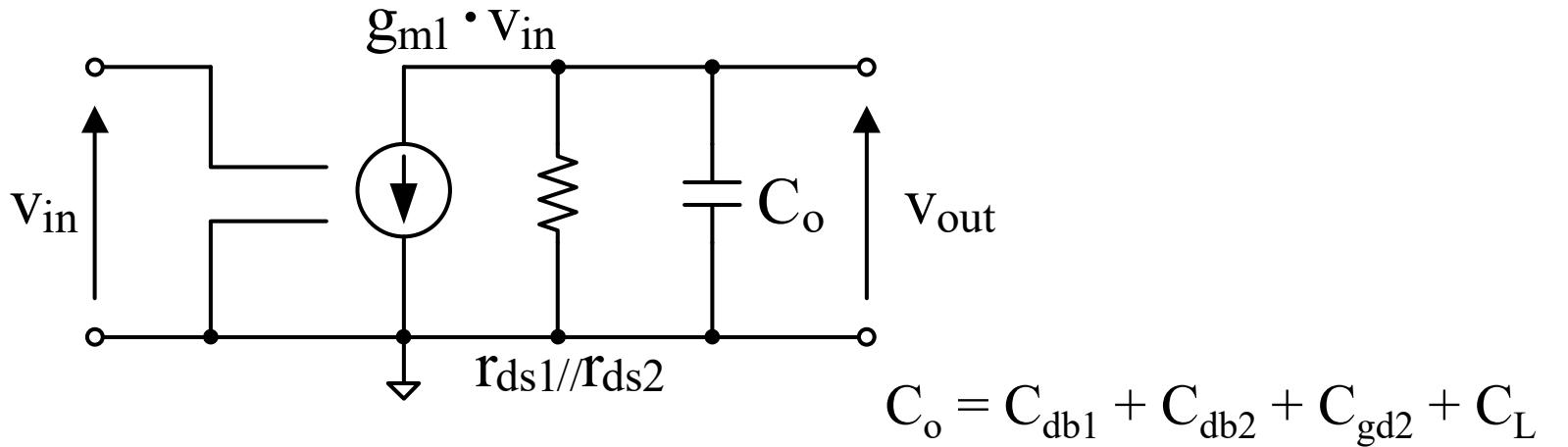


$$v_{out} = \frac{1}{\frac{1}{r_{ds1} // r_{ds2}} + j\omega \cdot C_o} (-g_m v_{in})$$

$$\begin{aligned} A(\omega) \equiv \frac{v_{out}}{v_{in}} &= \frac{-g_m (r_{ds1} // r_{ds2})}{1 + j\omega \cdot C_o (r_{ds1} // r_{ds2})} \\ &= \frac{-A_0(\omega = 0)}{1 + j\omega \cdot C_o (r_{ds1} // r_{ds2})} \end{aligned}$$

# Bode diagram of the CS amplifier

$$|A(\omega)| = \frac{A_0}{\sqrt{1 + \omega^2 / \omega_{po}^2}}$$
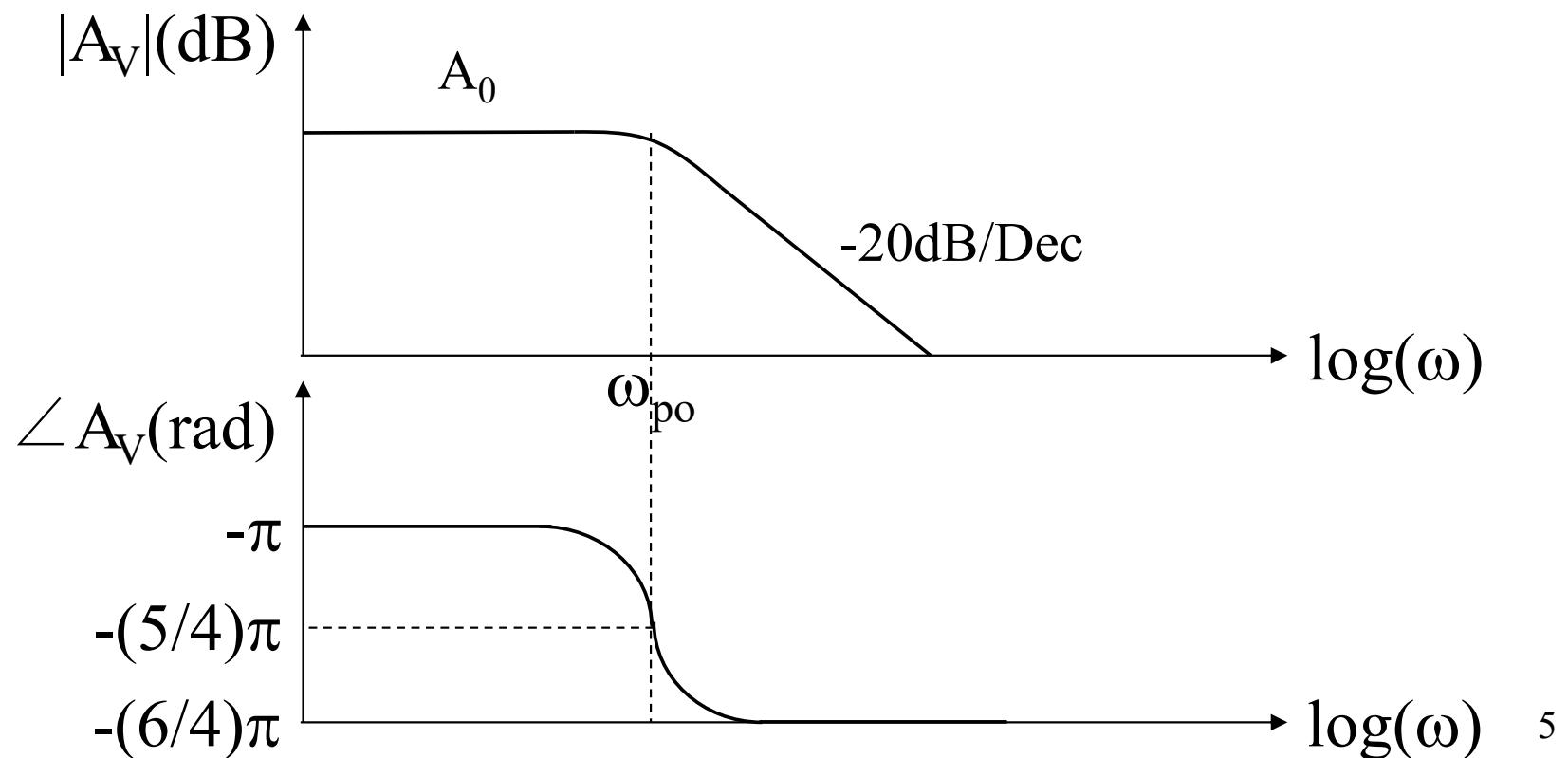
$$\omega_{po} = \frac{1}{C_o(r_{ds1} // r_{ds2})} \quad (\text{pole frequency of output})$$



# Bias dependence of a pole frequency

$$\begin{cases} g_{m1} = \sqrt{2\beta_1 I_{DS1}} \\ r_{ds1} // r_{ds2} = \frac{1}{g_{ds1} + g_{ds2}} = \frac{1}{(\lambda_1 + \lambda_2) \cdot I_{DS1}} \end{cases}$$

$$A_0 = g_{m1} (r_{ds1} // r_{ds2}) = \frac{\sqrt{2\beta_1}}{\lambda_1 + \lambda_2} \frac{1}{\sqrt{I_{DS1}}} \quad (\text{DC gain})$$

$$\omega_{po} = \frac{1}{C_o (r_{ds1} // r_{ds2})} = \frac{(\lambda_1 + \lambda_2) \cdot I_{DS1}}{C_o} \quad (\text{pole frequency})$$

$$\omega_{po} \cdot A_0^2 = \frac{1}{C_o} \frac{2\beta}{(\lambda_1 + \lambda_2)}$$

The product of the  $\omega_{po}$  and  $A_0^2$  is independent on the bias current.


# Unity gain frequency $\omega_u$ (= BGP)

$$\frac{A_0}{\sqrt{1+\omega_u^2/\omega_{po}^2}} = 1$$

$$\omega_u = \sqrt{(A_0^2 - 1)} \omega_{po}$$


$$\simeq A_0 \omega_{po} = \frac{g_m}{C_o} \propto I_{DS}$$

$$= \frac{\beta(V_{GS} - V_T)}{C_o}$$

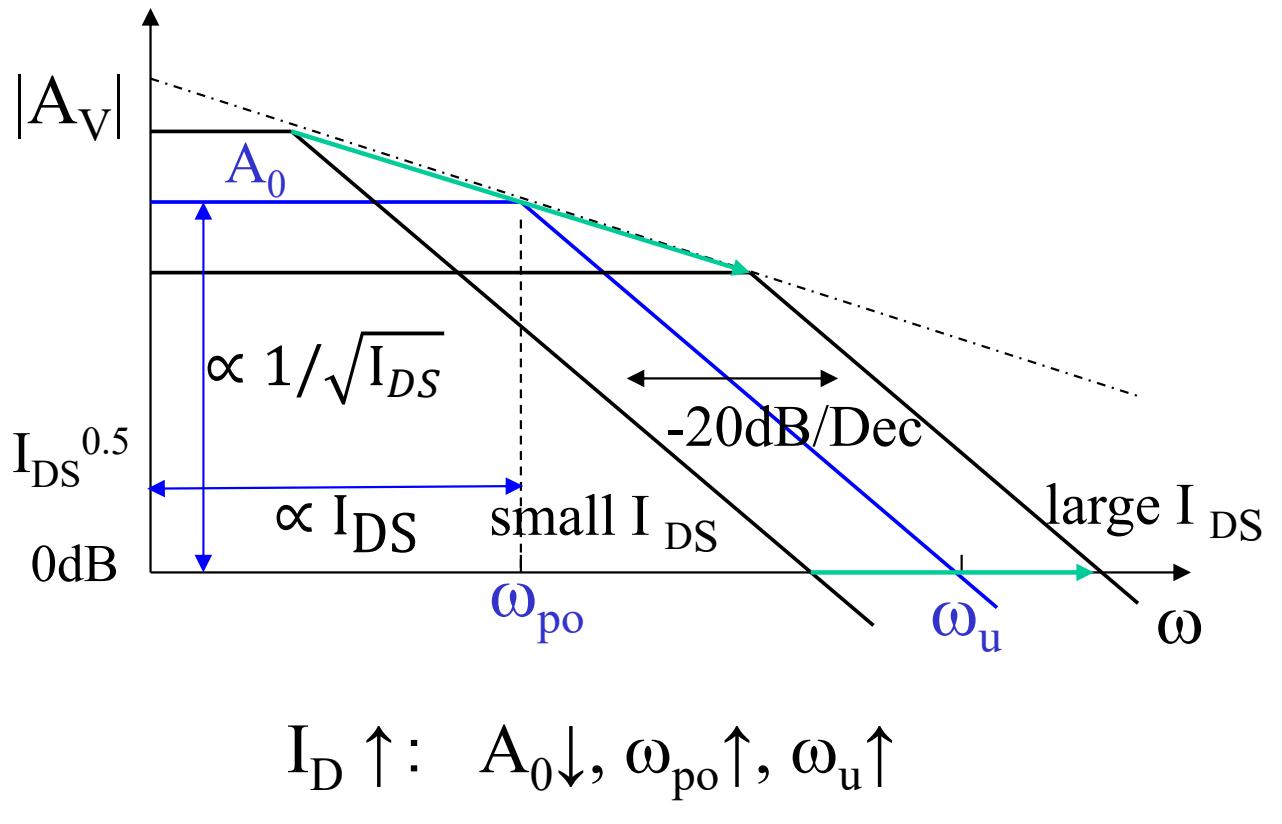

NOTE:  $\omega_u \doteq \text{GBP}$  (Gain Bandwidth Product)

# Influence of the input capacitance

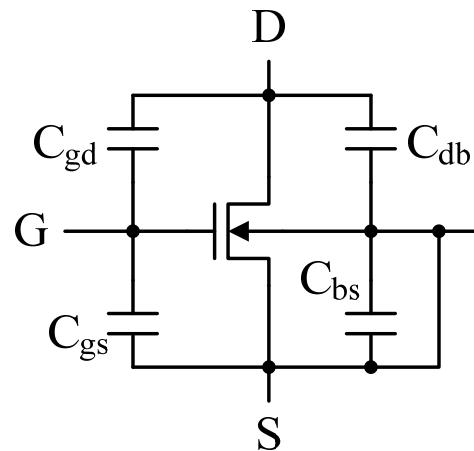


Output resistance of preceding stage

Miller effect  $\downarrow$

$$C_i = C_{gs1} + C_{gd1}(1 + A) \cong AC_{gd1}$$


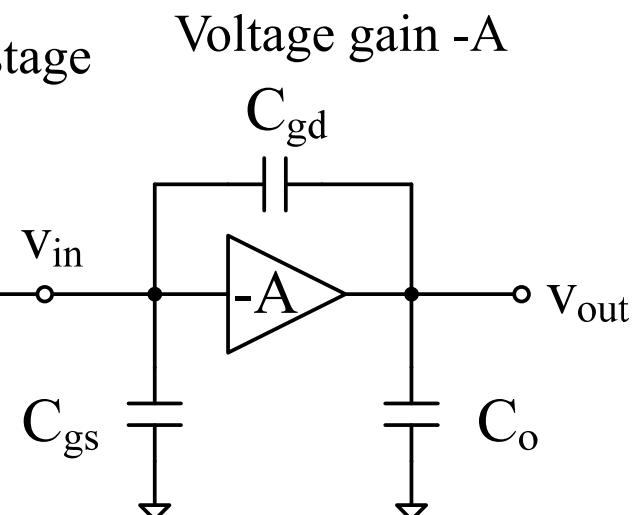
$$\omega_{pi} \cong \frac{1}{AR_i C_{gd1}} \quad (\text{pole frequency of input})$$



$$C_o = C_{db1} + C_{db2} + C_{gd2} + C_L$$

NOTE: The pole frequency is low when a voltage gain is large.
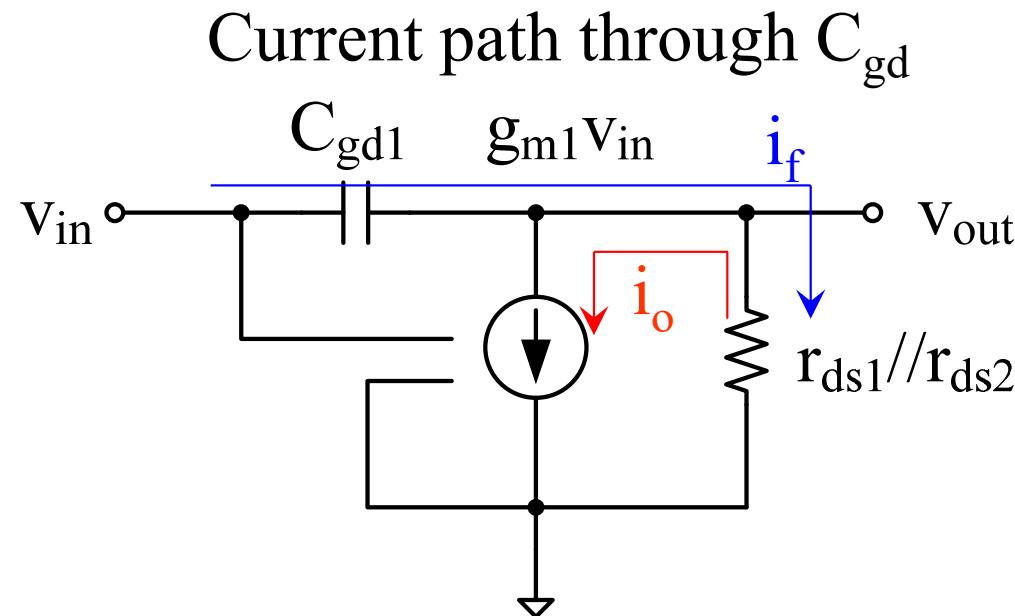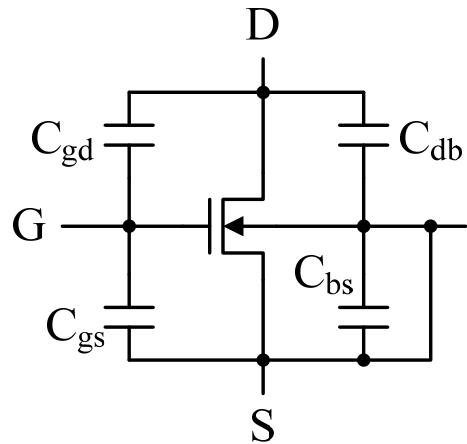
# Influence of the input-output capacitance (1)



$$\left\{ \begin{array}{l} v_{out} = (r_{ds1} // r_{ds2})(i_f - i_o) \\ i_f = j\omega \cdot C_{gd}(v_{in} - v_{out}) \end{array} \right.$$

# Influence of the input-output capacitance (1)

by competitive current  $i_o$  and  $i_f$       Normally  $(r_{ds1}/r_{ds2}) < 1/g_{m1}$ ,  
 $\omega_z < \omega_{pgd}$

$$\frac{v_{out}}{v_{in}} = \frac{- (r_{ds1} // r_{ds2}) g_{m1} (1 - j\omega \cdot \frac{C_{gd}}{g_{m1}})}{1 + j\omega \cdot C_{gd} (r_{ds1} // r_{ds2})} \equiv \frac{- (r_{ds1} // r_{ds2}) g_{m1} (1 - j\omega / \omega_z)}{1 + j\omega / \omega_{pgd}}$$

$i_f$  : Forward transmission signal from G to D


$i_o$  : Normally amplified signal

The balance of  $i_f$  and  $i_o$  generate the zero.
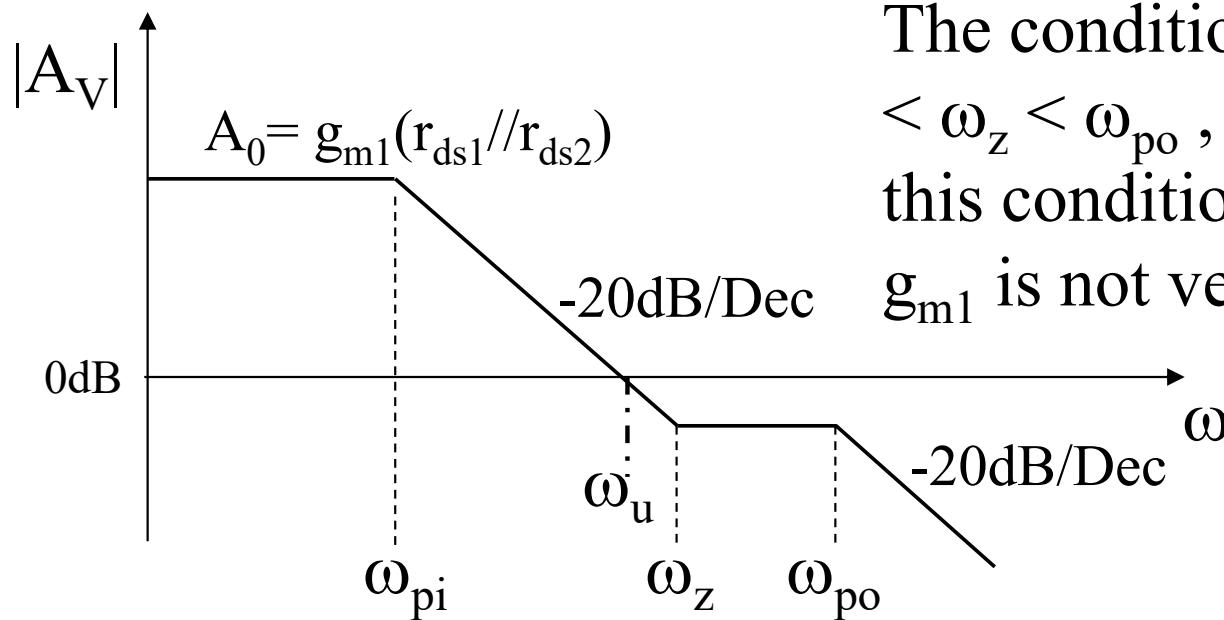
# Summary of AC characteristics of the CS amplifier

$$A_V = \frac{A_0(1 - j\omega/\omega_z)}{(1 + j\omega/\omega_{pi})(1 + j\omega/\omega_{po})}$$


2-pole and 1-zero transfer function  
(The  $\omega_{pgd}$  is placed in the very high frequency, thus it is usually negligible.)



The condition may not keep  $\omega_{pi} < \omega_z < \omega_{po}$ , but it is often that this condition is observed when  $g_{m1}$  is not very large.

**NOTE:** Pole in the left half plane and zero in the right half plane turns phase -90 degrees.

# Phase characteristic

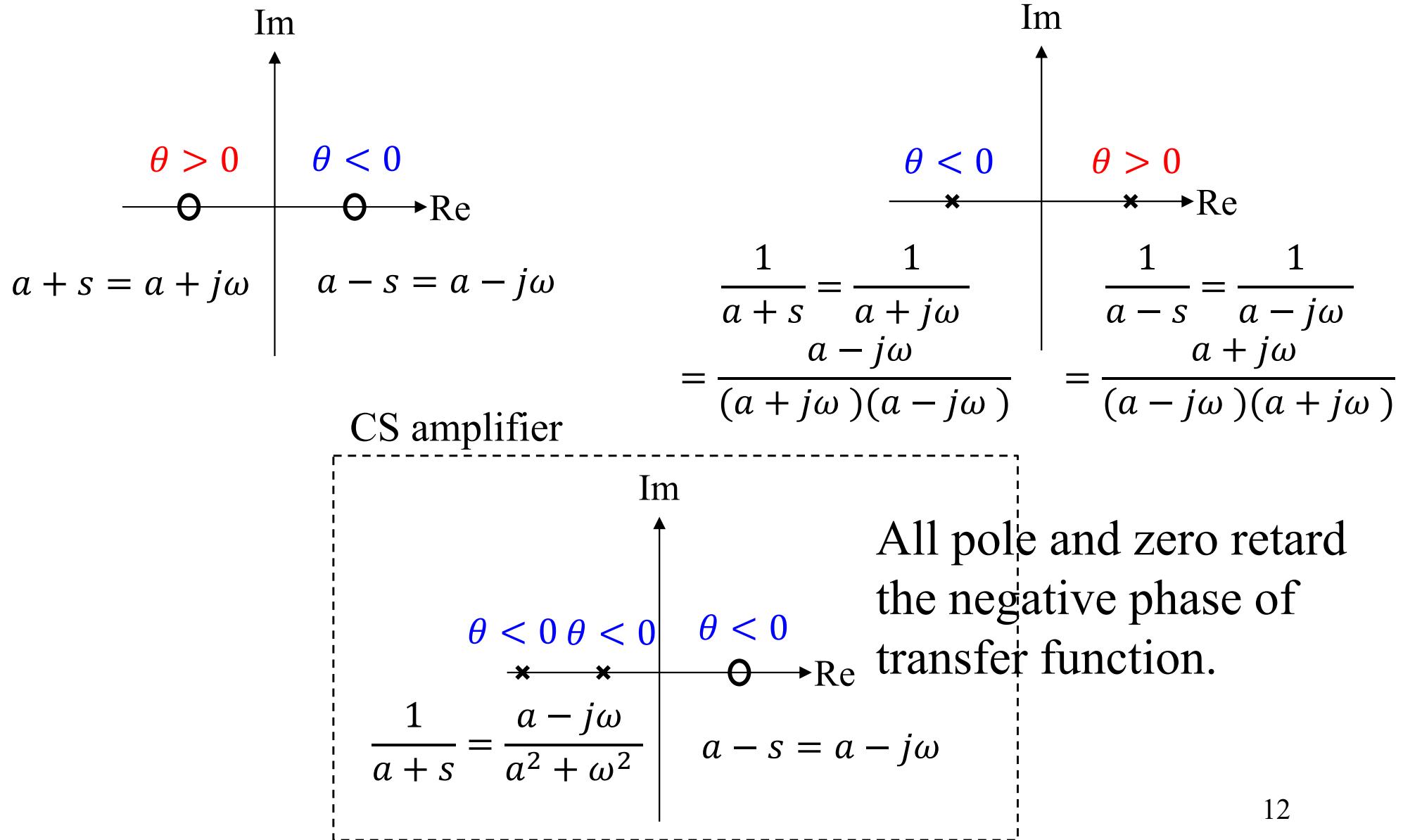


# 11.2 AC characteristics of cascode amplifier

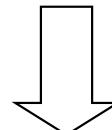
# Influence of the input capacitance

$$\left\{ \begin{array}{l} A_{M1} = \frac{g_{m1}r_{ds1}}{1 + g_{m2}r_{ds1}} \approx \frac{g_{m1}}{g_{m2}} \quad (\text{Voltage gain of M1}) \\ \omega_{pi} = \frac{1}{R_{in} \{ C_{gs1} + (1 + \frac{g_{m1}}{g_{m2}})C_{gd1} \}} \end{array} \right.$$


The voltage gain of M1 is almost unity, because the input resistance of M2 is  $1/gm_2$ .



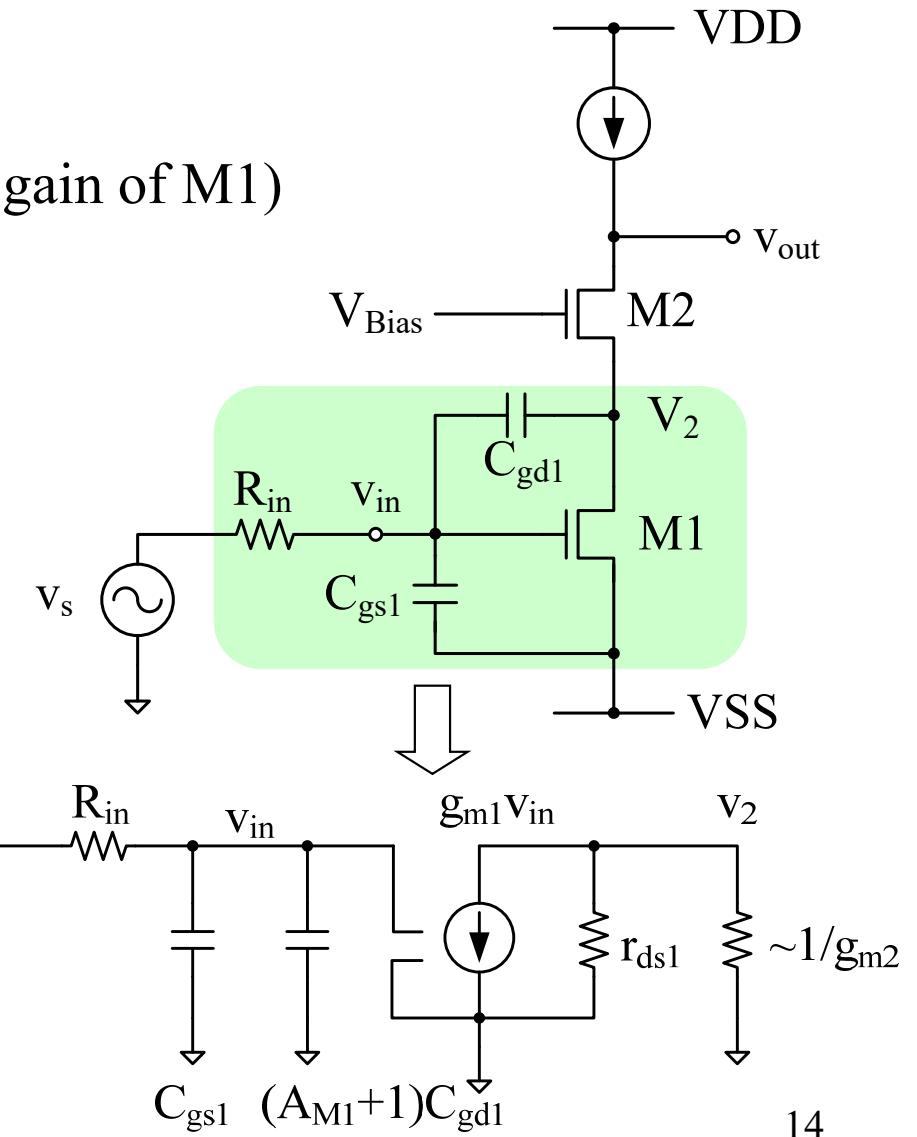Miller effect is negligible and  $\omega_{pi}$  is very high.



# Influence of the output capacitance

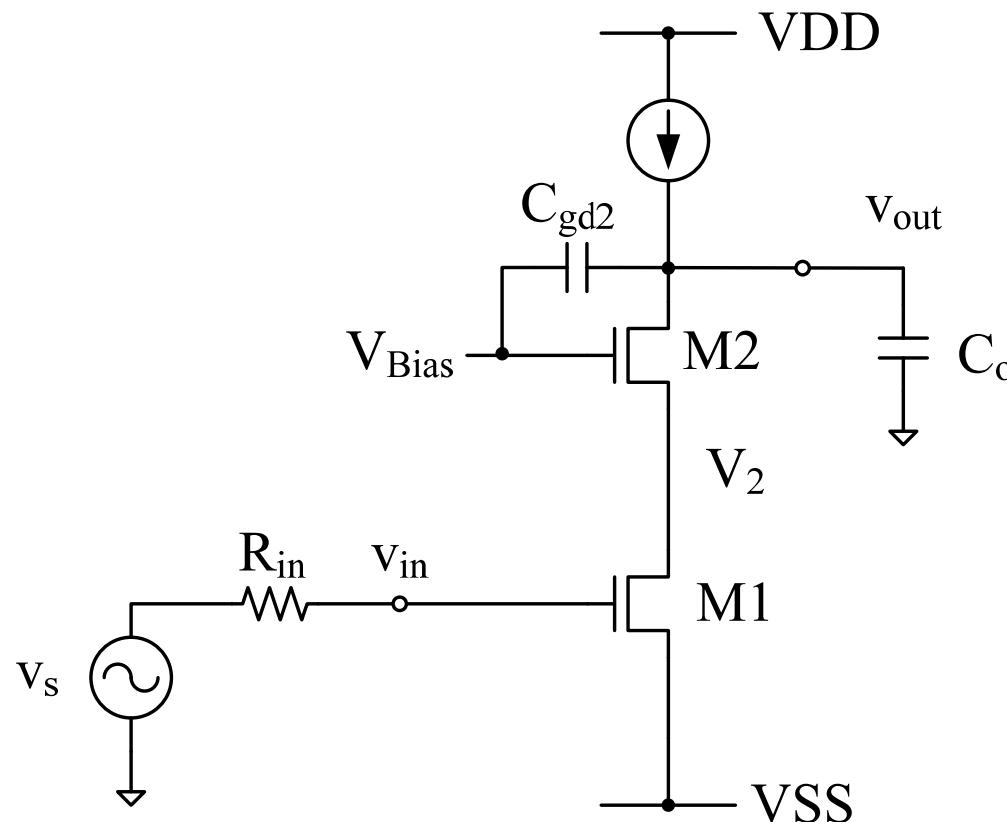


Output resistance of M2:

$$R_{out} = g_m r_{ds2} r_{ds1}$$
$$\therefore \omega_{po} = \frac{1}{R_{out}(C_{gd2} + C_o)}$$

Normally  $\omega_{po} < \omega_{pi}$ , because the output resistance of cascode amplifier  $R_{out}$  is very large.
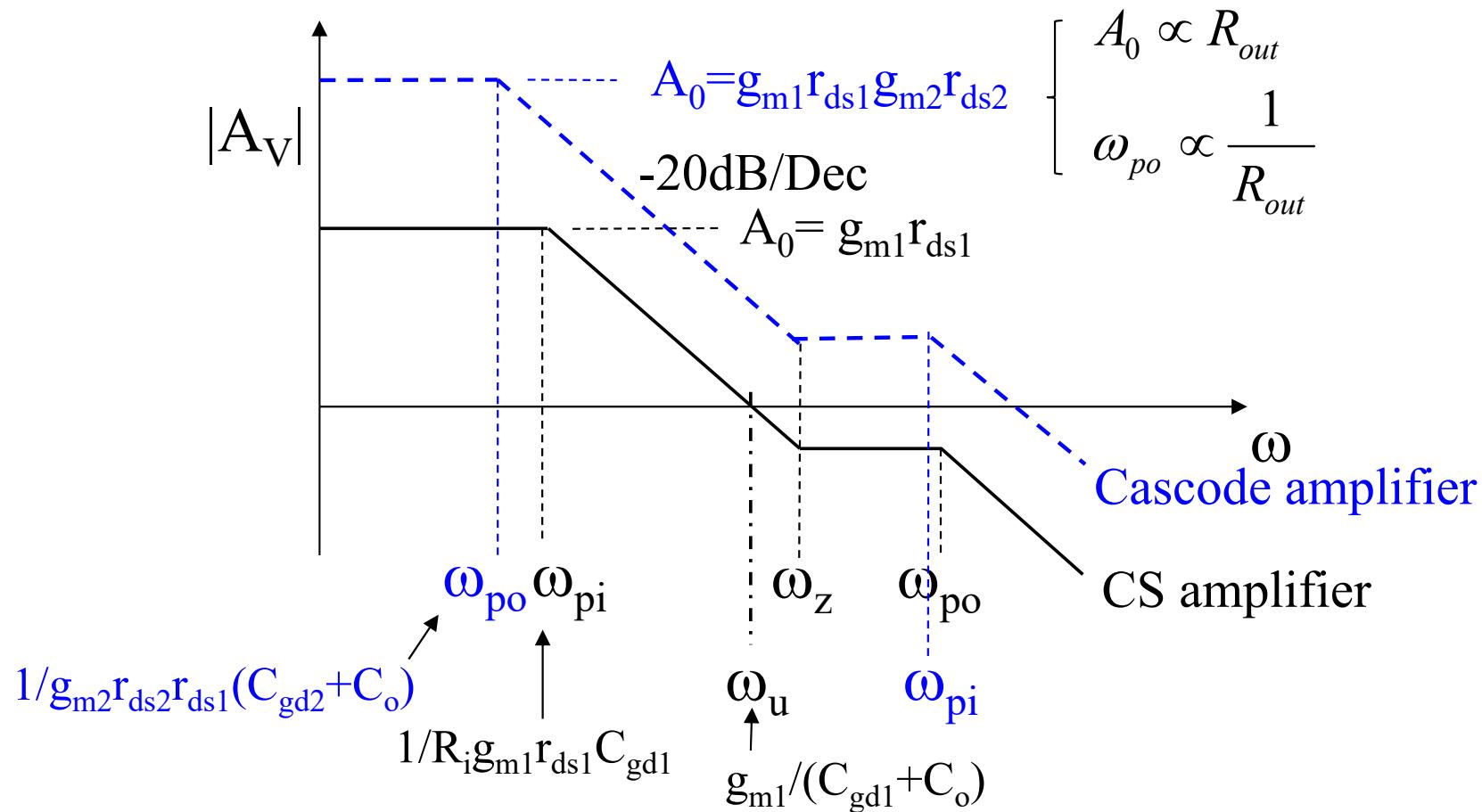
# Comparison between Cascode amplifier and CS amplifier




# 11.3 AC performance of amplifiers

# Simplified 1-pole model of AC characteristic of amplifiers

$$A_V(\omega) = \frac{A_0}{1 + j\omega/\omega_p} = \frac{A_0 \cdot \omega_p}{j\omega + \omega_p} \approx \frac{\omega_u}{j\omega + \omega_p}$$


$$|A_V(\omega)| = \left| \frac{v_{out}}{v_{in}} \right| = \frac{A_0}{\sqrt{1 + \omega^2 / \omega_p^2}}$$

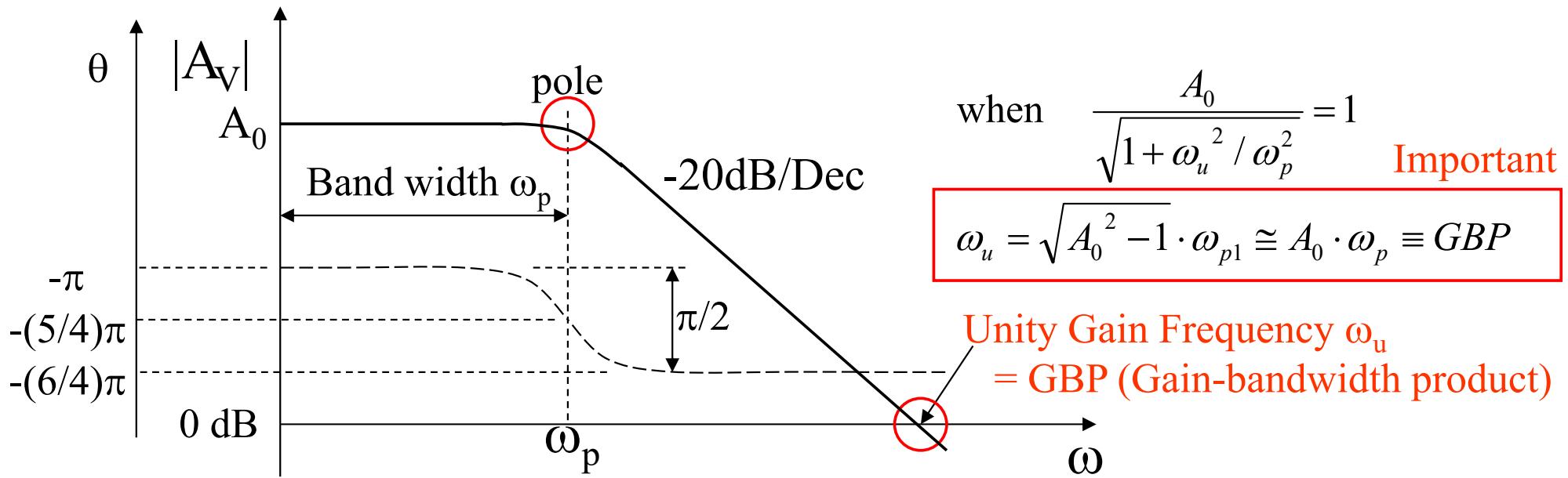[ $\omega_p$ : the pole frequency (or cut-off frequency)  
 $\omega_u$ : the unity gain frequency]



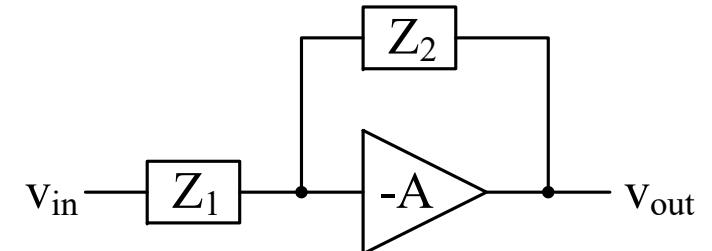
# Gain error of circuits and GBP

Gain of NFB amplifier  $G = \frac{v_{out}}{v_{in}} = \frac{-\frac{Z_2}{Z_1}}{1 + \frac{Z_2}{Z_1} + \frac{A}{Z_1}} \xrightarrow{A \rightarrow \infty} -\frac{Z_2}{Z_1}$



Gain error of NFB amplifier  $\frac{\Delta G}{G} = \frac{G(\infty) - G(A)}{G(\infty)} = \frac{1 + \frac{Z_2}{Z_1}}{A + (1 + \frac{Z_2}{Z_1})}$

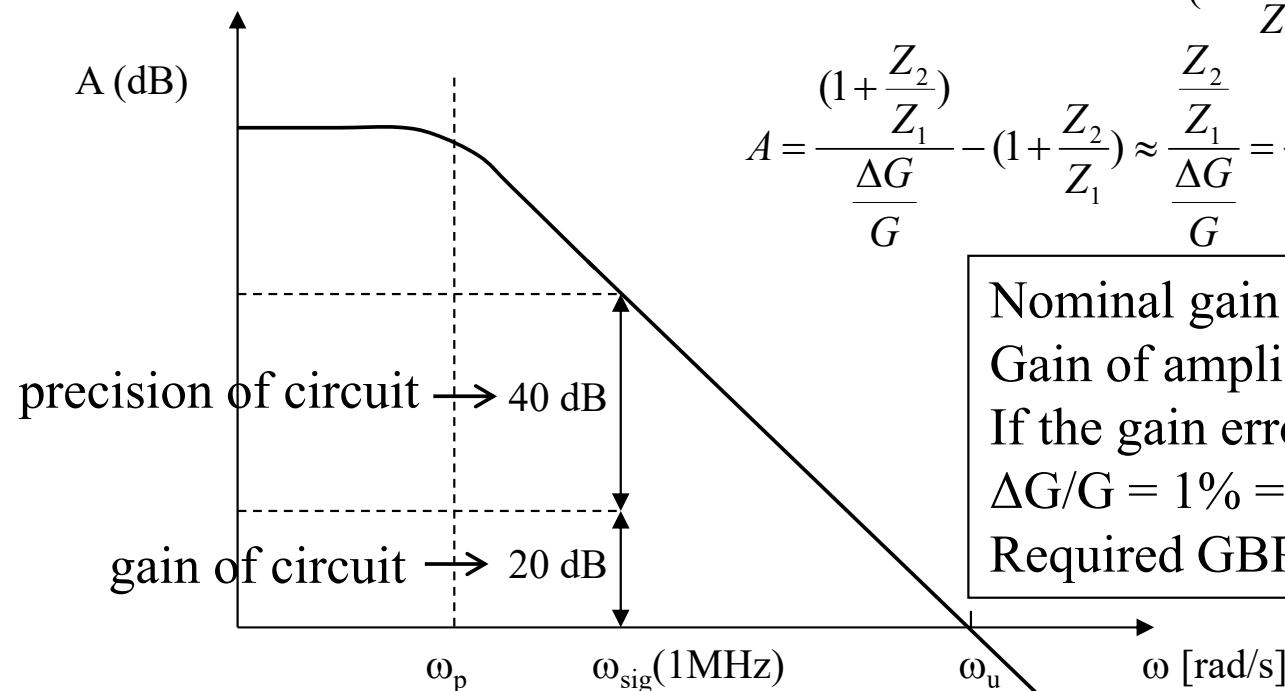
$$A = \frac{(1 + \frac{Z_2}{Z_1})}{\frac{\Delta G}{G}} - (1 + \frac{Z_2}{Z_1}) \approx \frac{\frac{Z_2}{Z_1}}{\frac{\Delta G}{G}} = \frac{G}{\frac{\Delta G}{G}} = G[dB] - \frac{\Delta G}{G}[dB]$$




Nominal gain  $G = 10.0 = 20 \text{ [dB]}$  (Ideal value)  
 Gain of amplifier A at  $\omega_{sig} = 60 \text{ [dB]}$   
 If the gain error should be suppressed below  
 $\Delta G/G = 1\% = 0.01 = -40 \text{ [dB]}$ ,  
 Required GBP  $\omega_u = 1[\text{MHz}] * 1000 = 1[\text{GHz}]$

NOTE: The gain error does not depend on  $\omega_p$ .

# Frequency dependence of the gain error

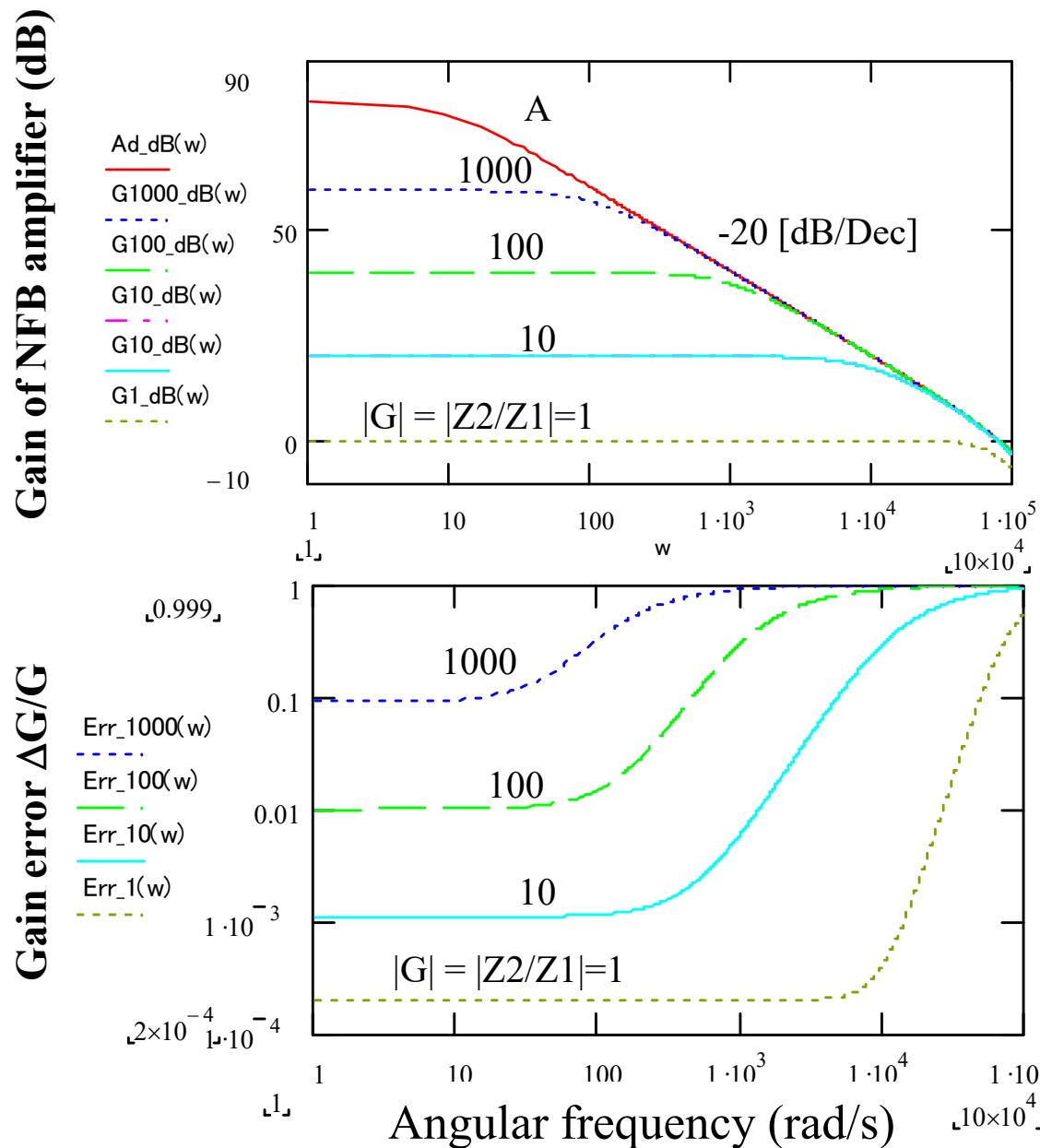


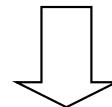The gain error is increased in high frequency, because the gain  $A$  is reduced.




The large GBP guarantees the low gain error of the circuit in the wide frequency range.
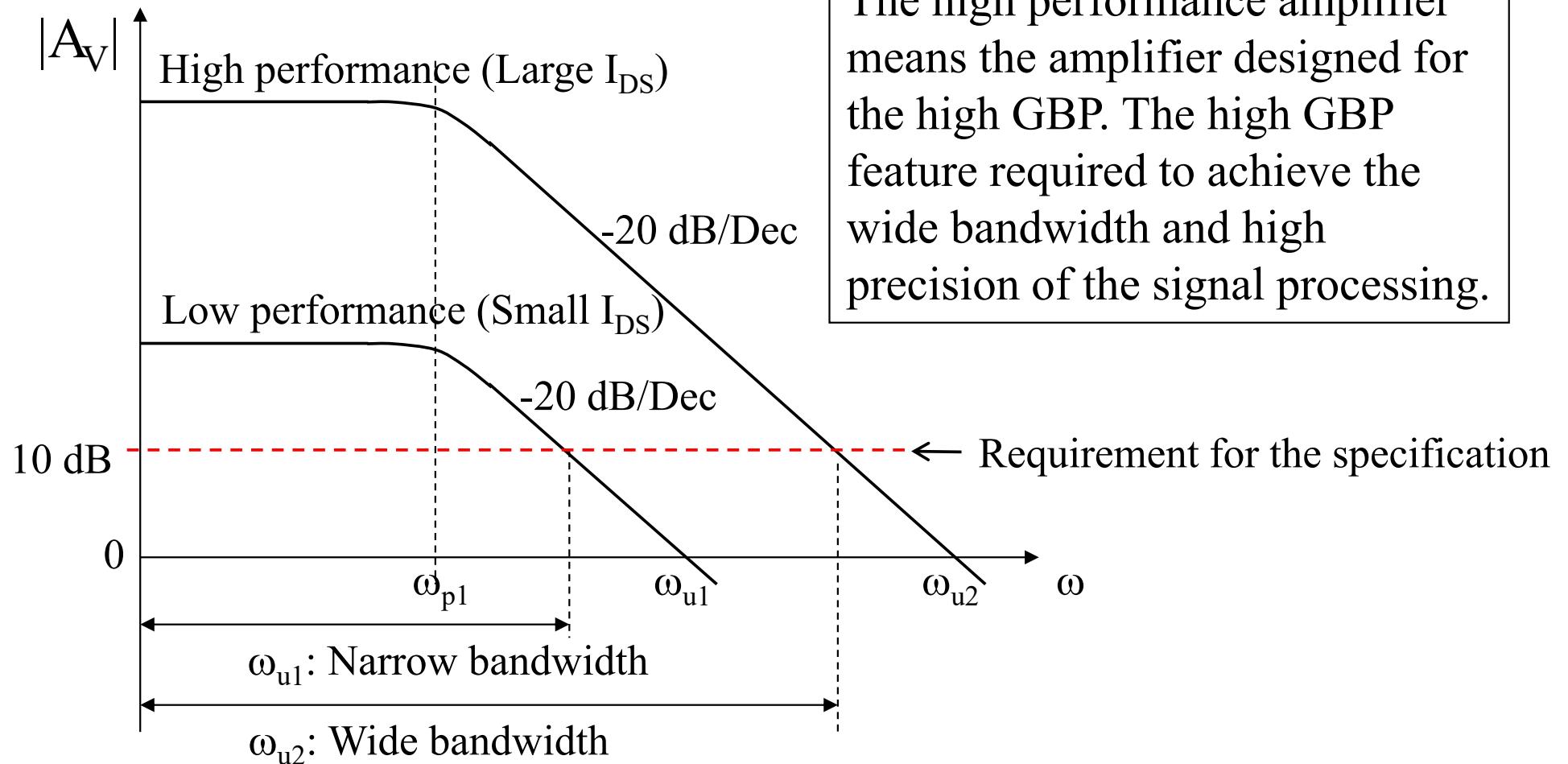
# GBP as a figure of merit (FOM) of amplifiers



## 11.4 Phase compensation

# NFB (Negative Feedback)

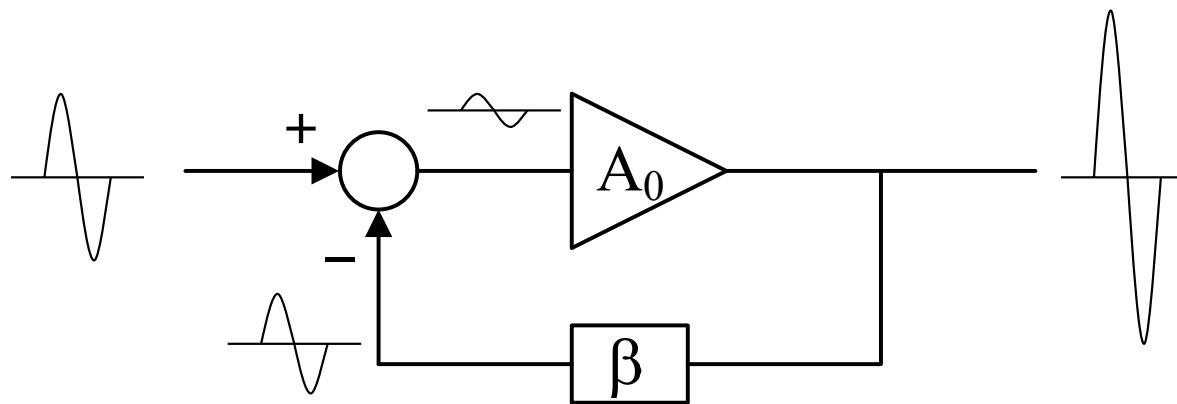


$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \beta \cdot A_0} \stackrel{A_0 \rightarrow \infty}{\cong} \frac{1}{\beta}$$

Harold Black, US Patent 1921


1. Precise control of transfer functions and stabilization of the gain
2. Suppression of the distortion
3. Extension of the frequency range
4. Suppression of the noise output to the output
5. Control of the input resistance and output resistance
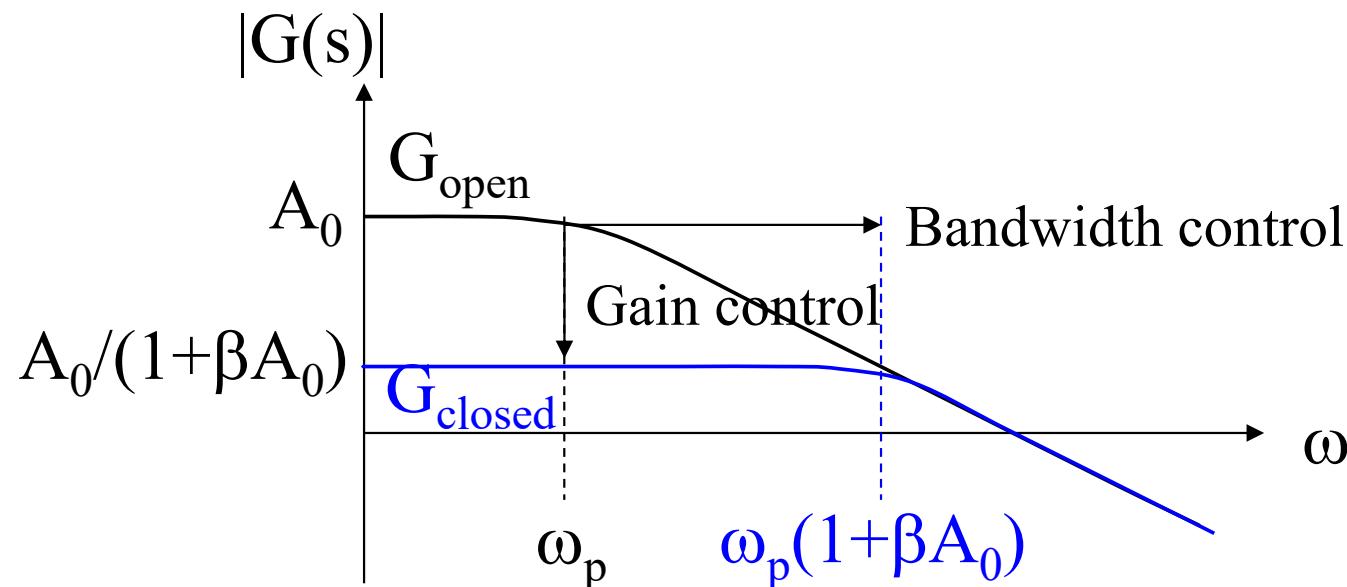
# Control of the gain and bandwidth

$$\left\{ \begin{array}{l} G_{open}(s) = \frac{A_0}{1 + s / \omega_p} \\ \\ G_{closed}(s) = \frac{A_0}{1 + \beta \cdot A_0} \frac{1}{1 + s / \omega_p(1 + \beta \cdot A_0)} \end{array} \right.$$



# NFB applied to multi-stage amplifier

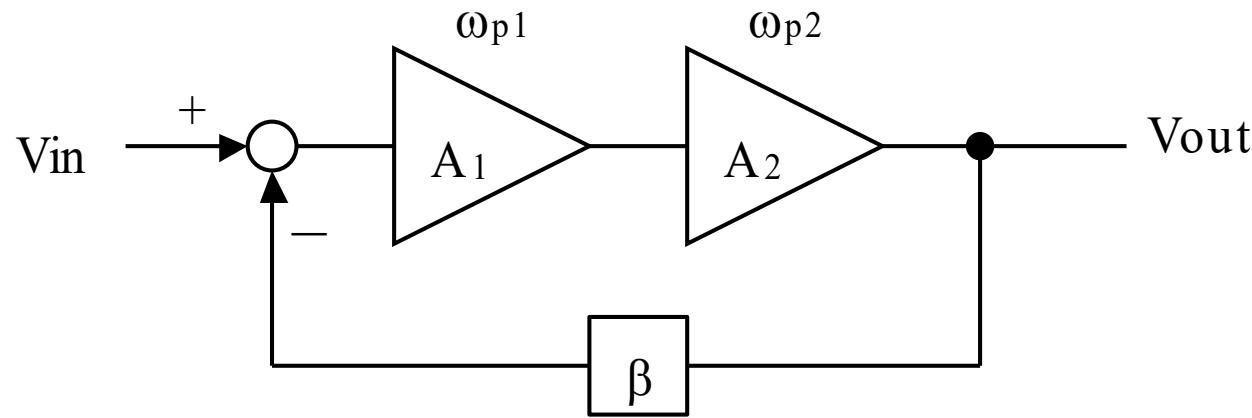


$$A_{total} = \frac{A_1 A_2}{1 + \beta \cdot A_1 A_2} \cong \frac{1}{\beta} \quad (A_1 A_2 \doteq \infty)$$

The effect of NFB is remarkable for the multi-stage amplifier, but  $\omega_{p1}$  and  $\omega_{p2}$  may be allocated in the neighbor frequency.
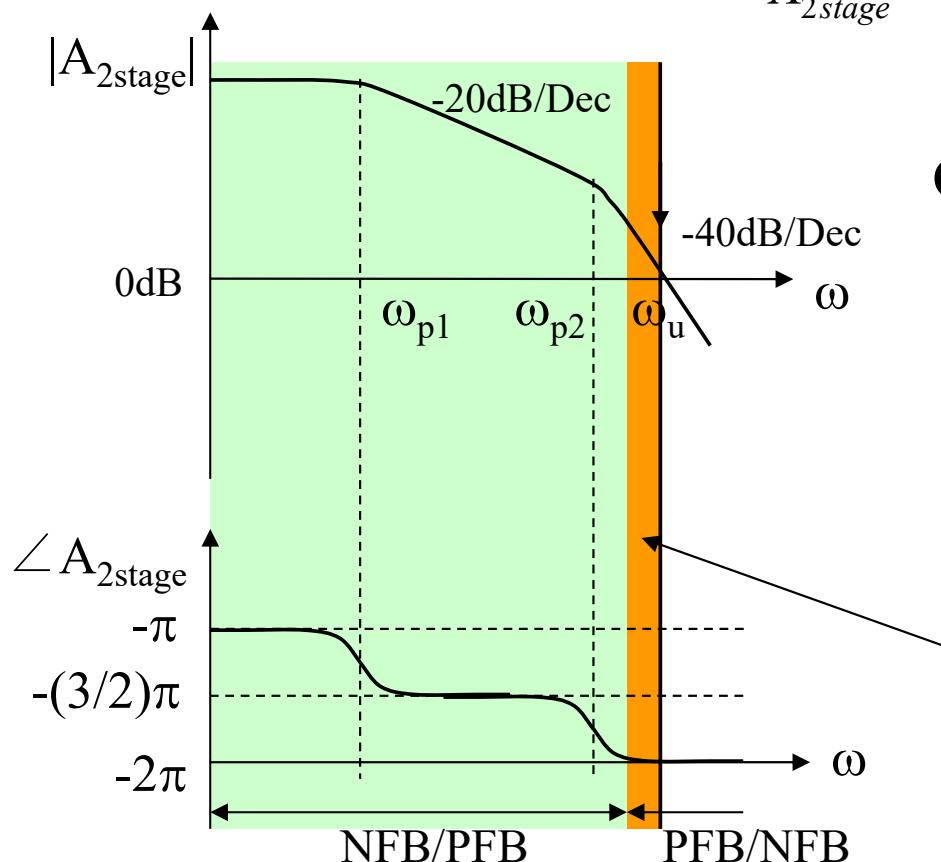
# Stability of the NFB circuit

Second  $\omega_p$  or  $\omega_z$  may causes the positive feedback and there is a problem in the circuit stability.



$$A_{2\text{stage}} = A_1(\omega)A_2(\omega) = \frac{A_0}{(1 + j\omega/\omega_{p1})(1 + j\omega/\omega_{p2})}$$


Oscillation condition of the loop gain

$$\begin{cases} -\beta \cdot A = \frac{-\beta \cdot A_0}{(1 + j\omega/\omega_{p1})(1 + j\omega/\omega_{p2})} \\ |-\beta \cdot A| \geq 0(\text{dB}) \\ \angle -\beta \cdot A = \pm 2\pi(\text{rad}) \end{cases}$$

In this frequency region, the NFB circuit works as a positive feedback (PFB) system.
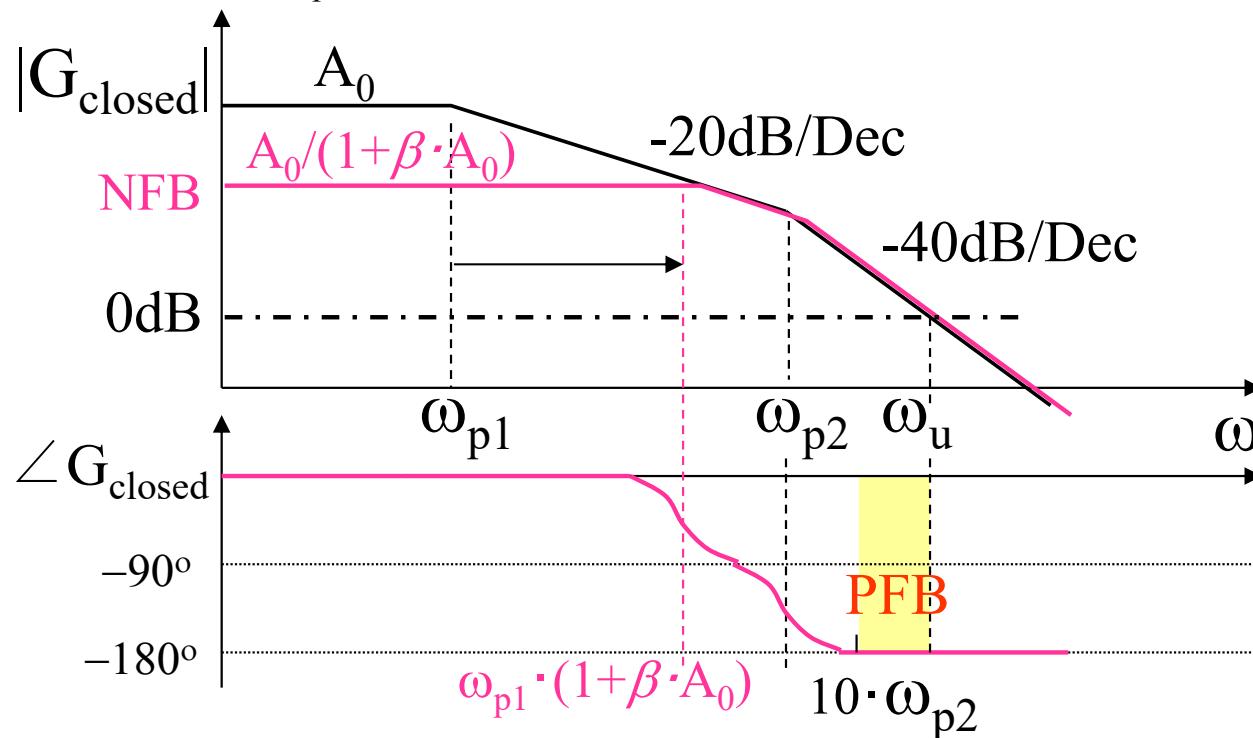
# Closed loop AC characteristic

$$\begin{aligned}
 A_{closed}(s) &= \frac{A_{open}(s)}{1 + \beta \cdot A_{open}(s)} = \frac{A_0(\text{const.})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2}) + \beta \cdot A_0(\text{const.})} \\
 &\approx \frac{A_0/(1 + \beta \cdot A_0)}{1 + s/\omega_{p1}(1 + \beta \cdot A_0)} \quad \text{, where } s/\omega_{p1} \gg s/\omega_{p2}
 \end{aligned}$$



# Displacement of the pole frequency

$$A_{closed}(s) = \frac{A_0}{(1+s/P\omega_{p1})(1+s/Q\omega_{p2})} \leftarrow \text{move the } \omega_{p1} \text{ and } \omega_{p2}$$


P and Q are set by the addition of feedback element  $\beta(s)$ .

$$\begin{aligned} A_{closed}(s) &= \frac{A_{open}(s)}{1 + \beta(s)A_{open}(s)} = \frac{A_0}{(1+s/\omega_{p1})(1+s/\omega_{p2}) + \beta(s)A_0} \quad \text{1st order} \\ &\equiv \frac{A_0}{(1+s/P\omega_{p1})(1+s/Q\omega_{p2})} = \frac{A_0}{(1+s/\omega_{p1})(1+s/\omega_{p2}) + sY} \end{aligned}$$
$$Y = \left(\frac{1}{P} - 1\right) \frac{1}{\omega_{p1}} + \left(\frac{1}{Q} - 1\right) \frac{1}{\omega_{p2}} \quad \text{But the P and Q cannot set independently, because the constraint } P \cdot Q = 1 \text{ is imposed.}$$


We can add the feedback loop to become  $\beta(s) = Y/A_0 * s$  to separate two pole each other by  $\omega_{p1} \rightarrow P \cdot \omega_{p1}$ ,  $\omega_{p2} \rightarrow Q \cdot \omega_{p2}$ .<sub>28</sub>
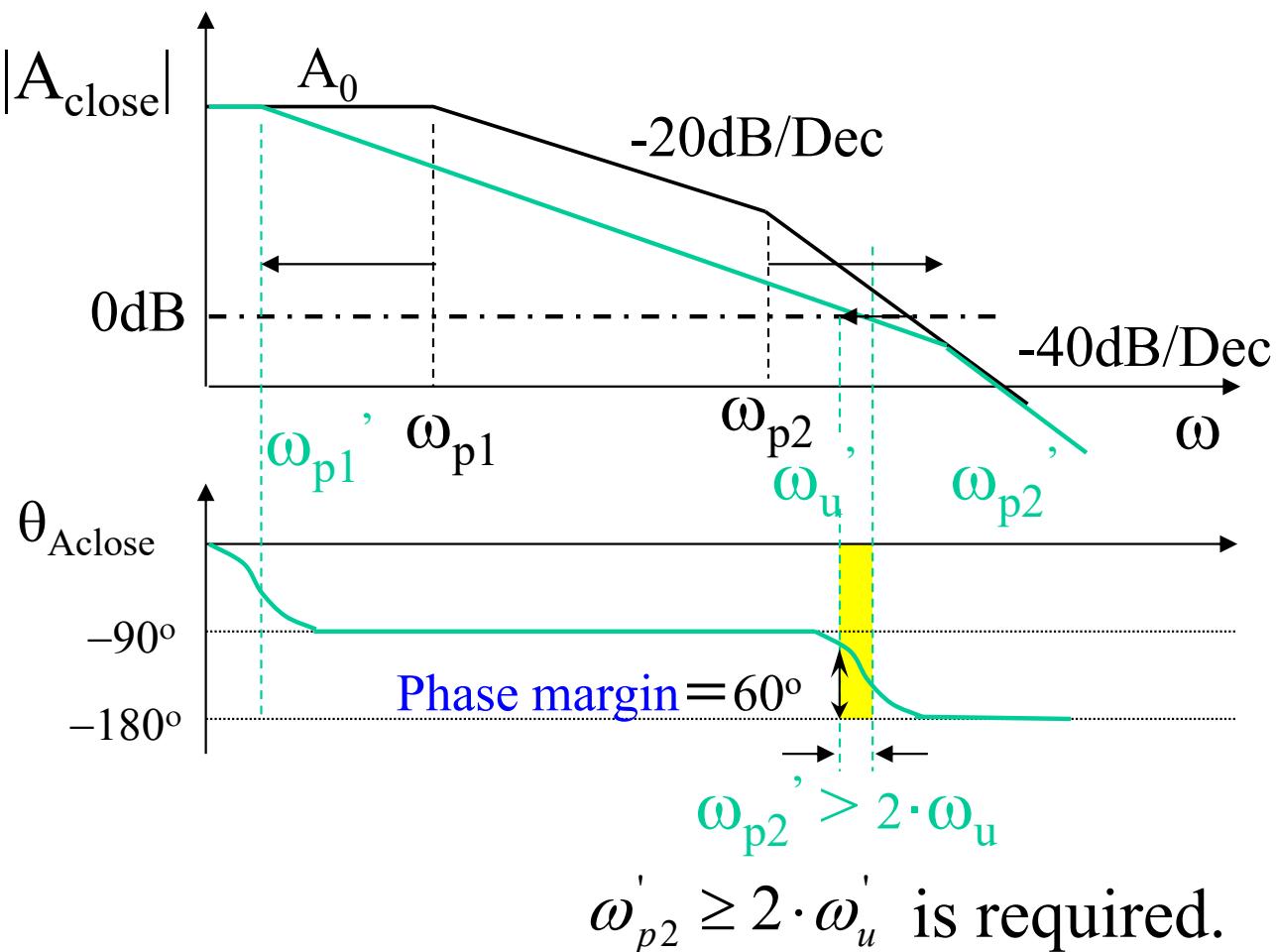
# Phase compensation

Phase margin  $> 60^\circ \rightarrow$  Stability of the NFB loop is compensated for the unity gain configuration ( $\beta = 1$ ).




# Phase margin of the voltage follower

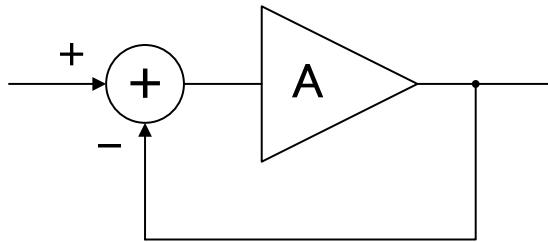


$$Gain = \frac{1}{1 + \frac{1}{A}}$$

$$A = e^{j(\pi - \theta)}$$

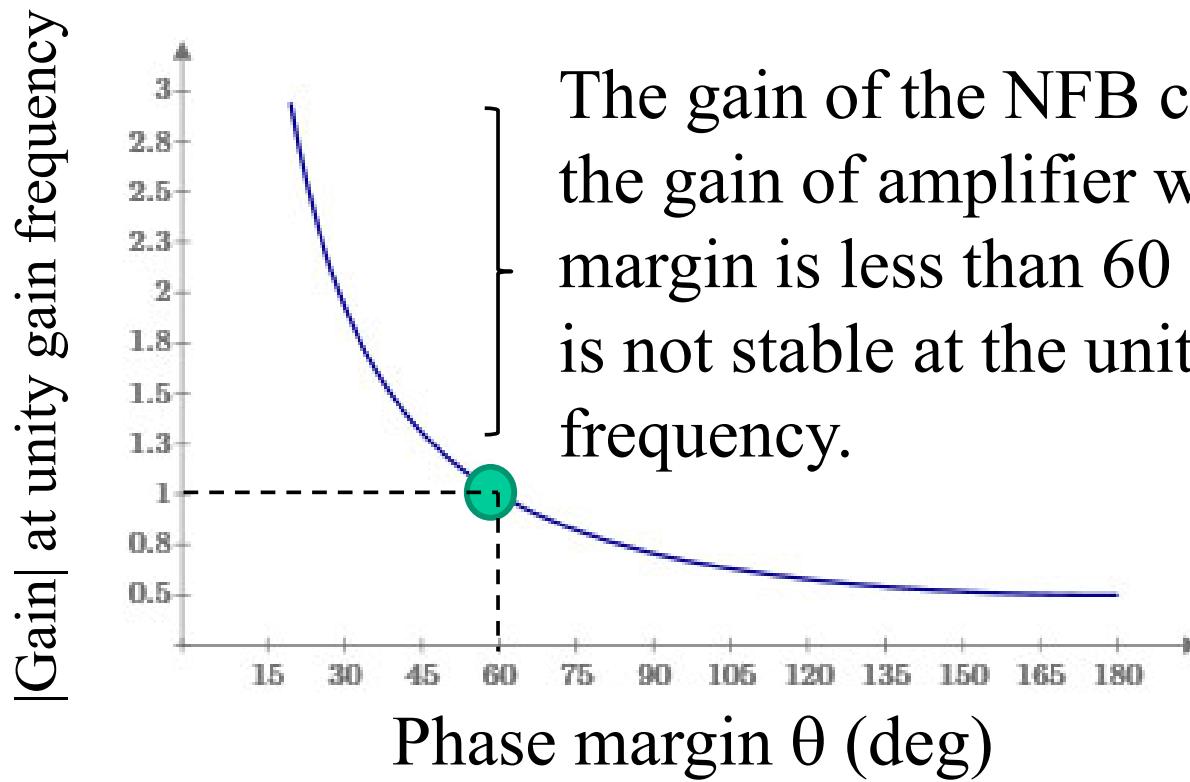

The gain of the NFB circuit exceeds the gain of amplifier when the phase margin is less than 60 deg. This circuit is not stable at the unity gain frequency.

# Design example (1)

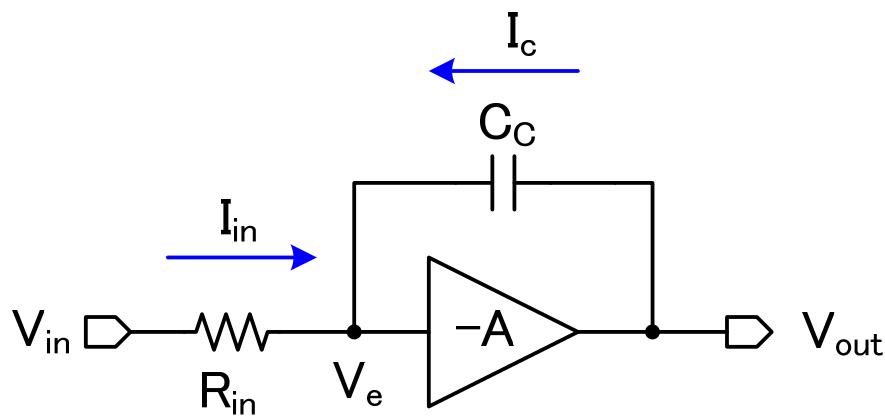

$$A(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

Phase compensation circuit of 2-pole amplifier

$$I_{in} = \frac{V_{in} - V_e}{R_{in}}$$

$$I_C = j\omega \cdot C_C (V_{out} - V_e) \cong j\omega \cdot C_C V_{out}$$


$$I_{in} + I_C = 0$$

$$\frac{V_{in} - V_e}{R_{in}} + j\omega \cdot C_C V_{out} = 0, \quad V_{out} = -AV_e$$

$$\begin{aligned} A_{Comp}(s) &= \frac{V_{out}}{V_{in}} = \frac{-A}{1 + j\omega \cdot C_C R_{in} A} \\ &= \frac{-A_0}{(1 + j\omega / \omega_{p1})(1 + j\omega / \omega_{p2}) + j\omega \cdot C_C R_{in} A_0} \\ &\equiv \frac{-A_0}{(1 + j\omega / \omega_{p1})(1 + j\omega / \omega_{p2}) + j\omega \cdot Y} \end{aligned}$$

NOTE: By Miller effect,  $C_C$  is amplified  $A_0 C_C$ , the time constant ( $Y$ ) introduced by the compensation is enlarged by  $Y = (A_0 C_C) R_{in}$  with the small  $C_C$ .

# Design example (2)

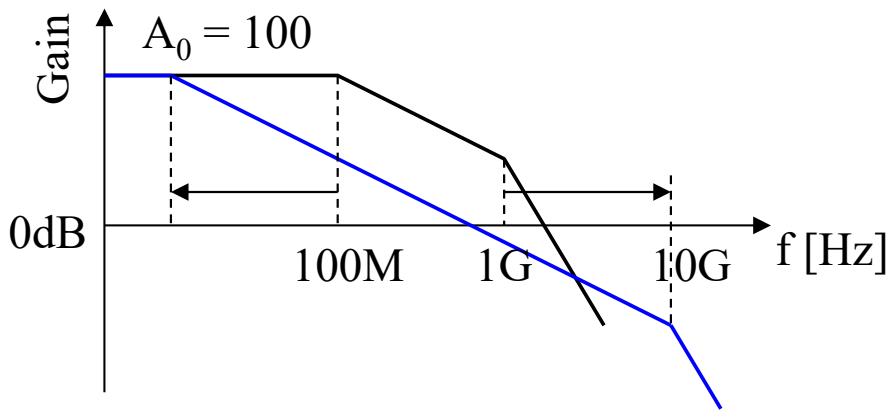

$$\begin{aligned}
 A_{Comp}(s) &= \frac{-A_0}{(1+s/\omega_{p1})(1+s/\omega_{p2})+sC_CRA_0} \\
 &= \frac{-A_0}{(1+s/P\omega_{p1})(1+s/Q\omega_{p2})} \\
 Y &= \left(\frac{1}{P}-1\right)\frac{1}{\omega_{p1}} + \left(\frac{1}{Q}-1\right)\frac{1}{\omega_{p2}} \\
 &= C_CRA_0
 \end{aligned}$$

If you set the parameters  $P = 1/10$ ,  $Q = 10$ ,

$$\begin{aligned}
 Y &= \left(\frac{1}{P}-1\right)\frac{1}{\omega_{p1}} + \left(\frac{1}{Q}-1\right)\frac{1}{\omega_{p2}} \\
 &= \frac{10-1}{2\pi \cdot 100M} + \frac{0.1-1}{2\pi \cdot 1G} = 1.27 \cdot 10^{-8} (s)
 \end{aligned}$$

$$C_C = \frac{Y}{RA_0} = \frac{1.27 \cdot 10^{-8} [s]}{100 [\Omega] \cdot 100} = 1.27 (\text{pF})$$

$$\begin{cases} R_{in} = 100 (\Omega) \\ C_C = 1.27 (\text{pF}) \end{cases}$$