

Lab. 13

**DESIGN AND  
CHARACTERIZATION OF  
FULL-DIFFERENTIAL OPA**

# 1. Design of full-differential OPA

- Determine the sizes of the MOSFETs and fill in the blank of Table I.
  - The area and perimeter of MOFET are given by  $W*3u$  and  $W+6u$ , respectively.

Target specifications

Parameter	Unit	Value	Remarks
GBP	Hz	40M	CL = 1.0pF
$A_d$	dB	100	@ 10Hz
Phase Margin	degree	60	
Slew Rate	V/us	10	CL = 1.0pF
Bias Current	A	200u	
Reference Current	A	10u	$I_{SS} = 20uA$

# Table I

## Folded-cascode differential amplifier

MOSFET	L(m)	W(m)	M	AD, AS(m <sup>2</sup> )	PD, PS(m)	W/L
M1, M2						
M3, M4, M7-M10	2u	10u	3	30p	16u	15
M5, M6, M11-M13	2u	10u	1	30p	16u	5

The size of M1 and M2 can be estimated from the GBP and CL.

## CMFB

MOSFET	L(m)	W(m)	M	AD, AS(m <sup>2</sup> )	PD, PS(m)	W/L
M1-M4	2u	16u	8	48p	22u	64
M5-M12						
M13-M16	2u	10u	1	30p	16u	5

Remember that the CMFB circuit is a replica of the current source load of the amplifier.

# Table II

## BIAS


MOSFET	L(m)	W(m)	M	AD, AS(m <sup>2</sup> )	PD, PS(m)	W/L
p-ch MOSFET	2u	10u	3	30p	16u	15
n-ch MOSFET	2u	10u	1	30p	16u	5

$$\Delta_{OV\_p-ch} = \sqrt{\frac{2I_{DS}}{\beta_p}} = \sqrt{\frac{2 \cdot 10\mu A}{33\mu A/V^2 \cdot 15}} = 0.201V \quad \Delta_{OV\_n-ch} = \sqrt{\frac{2I_{DS}}{\beta_n}} = \sqrt{\frac{2 \cdot 10\mu A}{98\mu A/V^2 \cdot 5}} = 0.202V$$


## BMR

MOSFET	L(m)	W(m)	M	AD, AS(m <sup>2</sup> )	PD, PS(m)	W/L
M1, M3, M4, M9, M10	2u	10u	1	30p	16u	5
M2	2u	10u	4	30p	16u	20
M5-M8	2u	10u	3	30p	16u	15
M11-M29	5u	5u	1	115p	11u	1


# Folded cascode differential amplifier

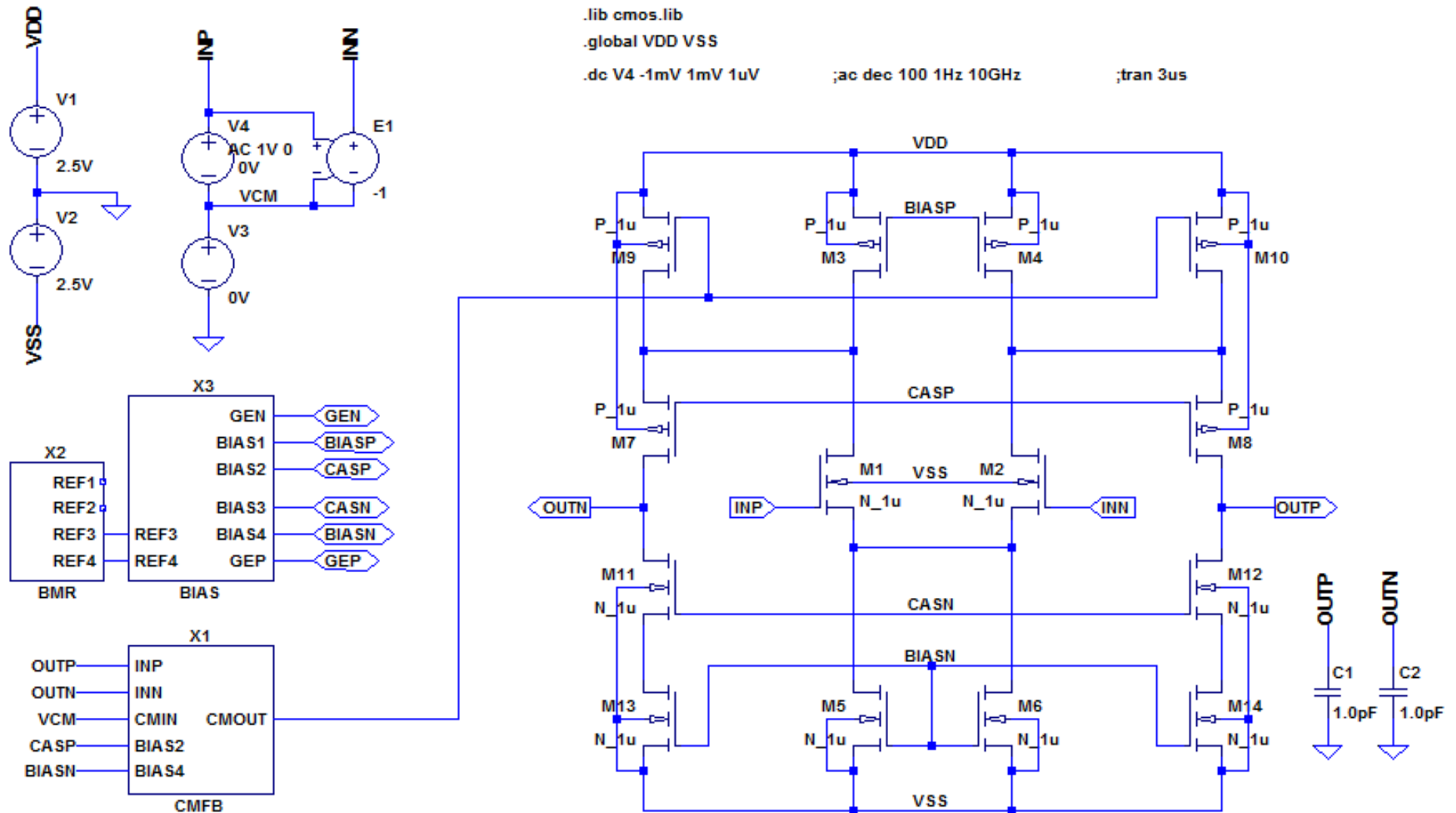


# CMFB

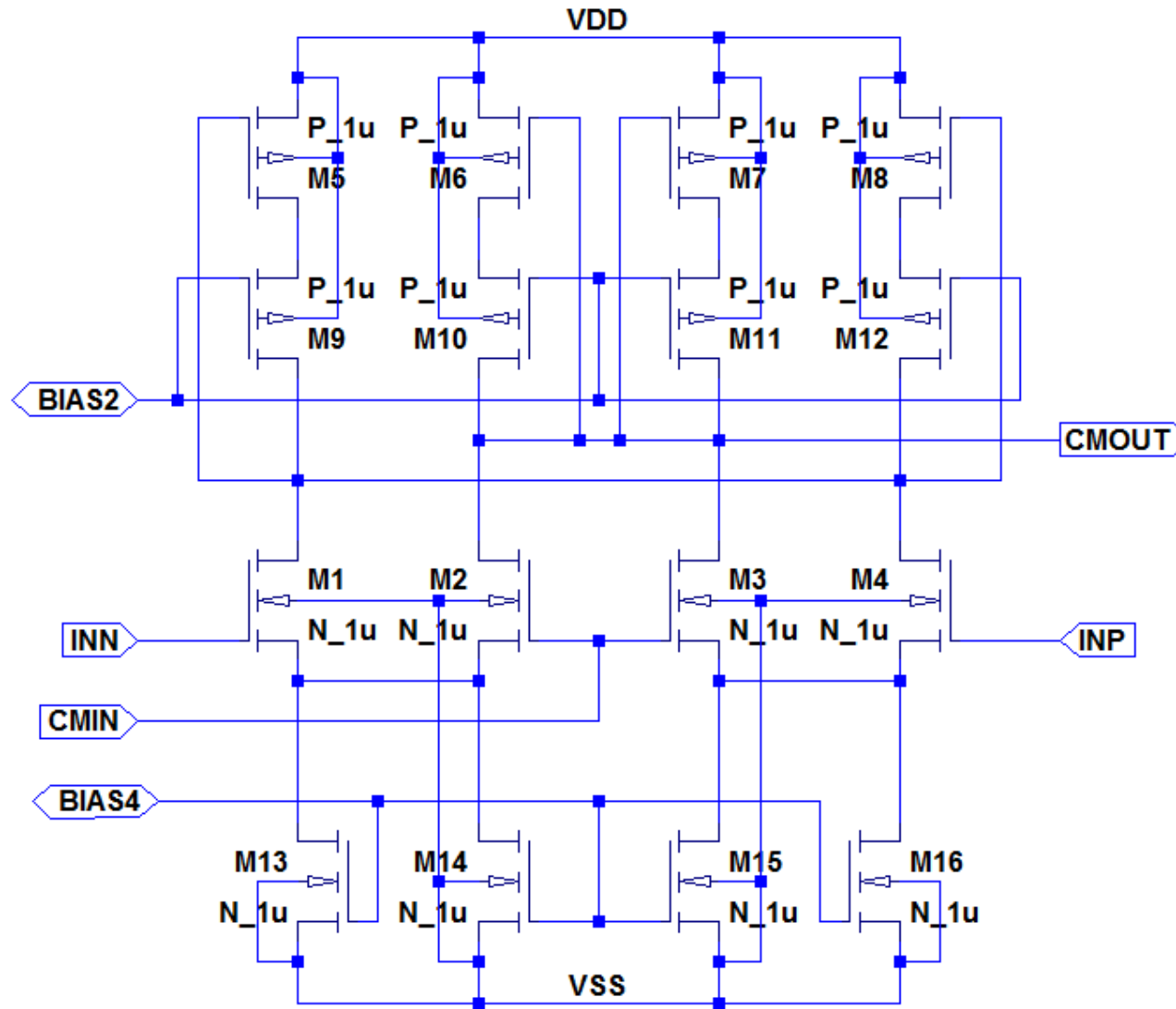

# Bias

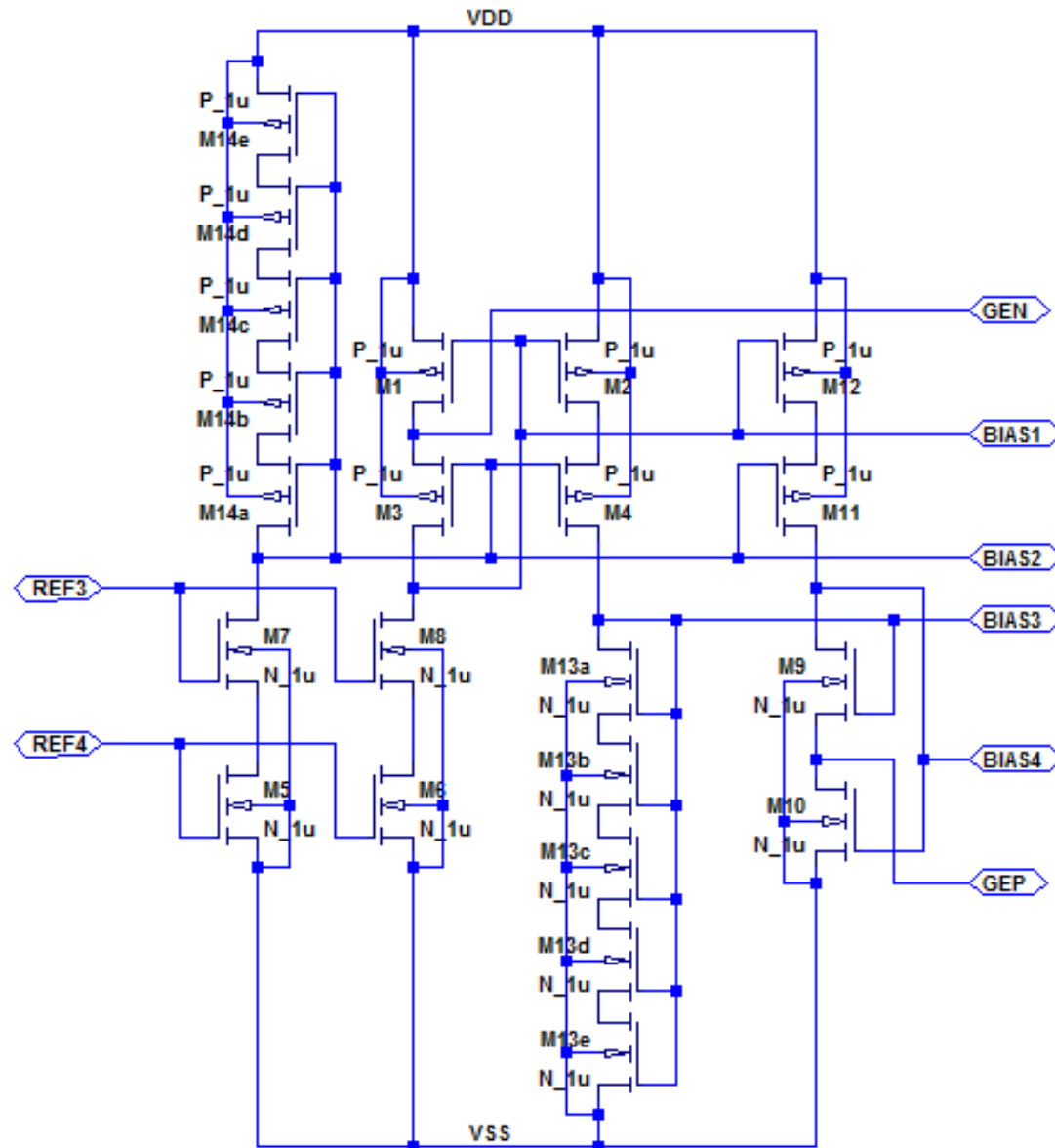

# BMR

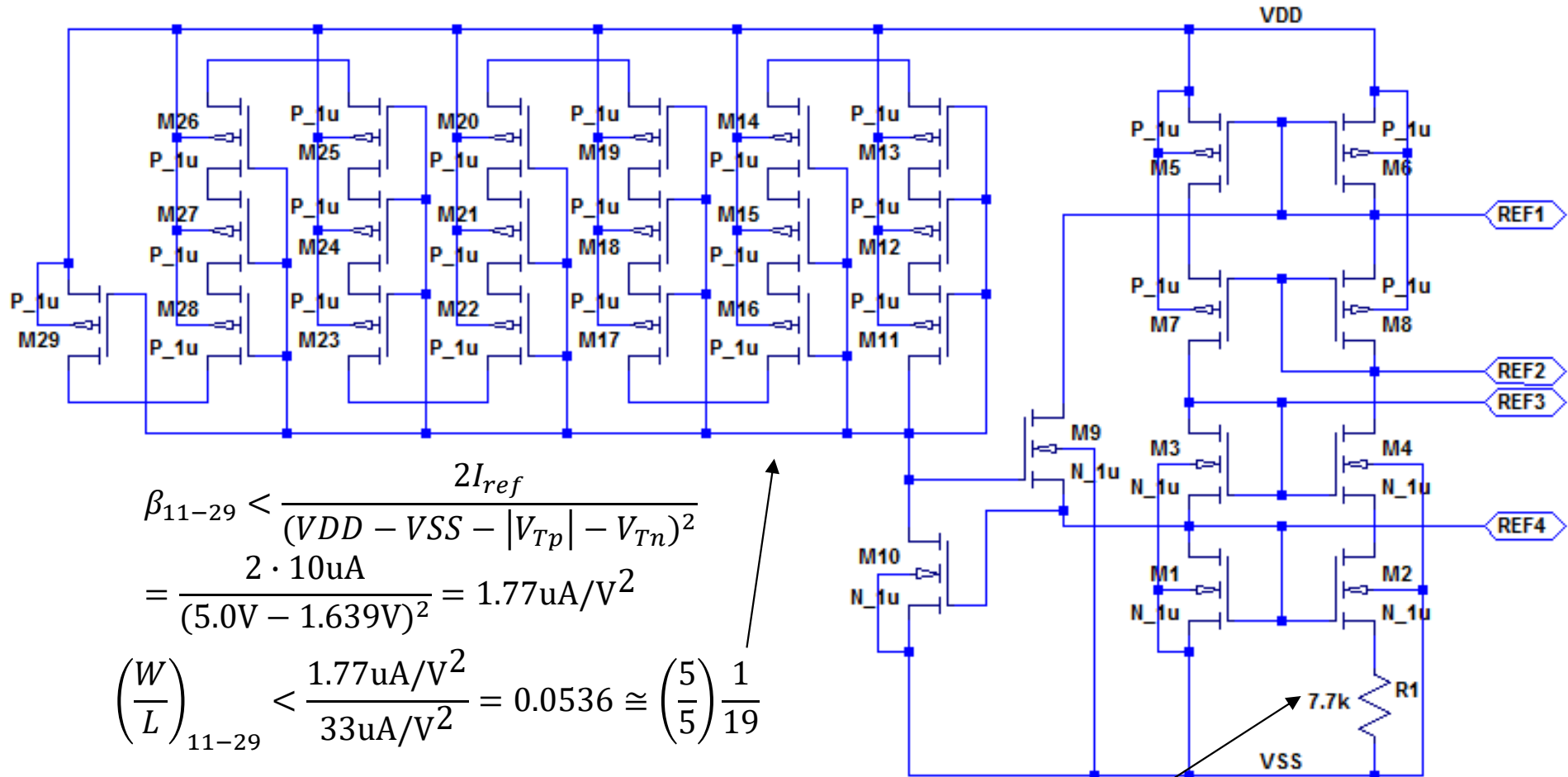

$$\beta_{11-29} < \frac{2I_{ref}}{(VDD - VSS - |V_{Tp}| - V_{Tn})^2}$$

$$= \frac{2 \cdot 10\mu A}{(5.0V - 1.639V)^2} = 1.77\mu A/V^2$$

$$\left(\frac{W}{L}\right)_{11-29} < \frac{1.77\mu A/V^2}{33\mu A/V^2} = 0.0536 \approx \left(\frac{5}{5}\right) \frac{1}{19}$$

$$R1 = \sqrt{\frac{2}{\beta_1 I_{ref}}} \left(1 - \frac{1}{\sqrt{K}}\right) = \sqrt{\frac{2}{98\mu A/V^2 \cdot 5 \cdot 10\mu A}} \left(1 - \frac{1}{\sqrt{4}}\right) = 10.1k\Omega \quad (\text{Adjusted})$$



## 2. Characterization

- Carry out the DC, AC, and TRAN analysis of the full-differential OPA and attach the simulation results to your report.
  - DC characteristic of  $V(\text{inp})$ ,  $V(\text{inn})$ ,  $V(\text{outp})$ ,  $V(\text{outn})$ ,  $V(\text{cmfb})$ ,  $I_d(\text{M1})$ ,  $I_d(\text{M2})$ , and  $I(V1)$ 
    - Check the offset voltage. The systematic offset should be removed by the CMFB.
  - AC characteristic of  $V(\text{outp})$  and  $V(\text{outn})$
  - The step response (TRAN characteristics) of  $V(\text{inp})$ ,  $V(\text{inn})$ ,  $V(\text{outp})$ , and  $V(\text{outn})$
- Fill out the blank in Table III by using your simulation results.

# Table III

- The specification estimated by the simulation.

Parameter	Unit	Value	Remarks
GBP	Hz		CL = 1.0pF
A <sub>d</sub>	dB		@ 10Hz
Phase Margin	degree		
Slew Rate	V/us		CL = 1.0pF
Total Bias Current	A		
Reference Current	A		I <sub>SS</sub> /2