


Lab. 14

# **CHARACTERIZATION OF OUTPUT BUFFER**

# 1. Output swing

- Carry out the DC analysis of the class-AB buffer shown in the next slide. Use 20 k $\Omega$  load resistor ( $R_L$ ).
- Observe the output voltage swing and the output current swing for the input voltage swept from -2.2V to 2.2V.

# Schematic

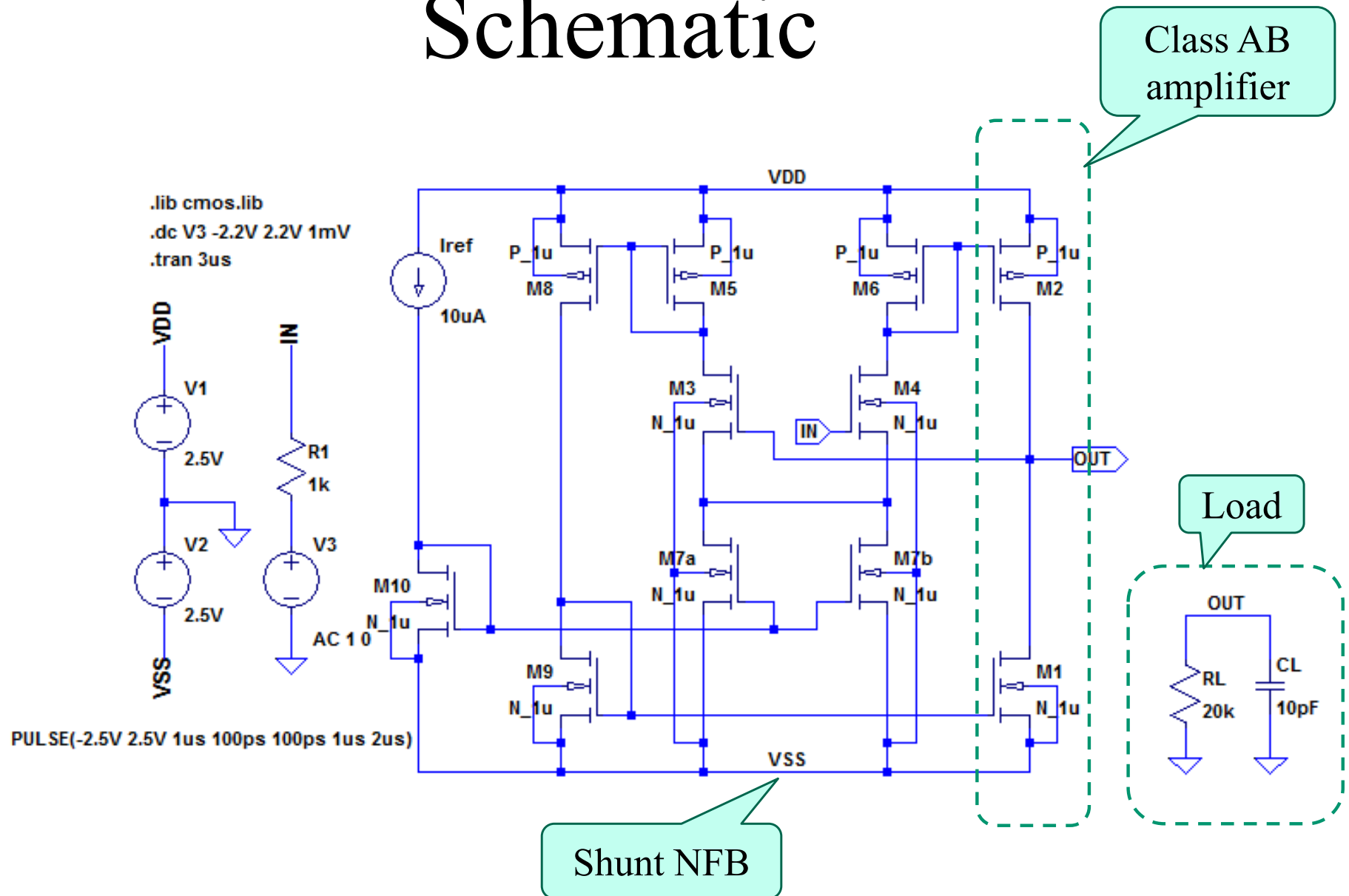

# Parameters

MOSFET	L(m)	W(m)	M	AD, AS(m <sup>2</sup> )	PD, PS(m)	W/L
M1, M9	2u	14u	8	42p	20u	56
M2, M8	2u	10u	33	30p	16u	165
M3, M4	2u	13u	16	39p	19u	104
M5,M6	2u	10u	3	30p	16u	15
M7a, M7b	2u	10u	1	30p	16u	5
M10	2u	10u	2	30p	16u	10

## 2. Transient response

- Carry out the step response analysis. Remove 20 k $\Omega$  load resistor (RL) and put in the load capacitance of 10pF.
- Observe the output voltage and  $SR = dV(\text{out})/d(\text{time})$ , and measure the value of slew rate at  $V(\text{out}) = 0V$ .

# Setting of the input pulse

**Independent Voltage Source - V3** [X]

Functions

- (none)
- PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Voff Vamp Fcar MDI Fsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE:

Vinitial[V]:   
Von[V]:   
Tdelay[s]:   
Trise[s]:   
Tfall[s]:   
Ton[s]:   
Tperiod[s]:   
Ncycles:

Make this information visible on schematic:

DC Value

DC value:

Make this information visible on schematic:

Small signal AC analysis(.AC)

AC Amplitude:   
AC Phase:

Make this information visible on schematic:

Parasitic Properties

Series Resistance[Ω]:   
Parallel Capacitance[F]:

Make this information visible on schematic:

# 3. Output resistance

- Draw up the schematic to measure the output resistance and run the AC analysis for the frequency range of 1Hz - 50MEGHz.
  - Output resistance is defined as a small-signal resistance of the output node when the input signal amplitude is zero.
- Plot the output resistance  $V(\text{out})/(-I(V3))$  and read out the value at 1kHz.

