


Lab. 15

# **CHARACTERIZATION OF CLOCKED COMPARATOR**



# 1. Characterization

- Carry out the TRAN analysis of the clocked comparator and attach the simulation results to your report.
  - $V(\text{inp})$ ,  $V(\text{inn})$ ,  $V(\text{outp})$ ,  $V(\text{vdn})$ ,  $V(\text{vdp})$ , and  $V(\text{clk})$
- Evaluate the comparison accuracy by simulation.
  - The accuracy depends on the clock frequency. Try to operate at  $f_{\text{clk}} = 10\text{MHz}$  ( $T_{\text{period}} = 100\text{ns}$ ).
  - The accuracy depends on the common mode voltage too. Evaluate the comparison accuracy for  $V_{\text{CM}} = -1.0\text{V}$ ,  $0.0\text{V}$ , and  $1.0\text{V}$ .

# Schematic

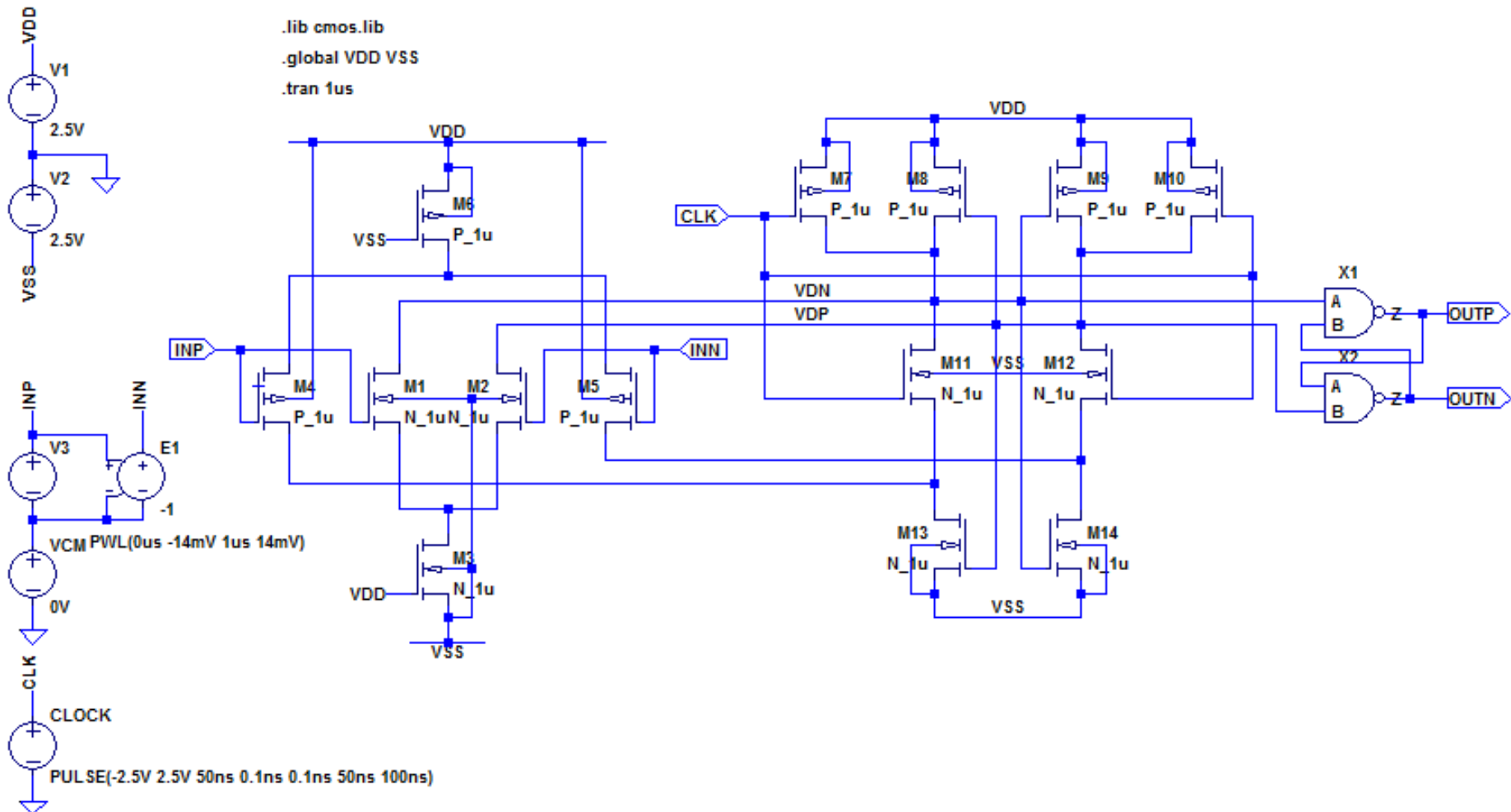

# Clock pulse and input voltage

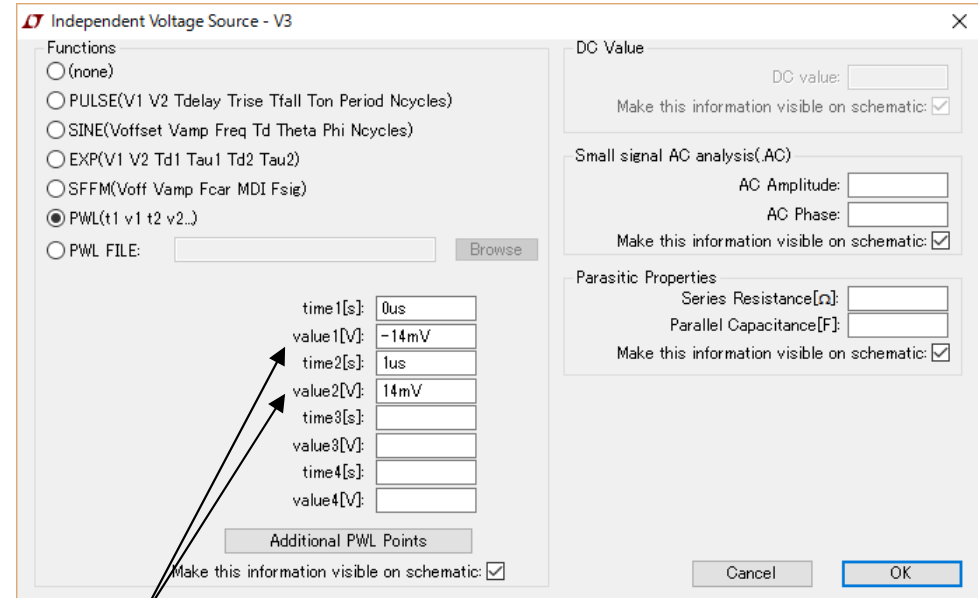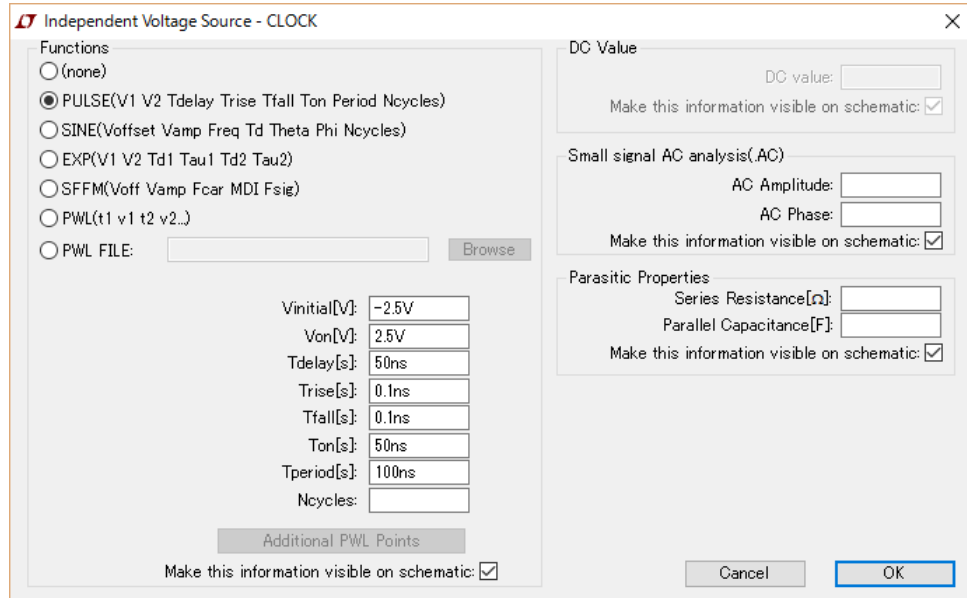


Change the Value1 and Value2 to evaluate the comparison accuracy.

# MOSFET parameters

MOSFET	L(m)	W(m)	M	AD, AS(m <sup>2</sup> )	PD, PS(m)	W/L
M1, M2	2u	10u	2	30p	16u	10
M3	4u	20u	2	60p	26u	10
M4, M5	2u	10u	6	30p	16u	30
M6	4u	20u	6	60p	26u	30
M7-M10	2u	10u	3	30p	16u	15
M11-M14	2u	10u	1	30p	16u	5

# NAND2 schematic

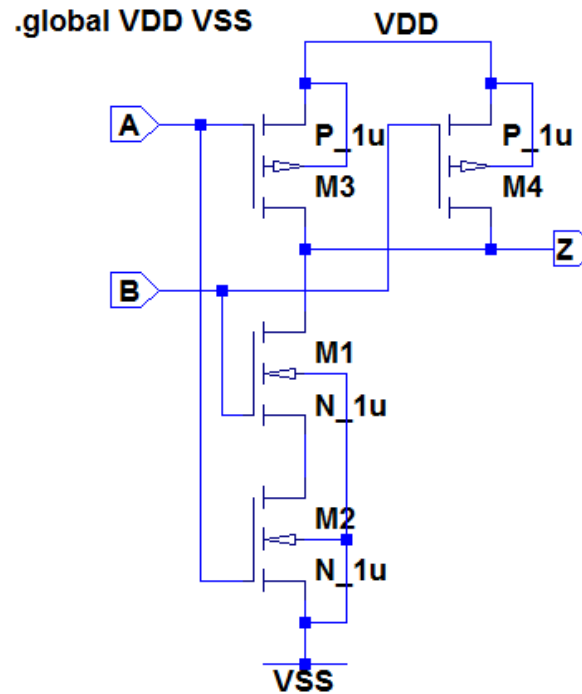

MOSFET	L(m)	W(m)	M	AD, AS(m <sup>2</sup> )	PD, PS(m)	W/L
M1, M2	1u	5u	4	15p	11u	5
M3, M4	1u	15u	1	45p	21u	15